

SS/SS

1. (a) i. First, let's find  $V_{n,out}^2$ . The noise contributions from  $R_S$ ,  $R_D$ , and  $M_1$  all appear as uncorrelated current sources flowing through  $R_S \parallel R_D \parallel R_{in}$  (where  $R_{in}$  is the input resistance excluding  $R_S$  and  $R_D$ ), which then experience a gain of 1 to the output (since  $M_2$  is biased by an ideal current source). The noise current of  $M_2$  flows to the output directly and gets converted to a voltage via  $R_{out}$ .

$$\begin{aligned} V_{n,out}^2 &= (\overline{I_{RS}^2} + \overline{I_{RD}^2} + \overline{I_{D1}^2}) (R_S \parallel R_D \parallel R_{in})^2 + \overline{I_{D2}^2} R_{out}^2 \\ &= (4kT/R_S + 4kT/R_D + 4kT\gamma g_{m1}) (R_S \parallel R_D \parallel R_{in})^2 + 4kT\gamma g_{m2} R_{out}^2 \end{aligned}$$

We can see that  $R_{in} = 1/g_{m1}$ , since  $v_{gs2} = 0$  in the small-signal model means  $M_1$  is effectively diode-connected for small-signal purposes.

Fig. 1 shows the test setup we'll use to find  $R_{out}$ .

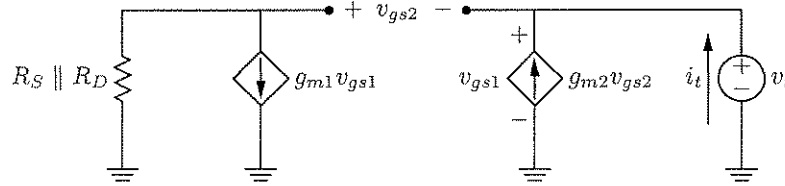


Figure 1: Test setup for finding  $R_{out}$

$$\begin{aligned} i_t &= -g_{m2}v_{gs2} \\ v_{gs2} &= -g_{m1}v_{gs1} (R_S \parallel R_D) - v_t \\ v_{gs1} &= v_t \\ v_{gs2} &= -v_t [g_{m1} (R_S \parallel R_D) + 1] \\ i_t &= g_{m2}v_t [g_{m1} (R_S \parallel R_D) + 1] \\ R_{out} &= \frac{v_t}{i_t} = \frac{1}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]} \end{aligned}$$

Thus, we have:

$$\begin{aligned} V_{n,out}^2 &= 4kT \left[ \left( 1/R_S + 1/R_D + \gamma g_{m1} \right) \left( R_S \parallel R_D \parallel \frac{1}{g_{m1}} \right)^2 + \gamma g_{m2} \left( \frac{1}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]} \right)^2 \right] \\ &= 4kT \left[ \left( \frac{1}{R_S \parallel R_D} + \gamma g_{m1} \right) \left( R_S \parallel R_D \parallel \frac{1}{g_{m1}} \right)^2 + \frac{\gamma}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]^2} \right] \\ NF &= \frac{V_{n,out}^2}{A^2} \frac{1}{4kT R_S} \\ A &= \frac{R_D \parallel \frac{1}{g_{m1}}}{\left( R_D \parallel \frac{1}{g_{m1}} \right) + R_S} \\ NF &= \frac{1}{R_S} \left( 1 + \frac{R_S}{R_D \parallel \frac{1}{g_{m1}}} \right)^2 \left[ \left( \frac{1}{R_S \parallel R_D} + \gamma g_{m1} \right) \left( R_S \parallel R_D \parallel \frac{1}{g_{m1}} \right)^2 + \frac{\gamma}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]^2} \right] \\ &= R_S \left( \frac{1}{R_S \parallel R_D \parallel \frac{1}{g_{m1}}} \right)^2 \left[ \left( \frac{1}{R_S \parallel R_D} + \gamma g_{m1} \right) \left( R_S \parallel R_D \parallel \frac{1}{g_{m1}} \right)^2 + \frac{\gamma}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]^2} \right] \end{aligned}$$

$$\begin{aligned}
&= 1 + \frac{R_S}{R_D} + \gamma g_{m1} R_S + \frac{\gamma R_S (1/R_S + 1/R_D + g_{m1})^2}{g_{m2} [g_{m1} (R_S \parallel R_D) + 1]^2} \\
&= \boxed{1 + \frac{R_S}{R_D} + \gamma g_{m1} R_S + \frac{\gamma R_S}{g_{m2} (R_S \parallel R_D)^2}} \quad \checkmark \quad \textcircled{g_{m2}} \\
\lim_{R_D \rightarrow \infty} NF &= \boxed{1 + \gamma g_{m1} R_S + \frac{\gamma}{g_{m2} R_S}} \quad \checkmark \quad \textcircled{g_{m2}}
\end{aligned}$$

As we let  $R_D \rightarrow \infty$ , the contribution to the noise figure from  $R_D$  goes to zero, and the contribution to the noise figure from  $M_2$  decreases. Intuitively, we know that the noise current squared from  $R_D$  goes as  $1/R_D$  while the input resistance (which the noise flows through) is limited by  $(R_S \parallel 1/g_{m1})$ . Thus, as  $R_D$  increases, the noise current drops out while the input resistance stays finite, causing the noise contribution to drop out.

Similar intuition applies to the decrease in noise from  $M_2$ . We see that  $R_{out}$  decreases as  $R_D$  increases. Since the noise current of  $M_2$  flows through  $R_{out}$ , we can see that as  $R_D$  increases, the noise contribution from  $M_2$  will decrease.

- ii. Let  $R_{in}$  be the input resistance excluding  $R_S$ ,  $R_{out}$  the output resistance excluding  $R_D$ , and  $A_v$  the gain excluding  $R_S$  (i.e., from the source to the drain of  $M_1$ ).

$$\begin{aligned}
V_{n,out}^2 &= \left( \overline{I_{RS}^2} + \overline{I_{D2}^2} \right) (R_S \parallel R_{in})^2 A_v^2 + \overline{I_{RD}^2} (R_D \parallel R_{out})^2 + \{ I_{D1} [(R_S \parallel R_{in}) A_v - (R_D \parallel R_{out})] \}^2 \\
&= \left( \overline{I_{RS}^2} + \overline{I_{D2}^2} \right) (R_S \parallel R_{in})^2 A_v^2 + \overline{I_{RD}^2} (R_D \parallel R_{out})^2 + \overline{I_{D1}^2} [(R_S \parallel R_{in}) A_v - (R_D \parallel R_{out})]^2
\end{aligned}$$

We need to find  $R_{in}$ ,  $R_{out}$ , and  $A_v$ . Let's use Fig. 2 to find  $R_{in}$ .

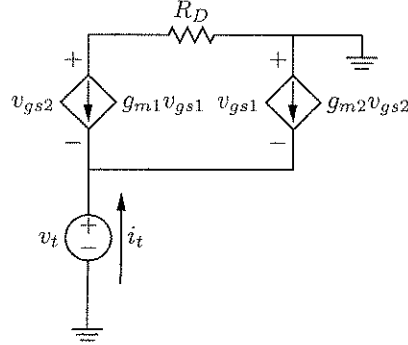


Figure 2: Test setup for finding  $R_{in}$ .

$$\begin{aligned}
i_t &= -g_{m1} v_{gs1} - g_{m2} v_{gs2} \\
v_{gs1} &= -v_t \\
v_{gs2} &= -g_{m1} v_{gs1} R_D - v_t \\
&= g_{m1} R_D v_t - v_t \\
&= v_t (g_{m1} R_D - 1) \\
i_t &= g_{m1} v_t - g_{m2} v_t (g_{m1} R_D - 1) \\
&= v_t [g_{m1} + g_{m2} (1 - g_{m1} R_D)] \\
R_{in} &= \frac{v_t}{i_t} = \frac{1}{g_{m1} + g_{m2} (1 - g_{m1} R_D)}
\end{aligned}$$

Let's use Fig. 3 to find  $R_{out}$ .

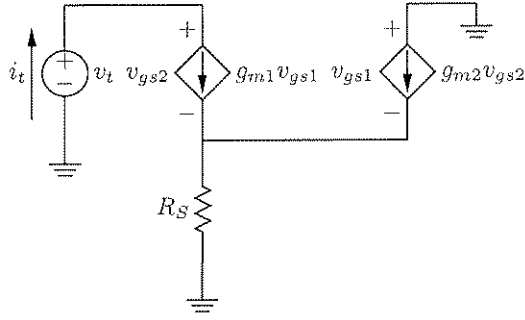


Figure 3: Test setup for finding  $R_{out}$

$$\begin{aligned}
 i_t &= g_{m1}v_{gs1} \\
 -v_{gs1} &= (i_t + g_{m2}v_{gs2})R_S \\
 v_{gs2} &= v_t + v_{gs1} \\
 -v_{gs1} &= (i_t + g_{m2}v_t + g_{m2}v_{gs1})R_S \\
 -v_{gs1}(1 + g_{m2}R_S) &= (i_t + g_{m2}v_t)R_S \\
 v_{gs1} &= -\frac{(i_t + g_{m2}v_t)R_S}{1 + g_{m2}R_S} \\
 i_t &= -g_{m1}\frac{(i_t + g_{m2}v_t)R_S}{1 + g_{m2}R_S} \\
 i_t\left(1 + \frac{g_{m1}R_S}{1 + g_{m2}R_S}\right) &= -\left(\frac{g_{m1}g_{m2}R_S}{1 + g_{m2}R_S}\right)v_t \\
 i_t\left(\frac{1 + (g_{m1} + g_{m2})R_S}{1 + g_{m2}R_S}\right) &= -\left(\frac{g_{m1}g_{m2}R_S}{1 + g_{m2}R_S}\right)v_t \\
 R_{out} = \frac{v_t}{i_t} &= -\frac{1 + (g_{m1} + g_{m2})R_S}{g_{m1}g_{m2}R_S}
 \end{aligned}$$

Let's use Fig. 4 to find  $A_v$ .

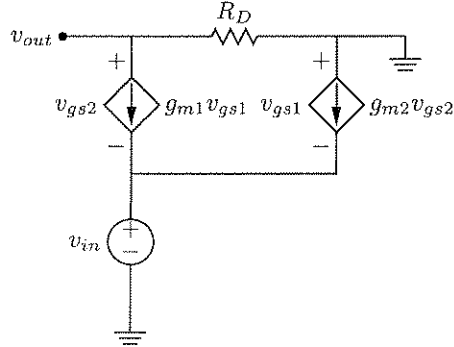


Figure 4: Test setup for finding  $A_v$

$$\begin{aligned}
 v_{out} &= -g_{m1}v_{gs1}R_D \\
 v_{gs1} &= -v_{in} \\
 v_{out} &= g_{m1}R_Dv_{in} \\
 A_v = \frac{v_{out}}{v_{in}} &= g_{m1}R_D
 \end{aligned}$$

Now we can write  $V_{n,out}^2$ :

$$\begin{aligned}
R_S \parallel R_{in} &= \frac{\frac{R_S}{g_{m1} + g_{m2}(1 - g_{m1}R_D)}}{R_S + \frac{1}{g_{m1} + g_{m2}(1 - g_{m1}R_D)}} \\
&= \frac{R_S}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \\
R_D \parallel R_{out} &= \frac{\frac{R_D + (g_{m1} + g_{m2})R_S R_D}{g_{m1}g_{m2}R_S}}{R_D - \frac{1 + (g_{m1} + g_{m2})R_S}{g_{m1}g_{m2}R_S}} \\
&= \frac{R_D + (g_{m1} + g_{m2})R_S R_D}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \\
V_{n,out}^2 &= 4kT \left\{ \left( \frac{1}{R_S} + \gamma g_{m2} \right) \left[ \frac{g_{m1}R_S R_D}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \right]^2 \right. \\
&\quad + \frac{1}{R_D} \left[ \frac{R_D + (g_{m1} + g_{m2})R_S R_D}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \right]^2 \\
&\quad \left. + \gamma g_{m1} \left[ \frac{g_{m1}R_S R_D - R_D - (g_{m1} + g_{m2})R_S R_D}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \right]^2 \right\} \\
&= \frac{4kT}{[1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D]^2} \left\{ \left( \frac{1}{R_S} + \gamma g_{m2} \right) (g_{m1}R_S R_D)^2 \right. \\
&\quad \left. + R_D [1 + (g_{m1} + g_{m2})R_S]^2 + \gamma g_{m1} R_D^2 [1 + g_{m2}R_S]^2 \right\} \\
NF &= \frac{V_{n,out}^2}{A^2} \frac{1}{4kT R_S} \\
A &= \frac{R_{in}}{R_S + R_{in}} A_v \checkmark \\
&= \frac{g_{m1}R_D}{1 + (g_{m1} + g_{m2})R_S - g_{m1}g_{m2}R_S R_D} \\
NF &= \frac{1}{(g_{m1}R_D)^2 R_S} \left\{ \left( \frac{1}{R_S} + \gamma g_{m2} \right) (g_{m1}R_S R_D)^2 + R_D [1 + (g_{m1} + g_{m2})R_S]^2 + \gamma g_{m1} R_D^2 (1 + g_{m2}R_S)^2 \right\} \\
&= \boxed{1 + \gamma g_{m2}R_S + \frac{\gamma}{g_{m1}R_S} (1 + g_{m2}R_S)^2 + \frac{1}{g_{m1}^2 R_S R_D} [1 + (g_{m1} + g_{m2})R_S]^2} \checkmark \textcircled{S_1} \\
\lim_{R_D \rightarrow \infty} NF &= \boxed{1 + \gamma g_{m2}R_S + \frac{\gamma}{g_{m1}R_S} (1 + g_{m2}R_S)^2} \checkmark \textcircled{S_2}
\end{aligned}$$

As we let  $R_D \rightarrow \infty$ , the contribution to the noise figure from  $R_D$  goes to zero, while all other terms remain the same. Intuitively, the noise current squared of  $R_D$  goes as  $1/R_D$ , while the output resistance is limited by  $R_{out}$ , which is independent of  $R_D$  (note again that  $R_{out}$  refers to the output resistance neglecting  $R_D$ , so the total output resistance would be  $R_D \parallel R_{out}$ ). Thus, as  $R_D$  goes to infinity, its noise current goes to zero while the resistance it flows through approaches a finite value, meaning its noise contribution goes to zero.

(b) i.

$$\lim_{g_{m2} \rightarrow 0} NF = \boxed{\infty} \quad \text{SIS}$$

As we let  $g_{m2} \rightarrow 0$ , the noise figure goes to infinity. Intuitively, the noise current squared of  $M_2$  goes as  $g_{m2}$ , but the output resistance goes at  $1/g_{m2}$ . Since the noise contribution of  $M_2$  is obtained by multiplying the square of the noise current by the square of the output resistance, the noise contribution of  $M_2$  goes as  $1/g_{m2}$ . Thus, as  $g_{m2}$  goes to zero, the noise contribution of  $M_2$  goes to infinity, causing the noise figure to go to infinity.

ii.

$$\lim_{g_{m2} \rightarrow 0} NF = \boxed{1 + \frac{\gamma}{g_{m1} R_S} + \frac{(1 + g_{m1} R_S)^2}{g_{m1}^2 R_S R_D}} \quad \text{SIS}$$

As we let  $g_{m2} \rightarrow 0$ , the contribution to the noise figure from  $M_2$  goes to zero and the contributions from  $M_1$  and  $R_D$  decrease. Intuitively, the noise current from  $M_2$  flows through a finite input resistance, and since the noise current from  $M_2$  goes to zero as  $g_{m2} \rightarrow 0$ , the noise contribution from  $M_2$  goes to zero.

We also see that the output resistance will decrease to  $R_D$  as  $g_{m2} \rightarrow \infty$  (note that it actually is a decrease, not an increase, since  $R_{out} < 0$ , where again  $R_{out}$  is the output resistance neglecting  $R_D$ ). Since the noise currents of  $M_1$  and  $R_D$  flow through this output resistance, their noise contributions will decrease.

2. (a) Using  $\boxed{W_2 = 13.7 \mu\text{m}}$  causes the drain of  $M_1$  to resonate at 5.2 GHz. The AC response of the circuit is shown in Fig. 5.

(b) Let  $R_{out1}$  be the output resistance of the first stage at 5.2 GHz,  $R_{in1}$  be the resistance seen at the source of  $M_1$  at 5.2 GHz, and  $A_{v1}$  be the gain from the source of  $M_1$  to the drain of  $M_1$ .

$$V_{n,out}^2 = \overline{I_{RS}^2} R_{in1}^2 A_{v1}^2 + \overline{I_{RP}^2} R_{out1}^2 + \overline{I_{D1}^2} (R_{in1} A_v - R_{out1})^2$$

We can use SPICE to measure  $R_{in1}$ ,  $R_{out1}$ ,  $A_{v1}$ , and  $g_{m1}$ . We can estimate  $\gamma$  using SPICE as well by taking the noise measured from  $M_1$  and dividing it by  $4kTg_{m1}$ .

$$R_{in1} = 48.870 \Omega$$

$$R_{out1} = 2.5872 \text{ k}\Omega$$

$$A_{v1} = 27.5236$$

$$g_{m1} = 18.1324 \text{ mS}$$

$$\gamma = 0.81819$$

$$R_{P1} = 1.3069 \text{ k}\Omega$$

$$T = 298.15 \text{ K}$$

$$k = 1.38065 \times 10^{-13} \text{ J/K}$$

$$V_{n,out}^2 = 1.0570 \times 10^{-15} \text{ V}^2/\text{Hz}$$

$$NF = \frac{V_{n,out}^2}{A^2} \frac{1}{4kTR_S}$$

$$A = 27.708$$

$$NF = \boxed{1.67235} \quad \text{SIS}$$

Using SPICE to find the noise figure (by dividing the total output noise by the output noise contributed by the source resistance), we get  $NF = \boxed{1.78516}$ . The calculated and simulated values differ by about 6.75 %, which is relatively good agreement.

- (c) The noise figure of the overall amplifier is  $NF = 1.8087$ . The second stage increases the noise figure by only about 1.32 %. This makes sense intuitively because the gain of the first stage is relatively large ( $A = 27.708$ ). This reduces the contribution of the second stage to the noise figure, as can be seen from the Friis equation.

This is the SPICE netlist used for this problem:

```
* EE215C HW2 Problem 2

.inc '215a.sp'

.param W2=13.7u
.param PI=3.14159265358979323846
.param Q=5
.param FREQ=5.2e9
.param L1=8n
.param RP1='2*PI*L1*FREQ*Q'
.param L2=6n
.param RP2='2*PI*L2*FREQ*Q'

vdd vdd gnd 1.8V
vin vin gnd AC 1
rs vin 1 50
c1 1 vs1 1u
i1 vs1 gnd 2.5m
m1 vd1 vdd vs1 gnd CMOSN W=50u L=0.18u
+PS='2*5e-5+1.2e-6' PD='2*5e-5+1.2e-6' AS='5e-5*0.6e-6' AD='5e-5*0.6e-6'
l1 vdd vd1 L1
rp1 vdd vd1 RP1

m2 vout vd1 vs2 gnd CMOSN W=W2 L=0.18u
+PS='2*W2+1.2e-6' PD='2*W2+1.2e-6' AS='W2*0.6e-6' AD='W2*0.6e-6'
i2 vs2 gnd 2m
c2 vs2 gnd 750f
c3 vout gnd 60f
l2 vdd vout L2
rp2 vdd vout RP2

* Used for finding the resonance frequency.
.ac lin 1000 5G 5.4G

* Used for finding the noise figure.
** .noise v(vout) vin 1
.option post nomod accurate
.end
```

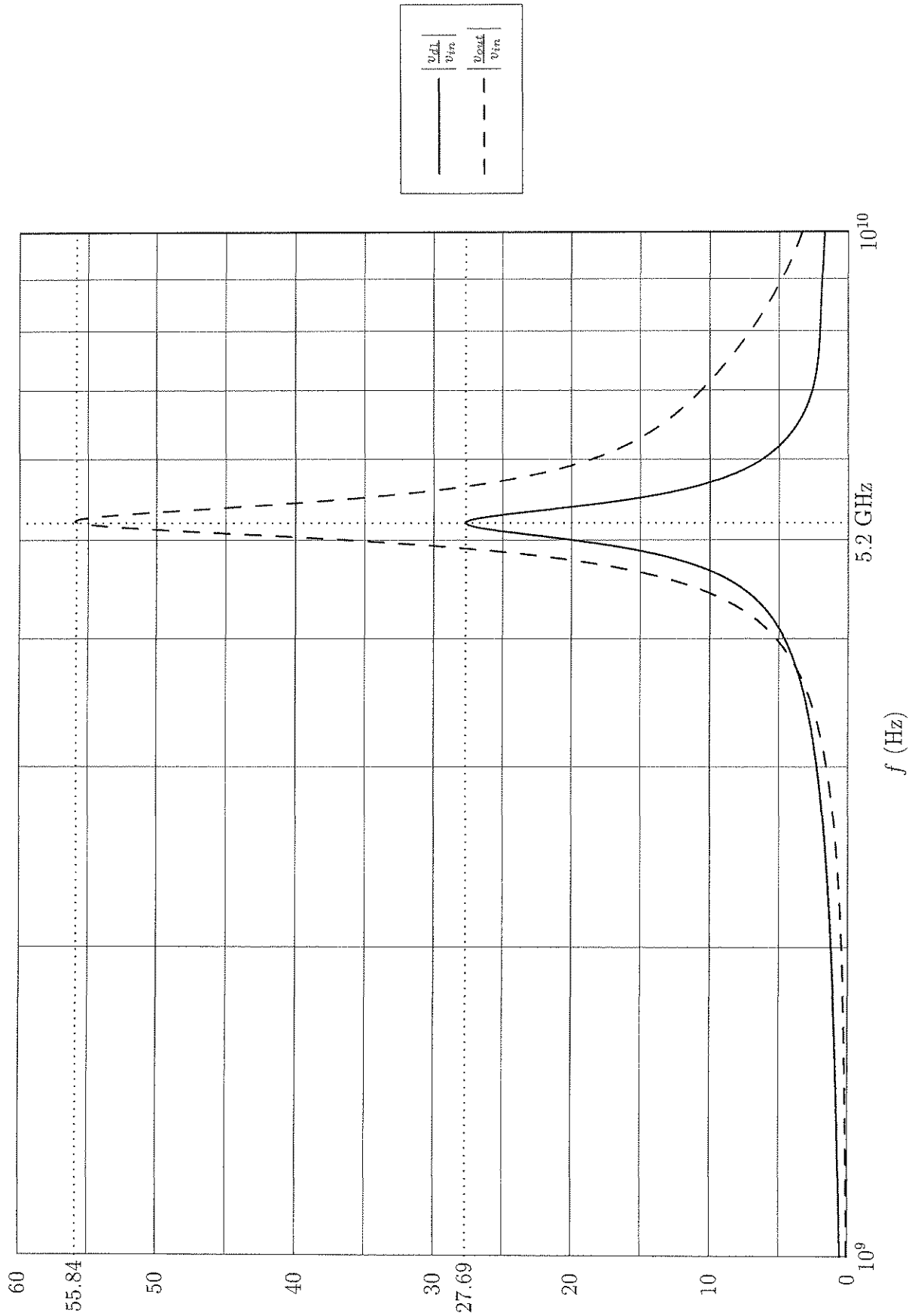


Figure 5: AC response of the LNA

