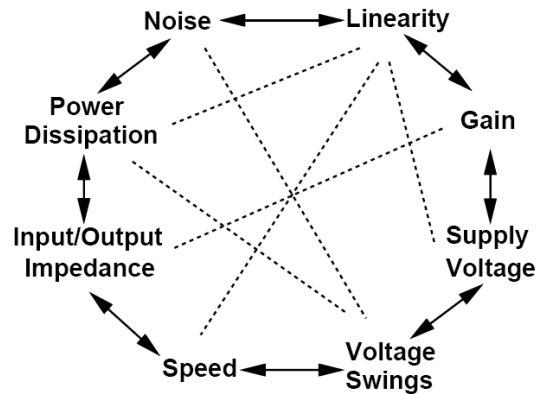


Single-Stage Amplifiers

Many aspects of the performance of amplifiers are critical. We summarize the trade-offs as shown below.





The amplifiers to be studied here include: CS and CG stages, source followers, and cascades. For each stage, we wish to study both the large-signal and small-signal properties.

Amplifier Categories

Common-Source Stage	Source Follower	Common-Gate Stage	Cascode
With Resistive Load	With Resistive Bias	With Resistive Load	Telescopic
With Diode-Connected Load	With Current-Source Bias	With Current-Source Load	Folded
With Current-Source Load			
With Active Load			
With Source Degeneration			

Common Source Stage

- Large-Signal Behavior

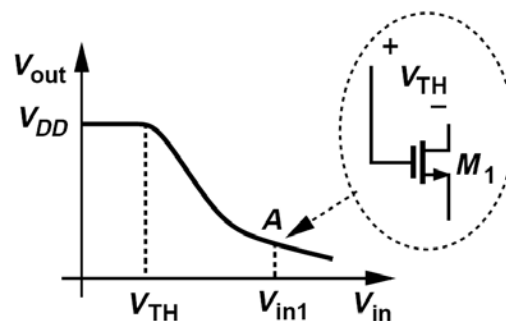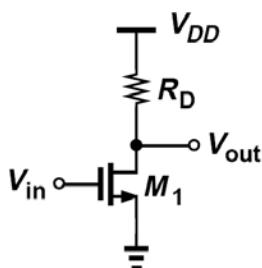


What is the small-signal gain in this region?

At point A: $V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$.

How do we maximize the gain?


- Small-Signal Analysis

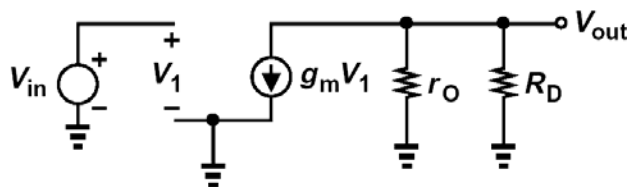We assume that the bias currents and voltages are chosen such that M_1 is in saturation and Q_1 in forward active region.




Voltage Gain:

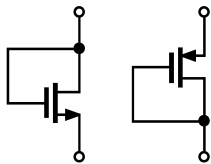
Sometimes we don't want to use a resistive load. So we try other tricks:



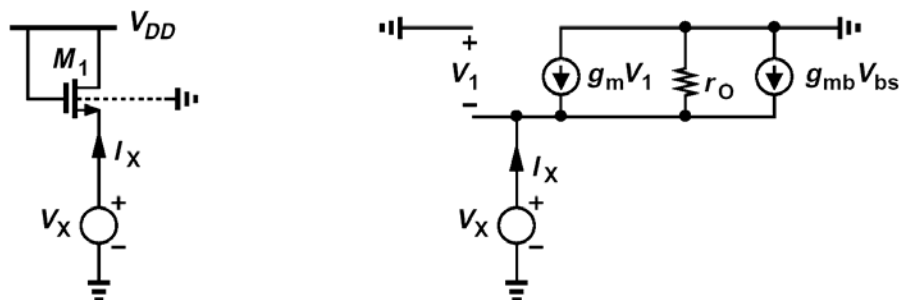This device can operate as a resistor. How about this:




Common Source with "Diode" Load

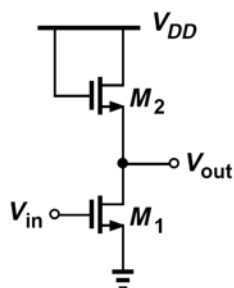


How do we maximize the voltage gain here?

Large Signal Behavior:

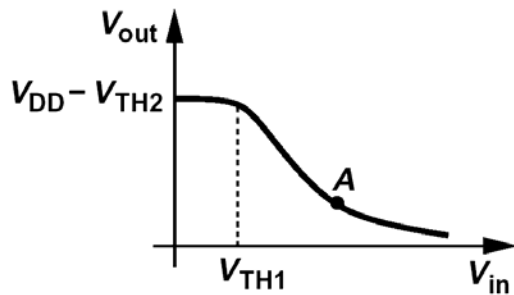


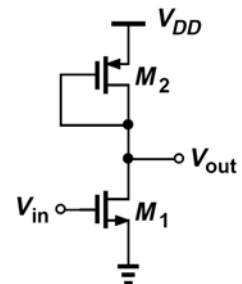Example: Common Source with PMOS Diode Load




Both versions suffer from serious headroom limitations at low supply voltages.

CS Stage with Current Source Load

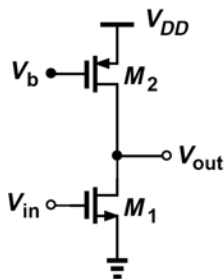


What happens to the gain as I_D decreases?


CS Stage with Active Load

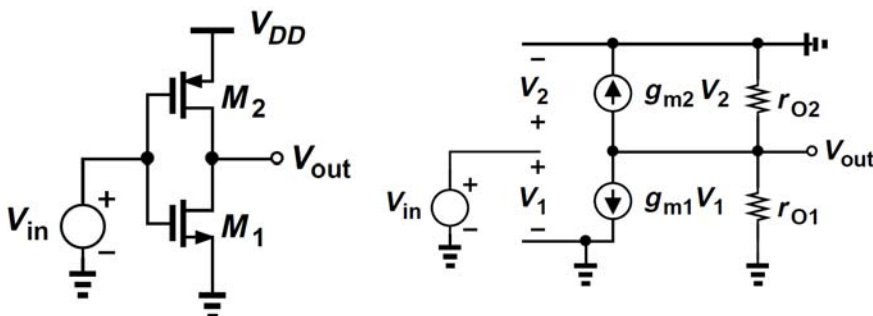


CS Stage with Source Degeneration

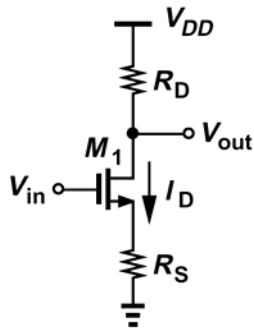

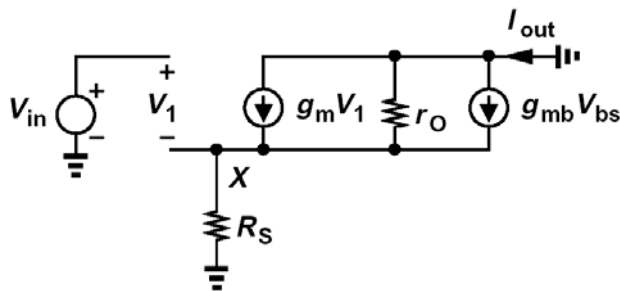It is useful to find the Gm of the stage:




Also, the output impedance:

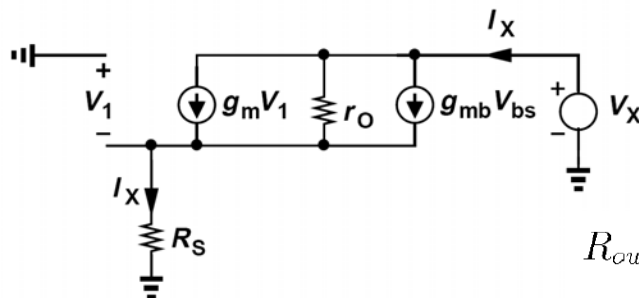



$$\begin{aligned} R_{out} &= [1 + (g_m + g_{mb})R_S]r_O + R_S \\ &= [1 + (g_m + g_{mb})r_O]R_S + r_O. \end{aligned}$$

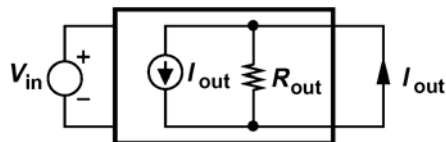Now let's compute the gain by noting that:




$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb})R_S r_O}$$

If $\lambda=0$ and $g_{mb}=0$, then:

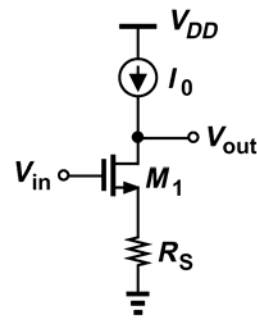
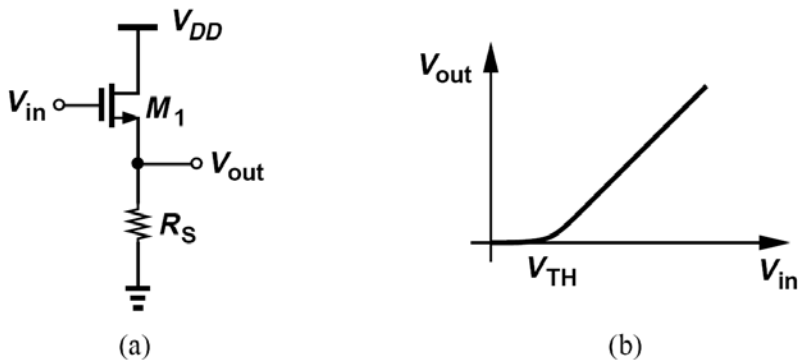
Example**Source Followers****- Large-Signal Behavior**

Sketch the gain vs. input.

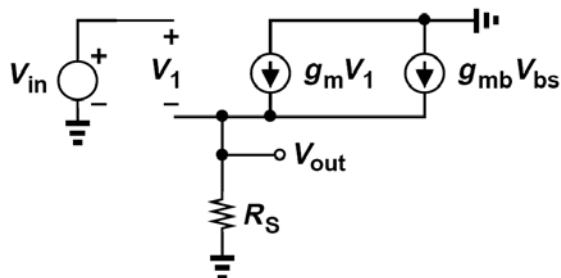- Small-Signal Behavior



$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

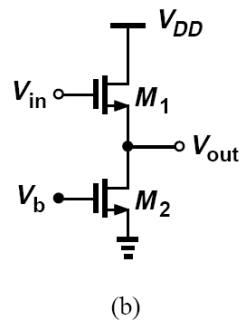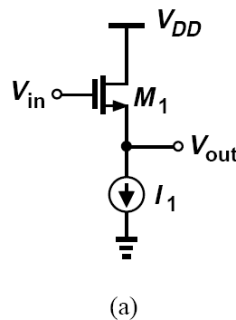- Often use a current source in place R_S to have a better definition of the bias current.




How good a buffer is a source follower? Input impedance =



Output Impedance:

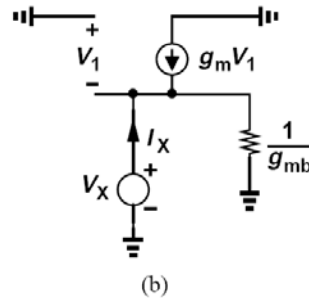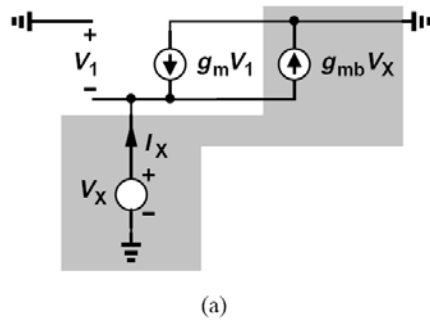


Another method of finding the gain:

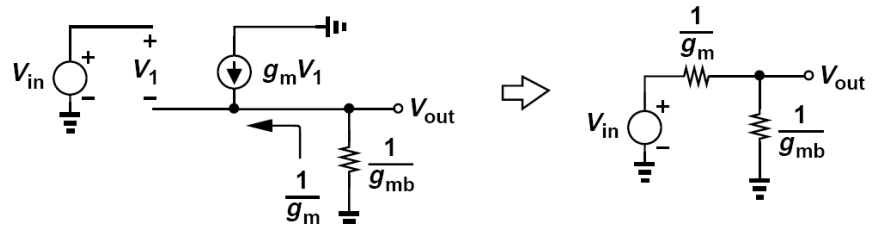

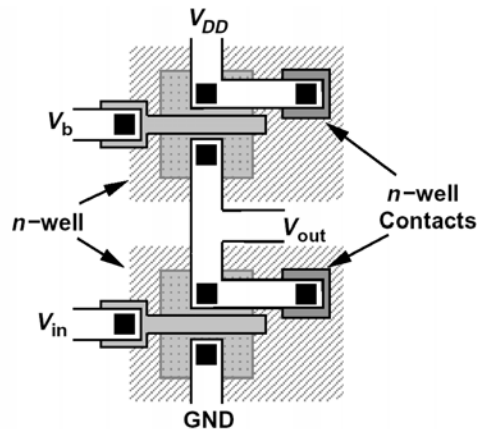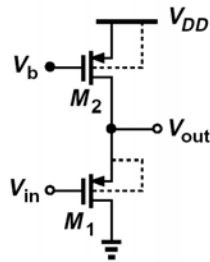- Can eliminate body effect in PMOS version:





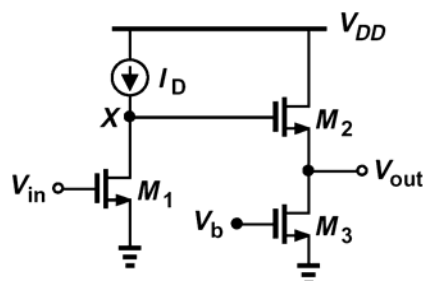- Source followers are used only occasionally. They introduce noise and consume voltage headroom. For example:





Common-Gate Stage

- Large-Signal Behavior

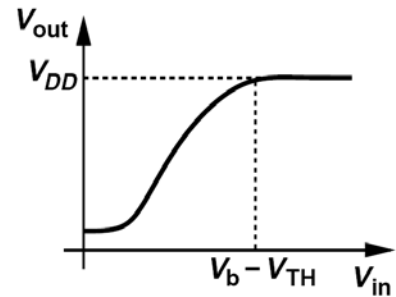
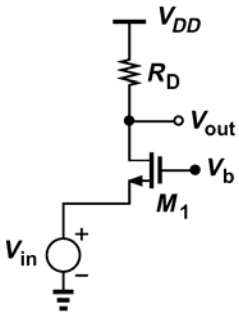


- Small-Signal Behavior

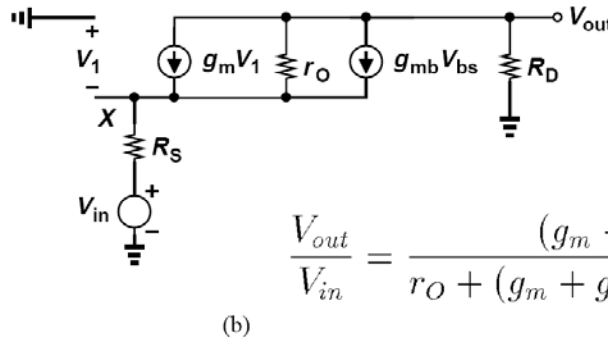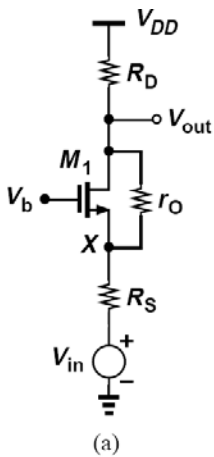




$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D.$$

• Input Impedance

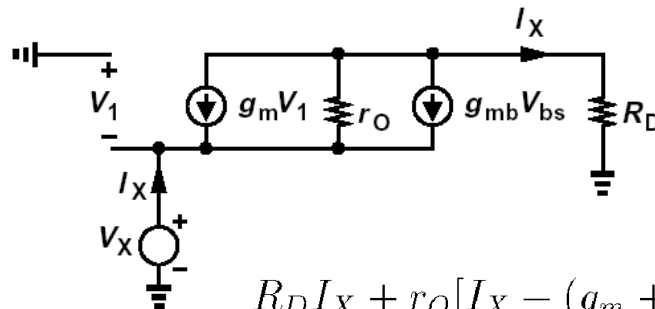
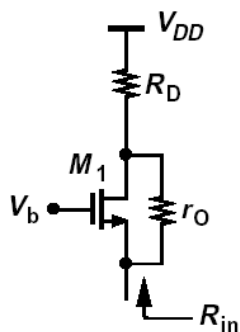


$$R_D I_X + r_O [I_X - (g_m + g_{mb}) V_X] = V_X.$$

$$\begin{aligned} \frac{V_X}{I_X} &= \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O} \\ &\approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{g_m + g_{mb}} \end{aligned}$$

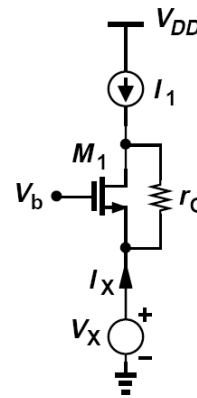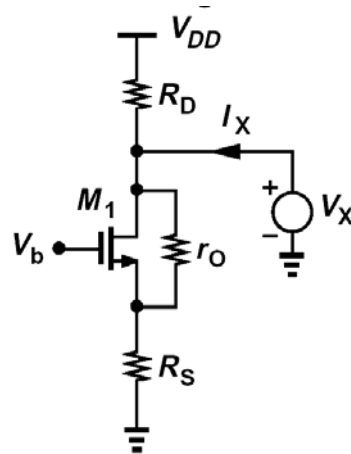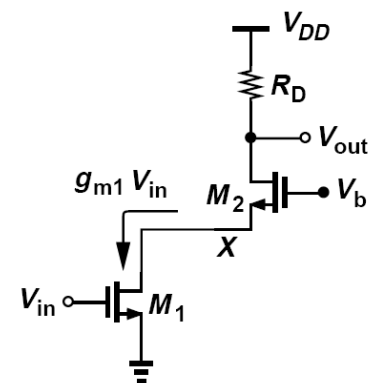
Example**• Output Impedance****Cascode Stage**

How do we choose the bias conditions?

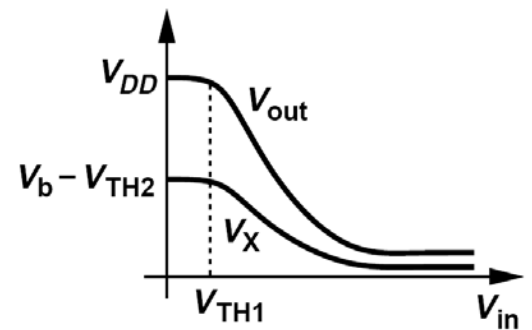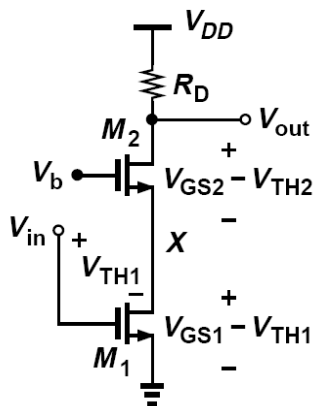


What is the maximum output voltage swing?

Gain Calculation:

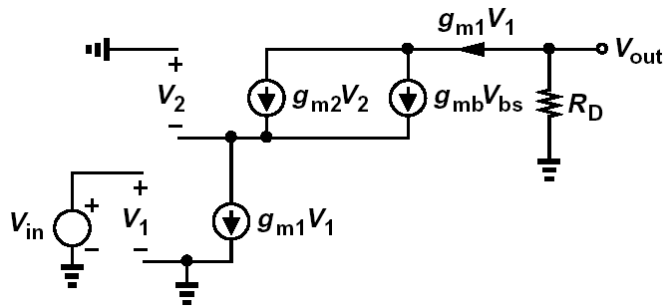


Output Impedance:

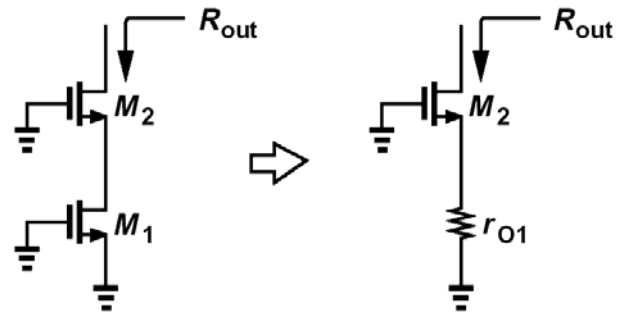

Cascode Stage with Current Source Load

Bias currents and voltages are chosen such that all MOSFETs are in saturation.

Voltage Gain:

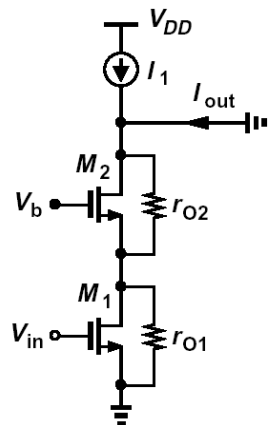


$$I_{out} = g_{m1} V_{in} \frac{r_{O1}}{r_{O1} + \frac{1}{g_{m2} + g_{mb2}} || r_{O2}}$$


$$G_m = \frac{g_{m1} r_{O1} [r_{O2} (g_{m2} + g_{mb2}) + 1]}{r_{O1} r_{O2} (g_{m2} + g_{mb2}) + r_{O1} + r_{O2}}$$

$$|A_v| = G_m R_{out}$$
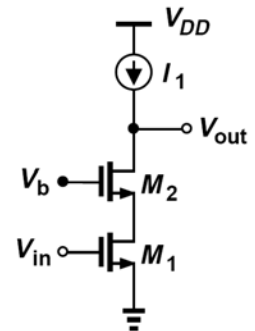
$$= g_{m1} r_{O1} [(g_{m2} + g_{mb2}) r_{O2} + 1]$$



How do we maximize the voltage gain?

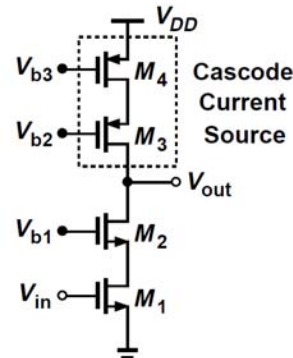
Actual realization:**Gain calculation:**

$$R_{out} = \{[1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2}\} \parallel \{[1 + (g_{m3} + g_{mb3})r_{O3}]r_{O4} + r_{O3}\}$$


$$A_v \approx g_{m1} [(g_{m2}r_{O2}r_{O1}) \parallel (g_{m3}r_{O3}r_{O4})]$$

Folded Cascode

The input and cascode devices need not be of the same type.

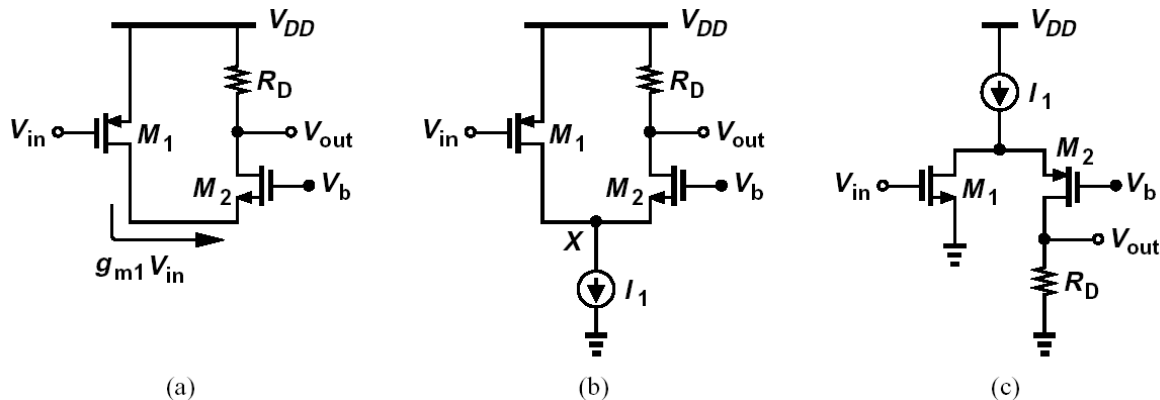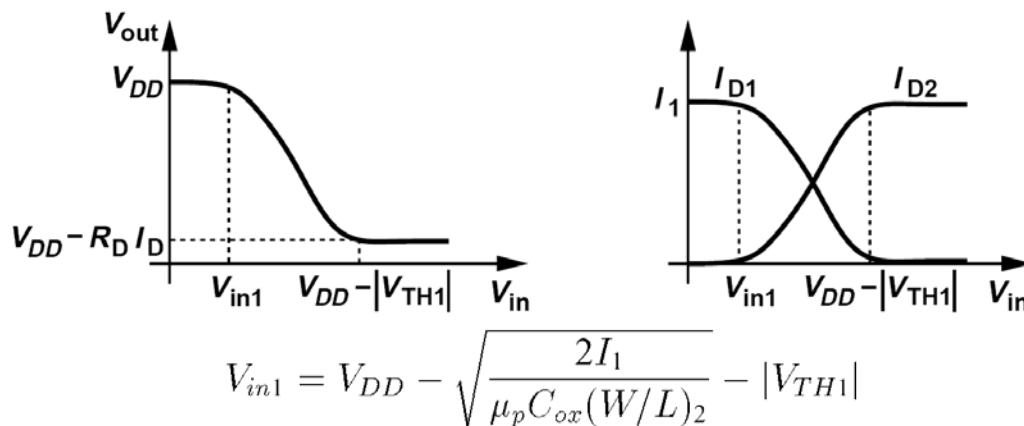
**- Large-Signal Behavior**

Let the input decrease from V_{DD} to zero.



- **Small-Signal Behavior**
Similar to that of simple cascode.



Example

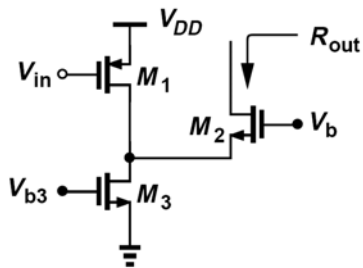


Other Applications of Cascodes

1. Reduction of Miller Effect

2. Shielding

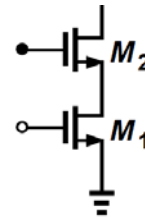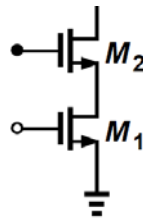

3. Stability

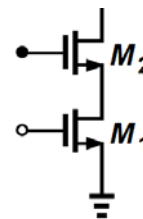

4. Reduction of Device Stress

