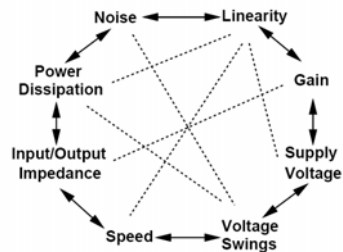


## Single-Stage Amplifiers

Many aspects of the performance of amplifiers are critical. We summarize the trade-offs as shown below.





The amplifiers to be studied here include: CS and CG stages, source followers, and cascodes. For each stage, we wish to study both the large-signal and small-signal properties.

### Amplifier Categories

Common-Source Stage	Source Follower	Common-Gate Stage	Cascode
With Resistive Load With Diode-Connected Load With Current-Source Load With Active Load With Source Degeneration	With Resistive Bias With Current-Source Bias	With Resistive Load With Current-Source Load	Telescopic Folded

### Common Source Stage

#### - Large-Signal Behavior

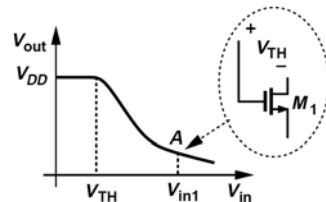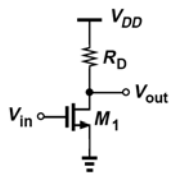


What is the small-signal gain in this region?

At point A:  $V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$

How do we maximize the gain?

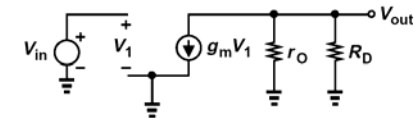
#### - Small-Signal Analysis

We assume that the bias currents and voltages are chosen such that  $M_1$  is in saturation and  $Q_1$  in forward active region.




Voltage Gain:

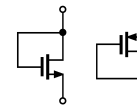
Sometimes we don't want to use a resistive load. So we try other tricks:



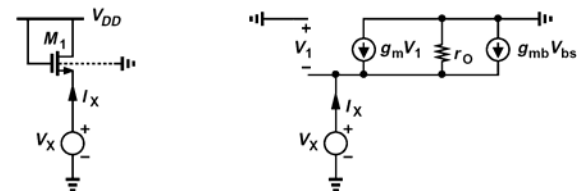This device can operate as a resistor. How about this:




### Common Source with "Diode" Load

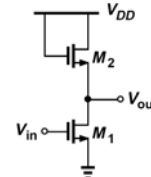


How do we maximize the voltage gain here?

Large Signal Behavior:

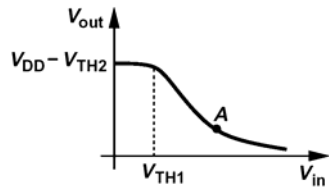


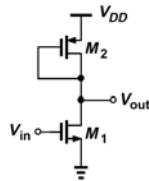Example: Common Source with PMOS Diode Load




Both versions suffer from serious headroom limitations at low supply voltages.

CS Stage with Current Source Load

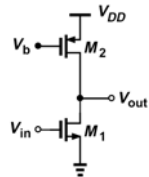


What happens to the gain as  $I_D$  decreases?


CS Stage with Active Load

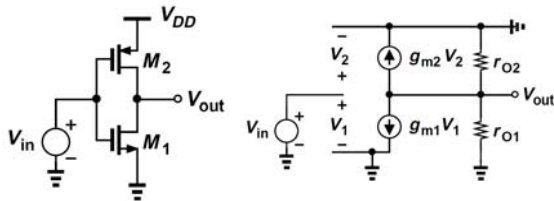


CS Stage with Source Degeneration

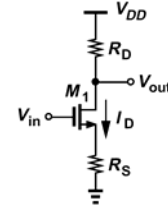

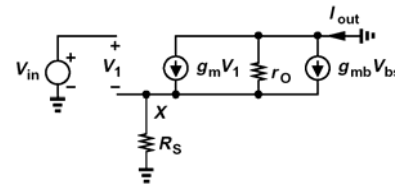It is useful to find the  $G_m$  of the stage:




Also, the output impedance:

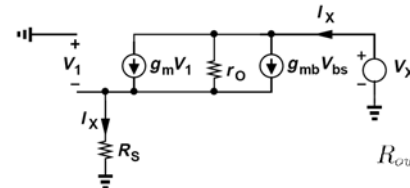

$$R_{out} = [1 + (g_m + g_{mb})R_S]r_O + R_S$$

$$= [1 + (g_m + g_{mb})r_O]R_S + r_O$$

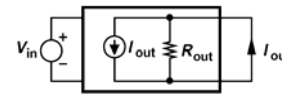
Now let's compute the gain by noting that:



$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb})R_S r_O}$$


If  $\lambda=0$  and  $g_{mb}=0$ , then:

### Example

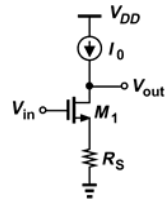


### Source Followers

#### - Large-Signal Behavior

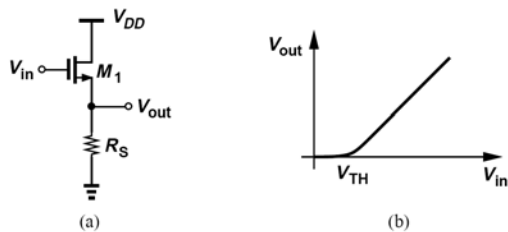


Sketch the gain vs. input.

#### - Small-Signal Behavior

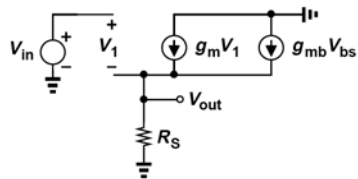


$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

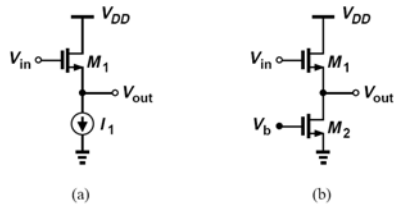- Often use a current source in place  $R_S$  to have a better definition of the bias current.




How good a buffer is a source follower? Input impedance =


Output Impedance:

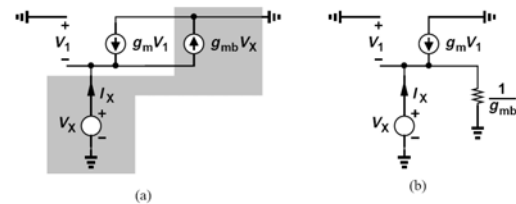


Another method of finding the gain:

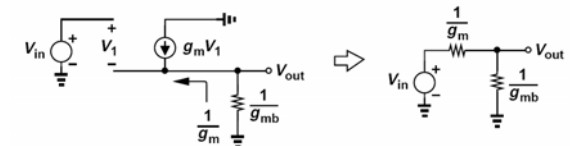

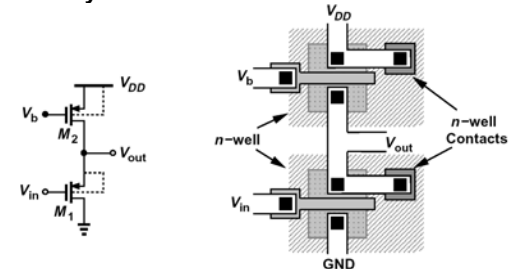- Can eliminate body effect in PMOS version:





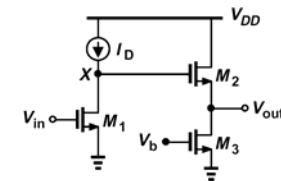- Source followers are used only occasionally. They introduce noise and consume voltage headroom. For example:





### Common-Gate Stage

#### - Large-Signal Behavior

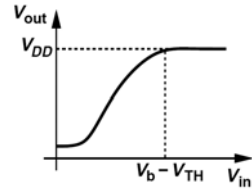
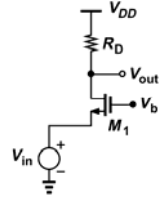


#### - Small-Signal Behavior

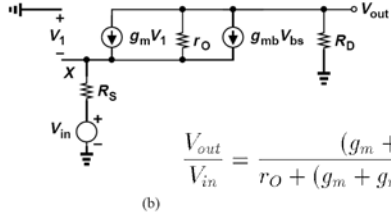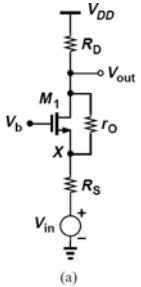

$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D$$

#### • Input Impedance

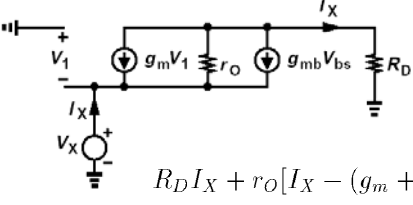
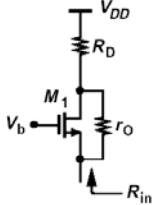


$$R_D I_X + r_O [I_X - (g_m + g_{mb}) V_X] = V_X$$

$$\frac{V_X}{I_X} = \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O} \approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{g_m + g_{mb}}$$




### Example

#### • Output Impedance

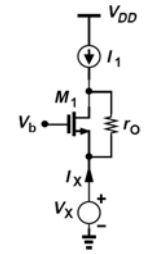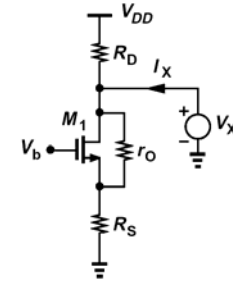


### Cascode Stage

How do we choose the bias conditions?

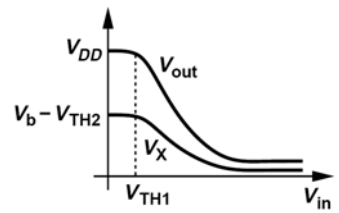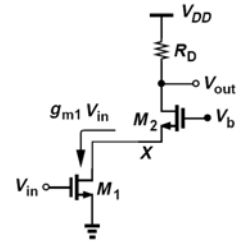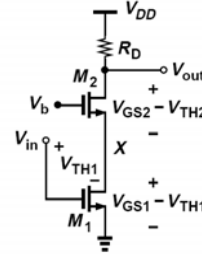


What is the maximum output voltage swing?

Gain Calculation:

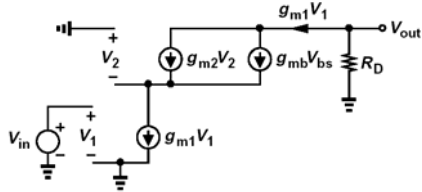


Output Impedance:

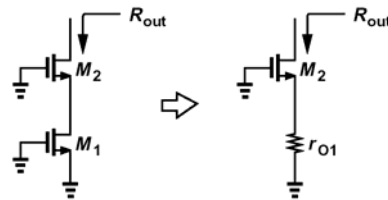

### Cascode Stage with Current Source Load


Bias currents and voltages are chosen such that all MOSFETs are in saturation.

Voltage Gain:

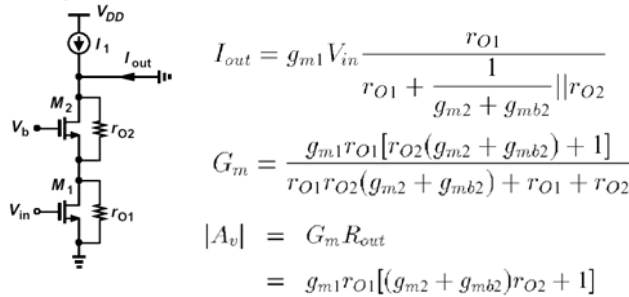

How do we maximize the voltage gain?

Actual realization:

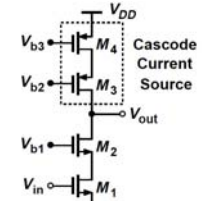


Gain calculation:

$$R_{out} = \{ [1 + (g_{m2} + g_{mb2}) r_{O2}] r_{O1} + r_{O2} \} || \{ [1 + (g_{m3} + g_{mb3}) r_{O3}] r_{O4} + r_{O3} \}$$

$$A_v \approx g_{m1} [(g_{m2} r_{O2} r_{O1}) || (g_{m3} r_{O3} r_{O4})]$$

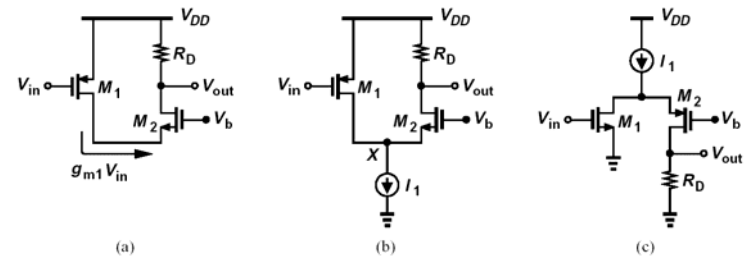
### Folded Cascode

The input and cascode devices need not be of the same type.




- Large-Signal Behavior

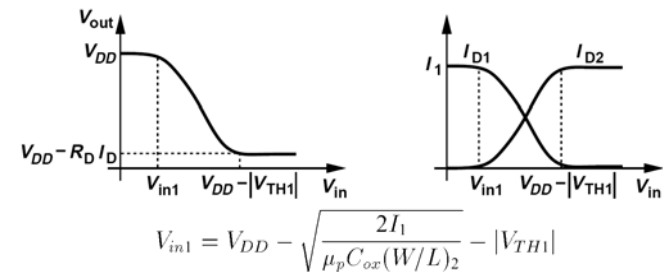Let the input decrease from  $V_{DD}$  to zero.




- **Small-Signal Behavior**  
Similar to that of simple cascode.

Example

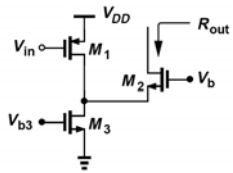


Other Applications of Cascodes


1. Reduction of Miller Effect

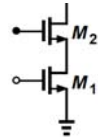

2. Shielding

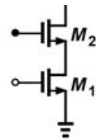

3. Stability

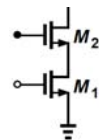

4. Reduction of Device Stress

