 


## Differential Amplifiers

- Differential & Single-Ended Operation


- A single-ended signal is taken with respect to a fixed potential (usually ground).

- A differential signal is taken between two nodes that have equal and opposite signals with respect to a "common mode" voltage and also equal impedances to a fixed potential (usually ground).




- Why Differential?

 
- Rejection of common-mode disturbance: supply noise, etc.



 - Rejection of coupling & feed through from other sources:




 - Reduction of coupling to other circuits;




- Maximum voltage swing almost twice that in single-ended operation;
- Even-order distortion suppressed (discussed later);
- Biasing is easier.

### Basic Differential Pair

 


 - Quantitative Analysis  
Differential Behavior:



Where does the maximum small-signal gain occur?


**Common-Mode Behavior:**

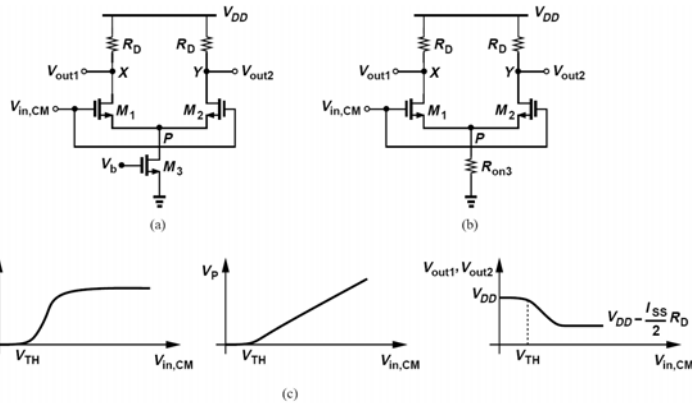


**Observations:**

- The small-signal gain drops as the difference between  $V_{in1}$  and  $V_{in2}$  increases.
- The input and output common-mode levels must be chosen carefully. The current source requires some voltage so as to exhibit a high output impedance.


How large can the output swings be?

 

**Large-Signal Analysis**

 
 
$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{W} - (V_{in1} - V_{in2})^2}$$



Note: If neglect sub-threshold behavior, for some  $V_{in1} - V_{in2}$  one transistor completely turns off. This occurs for a differential input of :

$$\Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This can be related to the overdrive at equilibrium:


- To achieve a wider linear range for  $V_{in1} - V_{in2}$ , need greater (equilibrium) overdrive. For a given bias current, this translates to lower transconductance for each device.
- How does the input-output characteristic change as  $W$  changes?

**Small-Signal Analysis**

If the circuit is perfectly symmetric and  $V_{in1}$  and  $V_{in2}$  change by equal and opposite amounts from equilibrium, then we can use the concept of "half circuit."

 **Lemma**


In the following symmetric circuit, if  $V_{in1}$  changes from  $V_0$  to  $V_0 + \Delta V$  and  $V_{in2}$  changes from  $V_0$  to  $V_0 - \Delta V$ , then  $V_x$  does not change.




$$g_m \Delta V_1 + g_m \Delta V_2 = 0$$

$$V_0 + \Delta V_{in} - (V_a + \Delta V_1) = V_0 - \Delta V_{in} - (V_a + \Delta V_2)$$

 
From another point of view, one transistor wants to pull  $V_x$  up while the other wants to pull it down.



=>  $V_x$  can be grounded.

 


**Other Types of Loads**

 


Calculate the voltage headroom requirement and small-signal gain.

How do we increase the gain of diff pair with current source loads?

**Common-Mode Response**  
**Case I : Symmetric Circuit**

 

**Case II: Asymmetric Circuit**

 


Effect of load resistance mismatch:

$$\Delta V_X = \Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$


$$\Delta V_Y = \Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$
 
## Current Mirrors & Active Loads

In analog design (and sometimes digital design), we may need to generate many well-defined bias currents. For example:




Each current source can be realized as:

 


If we apply a self-defined voltage to the gate or the base, the current is NOT well-defined. In MOSFETs,  $V_{TH}$  can vary by tens of millivolts from wafer to wafer, causing significant error.


Better approach:

 

 
So, all we need to generate is one reference current.  $I_{REF}$  is established by precision bandgap techniques or sometimes provides externally.



Example:

 


### The Gate Corner Problem

 


### Cascode Current Mirrors

Channel-length modulation causes error if the voltage across the diode-connected device is not equal to  $V_{DS}$  of current sources.

 


**Solution 1: Standard Cascode**

 


- What is the minimum allowable voltage across the current source?


Example:

 

**Solution 2: Low-Voltage Cascode**

 


**How to generate Vb?**

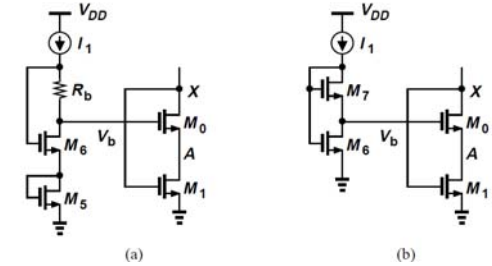

 
**Active Current Mirrors**

Diff Pair with Passive Load: Suppose we need a high-gain differential amplifier with single-ended output:





What is the voltage gain?


Diff Pair with Active Load:

 


**Large-Signal Behavior:**

  


**Small-Signal Behavior:**

 

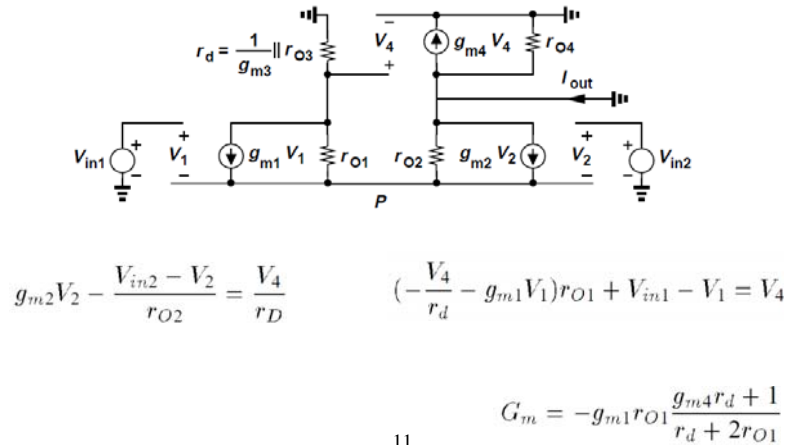**Calculate the gain as -GmRout. First, Gm:**



**Second, Rout:**

 

$$I_X = \frac{V_X}{2r_{O1,2} + \frac{1}{g_{m3}} \parallel r_{O3}} \left[ 1 + \left( \frac{1}{g_{m3}} \parallel r_{O3} \right) g_{m4} \right] + \frac{V_X}{r_{O4}}$$


$$\frac{I_X}{V_X} = \frac{1 + g_{m4}r_d}{2r_{O1} + r_d} + \frac{1}{r_{O4}} \quad |A_v| = g_{m1}(r_{O1} \parallel r_{O4}) \frac{2g_{m4}r_{O4} + 1}{2(g_{m4}r_{O4} + 1)}$$

$$= \frac{(1 + g_{m4}r_d)r_{O4} + 2r_{O1} + r_d}{(2r_{O1} + r_d)r_{O4}}$$


What is the dc output voltage in equilibrium?

How do we increase the voltage gain?



**Common-Mode Rejection**

 

What is the common-mode gain?

 

  Thus, even if the circuit is perfectly symmetric, CMRR is not infinite. In practice, random mismatches between the two sides result in a finite CMRR.



$$\Delta V_P = \Delta V_{in,CM} \frac{R_{SS}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}}$$

$$\begin{aligned} \Delta I_{D1} &= g_{m1}(\Delta V_{in,CM} - \Delta V_P) \\ &= \frac{\Delta V_{in,CM}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}} \frac{g_{m1}}{g_{m1} + g_{m2}} \\ \Delta I_{D2} &= g_{m2}(\Delta V_{in,CM} - \Delta V_P) \\ &= \frac{\Delta V_{in,CM}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}} \frac{g_{m2}}{g_{m1} + g_{m2}} \end{aligned}$$