

EE215A

Final Exam

Fall 2010

Name:.....*Solutions*.....

Time Limit: 3 Hours

Open Book, Open Notes

Each problem has 20 points.

All transistors are in saturation.


1. 20

2. 20

3. 20

4. 20

5. 20

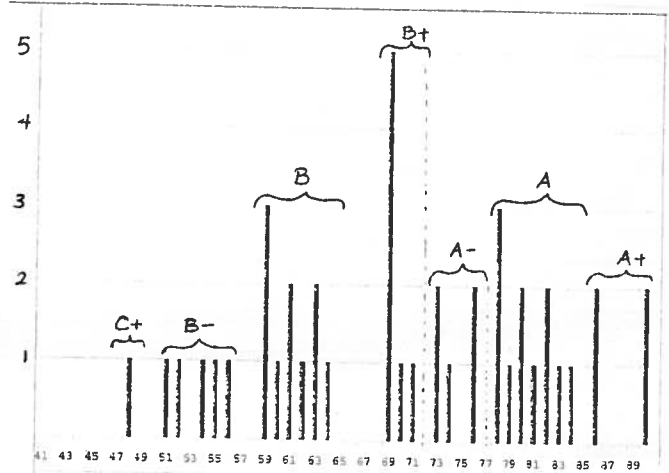


1. A transimpedance amplifier is shown below. Assume I_1 , I_2 , and I_3 are ideal. Also, $\lambda \neq 0$. Use feedback techniques in parts (a) and (b).

(a) Determine the open-loop transimpedance gain and input and output impedances.


(b) Determine the closed-loop transimpedance gain and input and output impedances. Simplify the expressions for $\lambda \rightarrow 0$.

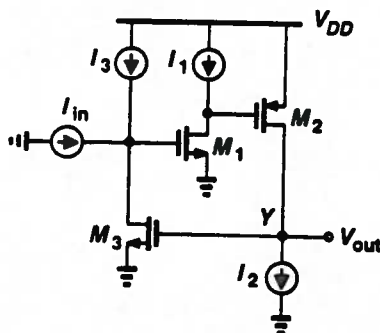(c) Assuming $\lambda = 0$, compute the input-referred thermal noise current of the closed-loop circuit.



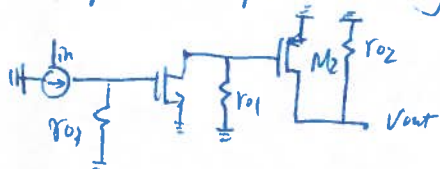(a) V-C Feedback: use Y model: $Y_{21} = g_{m3} = \beta$, $Y_{22} = 1/r_{o3}$, $Y_{11} = 0$

Open the loop with loading: (small signal)



$\Rightarrow$

$$\begin{aligned} R_{o,open} &= g_{m1} g_{m2} r_{o1} r_{o2} r_{o3} \\ R_{in,open} &= r_{o3} \\ R_{out,open} &= r_{o2} \end{aligned}$$

(b) close-loop: $R_{o,close} = R_{o,open} / (1 + R_{o,open} g_{m3})$

$$R_{o,close} = \frac{g_{m1} g_{m2} r_{o1} r_{o2} r_{o3}}{(1 + g_{m1} g_{m2} g_{m3} r_{o1} r_{o2} r_{o3})}$$


$$R_{in,close} = \frac{r_{o3}}{[1 + g_{m1} g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}]}$$

$$R_{out,close} = \frac{r_{o2}}{[1 + g_{m1} g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}]}$$

for $\lambda \rightarrow 0$,

$$\begin{aligned} R_{o,close} &= 1/g_{m3} \\ R_{in,close} &= 0 \\ R_{out,close} &= 0 \end{aligned}$$

(c) $\lambda = 0 \Rightarrow$

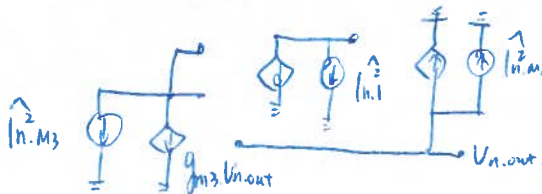

$$g_{m3} V_{in,out} = I_{n,M3}$$

$$V_{in,out}^2 = \frac{I_{n,M3}^2}{g_{m3}^2} = I_{n,M3}^2 \left(\frac{1}{g_{m3}} \right)^2$$

$R_{o,close} = 1/g_{m3}$


$$\hat{I}_{n,M1}^2 = \hat{I}_{n,M3}^2$$

2. It is possible to use the bulk terminal of PMOS devices as an input. Consider the amplifier shown below. Assume $\lambda \neq 0$ for all devices, $\gamma \neq 0$ for M_1 and M_2 , and $\gamma = 0$ for other transistors. Also, assume the input common-mode level is equal to V_{DD} .

(a) Calculate the voltage gain.

(b) Calculate the input-referred thermal noise voltage of the amplifier. To avoid confusion, use Γ (rather than γ) for the thermal noise coefficient of MOSFETs, e.g., $\overline{I_n^2} = 4kT\Gamma g_m$.

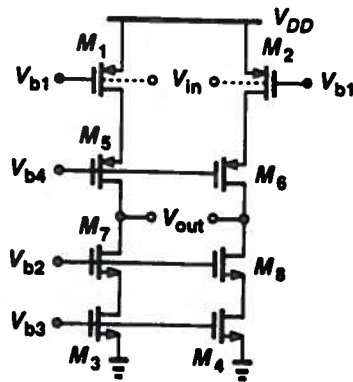(c) If the input common-mode level is raised to $V_{DD} + 0.5$ V, does the small-signal gain increase or decrease? Why?




(a) Fully symmetric $\Rightarrow$ use half circuit.

$$G_m = g_{mb1}$$

$$R_{out} \approx (g_{m5} r_{o5} r_{o1}) \parallel (g_{m7} r_{o7} r_{o3})$$

$$|Gain| = |g_{mb1} (g_{m5} r_{o5} r_{o1} \parallel g_{m7} r_{o7} r_{o3})|$$

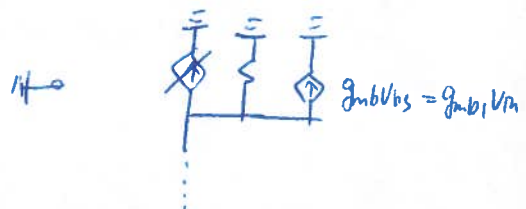

(b) Calculate half circuit first:

the noise contribution of M_5 & M_7

are negligible $\Rightarrow$ calculate only M_1 & M_3 :

$$\text{for } M_1: \hat{V}_{n,M1}^2 = 4kT\Gamma/g_{m1}$$

$$\text{Gain for } V_{n,M1} \text{ to output} \approx -g_{m1} R_{out}$$


$$\hat{V}_{n,out,M1}^2 = 4kT\Gamma g_{m1} R_{out}^2$$

$$\text{for } M_3: \hat{V}_{n,M3}^2 = 4kT\Gamma/g_{m3}$$

$$\text{Gain for } V_{n,M3} \text{ to output} \approx -g_{m3} R_{out}$$

$$\hat{V}_{n,out,M3}^2 = 4kT\Gamma g_{m3} R_{out}^2$$
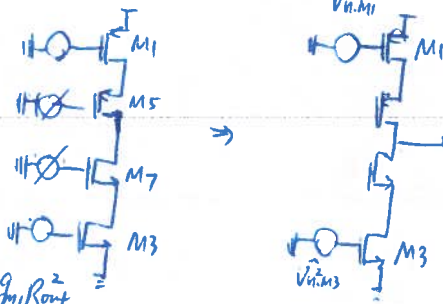
$$\hat{V}_{n,M,total}^2 = 2 \cdot 4 \cdot kT \cdot \Gamma \cdot (g_{m1} + g_{m3}) / g_{mb1}^2$$




$$(c) g_{mb} = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH}) \left(\frac{\gamma}{2}\right) / \sqrt{|2\phi_F + V_{SB}|}$$

$$|V_{TH}| \uparrow, |2\phi_F + V_{SB}| \uparrow, g_{mb} \downarrow \Rightarrow |Gain| \text{ decrease.}$$

(actually $R_{out} = g_{m5} r_{o5} r_{o1} \parallel g_{m7} r_{o7} r_{o3}$ changes slightly. $r_{o1} = \frac{1}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 \lambda}$ increase and all the other terms remain the same, R_{out} will increase only slightly.)

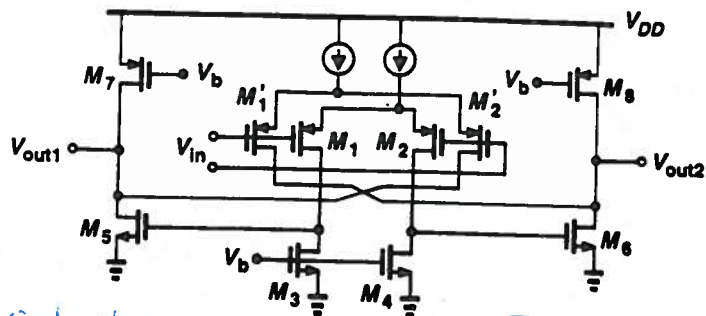3. The op amp shown below employs a fast path in parallel with a slow path. Assume $\lambda \neq 0$.
- Identify the fast and slow paths and determine the number of poles in each path.
 - Calculate the total small-signal differential gain of the op amp.
 - Which transistors typically limit the output voltage swing?






(a) fast path: $M1' M2'$, single stage

$\Rightarrow$ single pole

slow path: $M1, M2$, two stages

$\Rightarrow$ two poles.

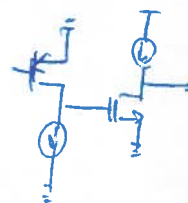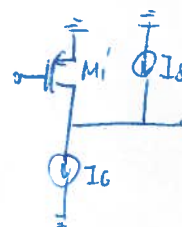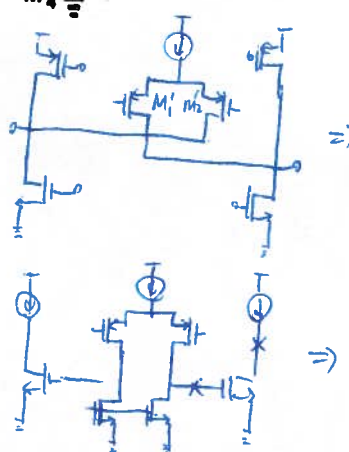

(b)

Using superposition:


$$V_{o1} = -V_{in} g_{m1} (R_{o1} \parallel R_{o3} \parallel r_{o1}')$$

$$V_{o2} = -V_{in} g_{m1} (R_{o1} \parallel R_{o3}) g_{m5} (R_{o5} \parallel R_{o7} \parallel r_{o1}')$$

$$V_o = V_{o1} + V_{o2} \Rightarrow \boxed{\text{Gain} = -[g_{m1}' + g_{m1} (R_{o1} \parallel R_{o3}) g_{m5}] (R_{o1}' \parallel R_{o5} \parallel R_{o7})}$$

(c)

$M1'$ & $M2'$

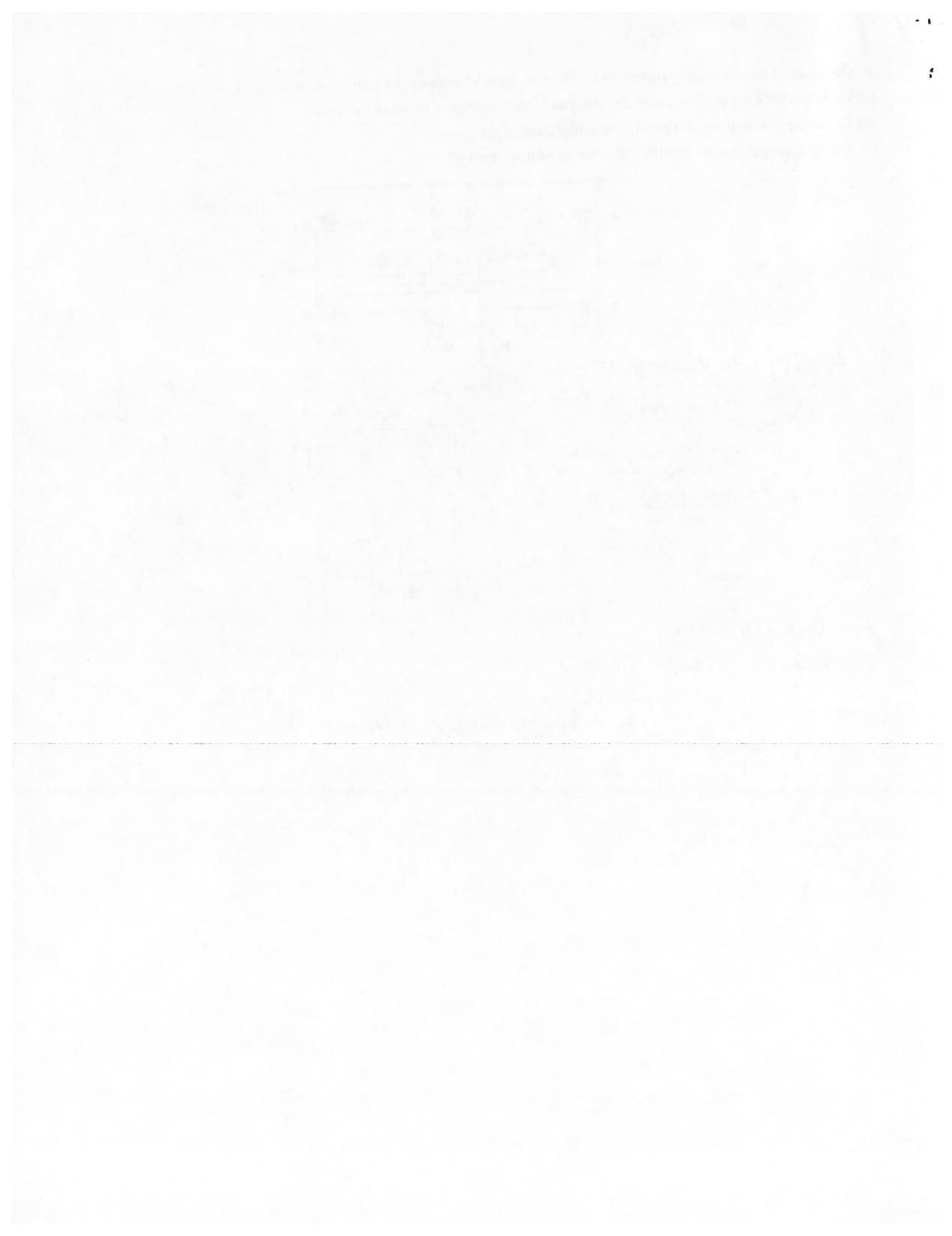


4. Consider the three-stage amplifier shown below. Assume all stages are identical and neglect all other capacitances. Also, $\lambda \neq 0$.

(a) Using Bode approximations, plot the magnitude and phase of the circuit's transfer function and identify important points. Explain why the amplifier is not stable if used in a unity-gain feedback loop.

(b) Compensate the amplifier (for unity-gain feedback) by adding a large capacitor, C_C , from node Y to ground. Determine the required value of C_C for a phase margin of 45° . You may assume $C_C \gg C_P$. Estimate the -3-dB bandwidth and unity-gain bandwidth of the amplifier after compensation.

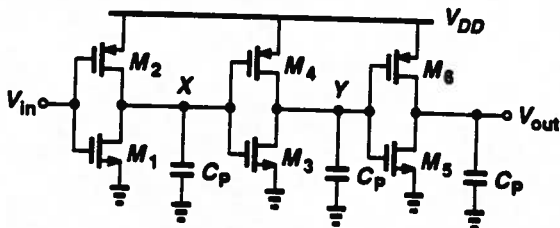(c) Compensate the amplifier (for unity-gain feedback) by adding a large capacitor, C_C , from node Y to node X. Determine the required value of C_C for a phase margin of 45° . You may assume $C_C \gg C_P$. Estimate the -3-dB bandwidth and unity-gain bandwidth of the amplifier after compensation.




$$(a) \omega_p = 1/C_P (r_{on} || r_{op})$$

$$A = A_0^3 / (1 + s/\omega_p)^3, \quad \beta > 1, \quad \text{where } |A_0| = |(g_{mn} + g_{mp}) \cdot (r_{on} || r_{op})|$$

Triple pole $\Rightarrow$ each stage has an identical pole. Suppose $A_0 \approx 10$, the unity gain BW will be one decade away from this pole, and the unity gain phase will be far below $-180^\circ \xrightarrow{A_0^3}$ Unstable!

$$(b) A = \frac{A_0^3}{[(1 + s/\omega_p)^2 (1 + s/\omega_{pY})]}, \quad \text{where } \omega_p = 1/C_P (r_{on} || r_{op}), \quad \omega_{pY} \approx 1/C_C (r_{on} || r_{op})$$

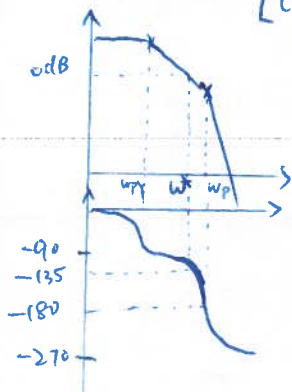

$$|A_0| = |(g_{mn} + g_{mp}) (r_{on} || r_{op})|$$

Assume ω^* the unity gain BW


$$\Rightarrow -2 \tan^{-1}(\omega^*/\omega_p) = -45^\circ$$

$$\frac{\omega^*}{\omega_p} \approx 0.414$$

$$\frac{A_0^3}{(1 + \frac{\omega^*}{\omega_p})^2 \sqrt{1 + (\frac{\omega^*}{\omega_{pY}})^2}} = 1$$

$$C_C = \frac{C_P}{0.414} \sqrt{\frac{A_0^6}{1.367} - 1}$$

$$-3\text{dB BW} = 1/C_C (r_{on} || r_{op}), \quad \text{Unity gain BW} = 0.414 / C_P (r_{on} || r_{op})$$

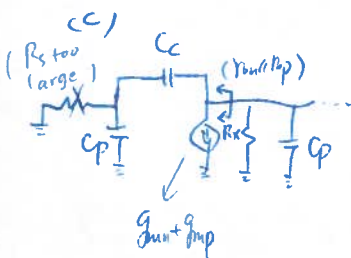

Small sig M3 & M4

$$A_0 = (g_{mn} + g_{mp}) (r_{on} || r_{op})$$

$$R_x = C_C + C_P / C_C (g_{mn} + g_{mp})$$

$$\omega_{pX} = 1/C_C (1 + A_0) (r_{on} || r_{op})$$

$$\omega_{pY} = 1 / \left(\frac{C_C + C_P}{C_C (g_{mn} + g_{mp})} || (r_{on} || r_{op}) \right) (C_P + \frac{C_P C_C}{C_P + C_C})$$

$$\approx (g_{mn} + g_{mp}) / 2 C_P$$

$$\omega_{pZ} = 1/C_P (r_{on} || r_{op})$$


pole splitting


the unity gain freq $\omega^* = \omega_{pZ}$

$$H(s) = \frac{A_0^3}{(1 + \frac{s}{\omega_{pX}}) (1 + \frac{s}{\omega_{pY}}) (1 + \frac{s}{\omega_{pZ}})}$$

$$\frac{A_0^3}{\sqrt{2} \cdot \sqrt{1 + (\frac{\omega_{pZ}}{\omega_{pX}})^2}} = 1$$


$$C_C = \frac{C_P}{1/A_0} \sqrt{\frac{A_0^6}{2} - 1}, \quad -3\text{dB BW} = 1/[C_C (1 + A_0)] (r_{on} || r_{op}), \quad BW_u = 1/C_C (r_{on} || r_{op})$$

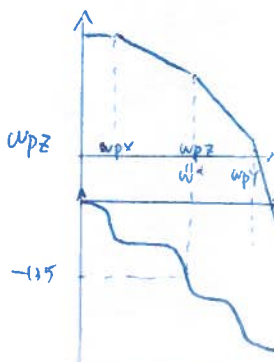

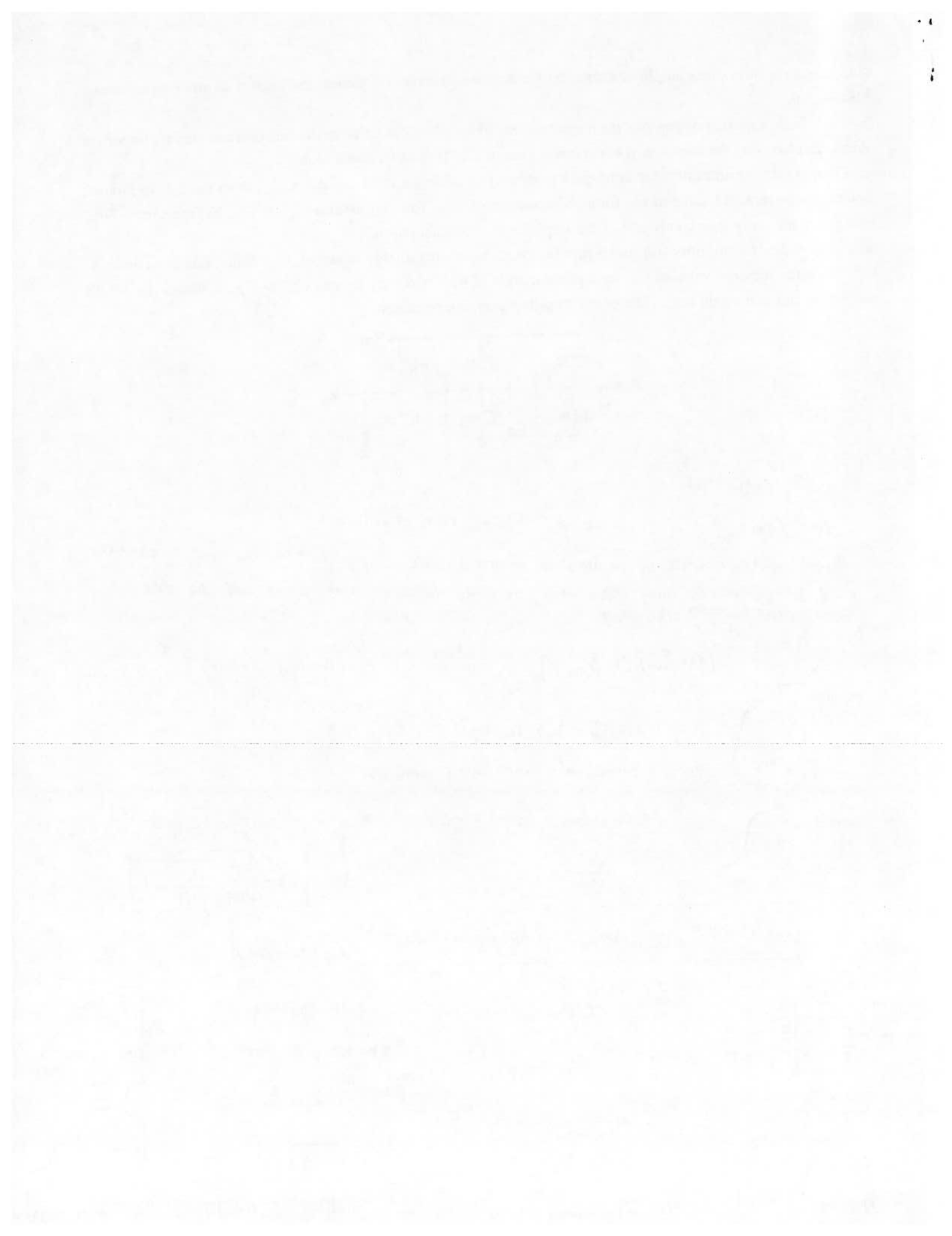

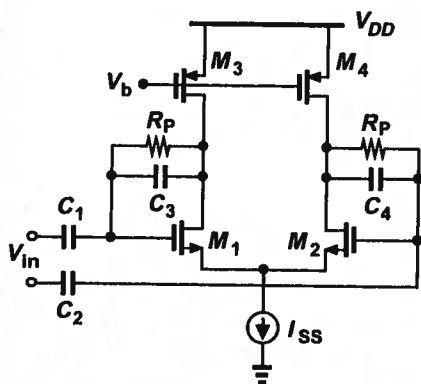
5. Consider the amplifier depicted below, where the common-mode feedback is not shown. Assume $\lambda \neq 0$, $V_{DD} = 3$ V, and the output CM level is 1.5 V. Neglect the transistor capacitances and assume R_p is very large.

- What is the maximum allowable differential output voltage swing?
- Determine the gain error of the circuit.
- Determine the small-signal time constant of the amplifier.
- Explain why you would or would not choose this topology for your final project.



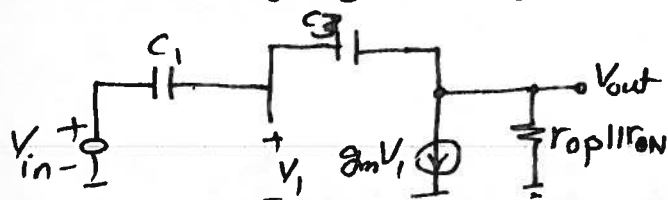(a) Each output node can swing by $\pm V_{TH}$ around the CM level $\Rightarrow$ total diff. swing = $\pm 2V_{TH}$.

(b), (c) Using the following equivalent circuit, we obtain the transfer function:



$$\frac{V_{out}}{V_{in}} = \frac{C_1 (C_3 s - g_m) (r_{op} || r_{on})}{(r_{op} || r_{on}) C_1 C_3 s + g_m (r_{op} || r_{on}) C_3 + C_1 + C_3}$$

$$\Rightarrow \tau = \frac{C_1 C_3 (r_{op} || r_{on})}{[g_m (r_{op} || r_{on}) + 1] C_3 + C_1}$$

$$\text{At } s=0, \quad \frac{V_{out}}{V_{in}} = \frac{-g_m C_1 (r_{op} || r_{on})}{g_m (r_{op} || r_{on}) C_3 + C_1 + C_3} = -\frac{C_1}{C_3} \frac{1}{1 + \frac{C_1 + C_3}{g_m (r_{op} || r_{on}) C_3}}$$

$$\Rightarrow \text{Gain Error} = \frac{C_1 + C_3}{C_3} \frac{1}{g_m (r_{op} || r_{on})}$$

(d) Since the gain error is too large, this topology would not meet the project's specifications.

EE215A

Final Exam

Fall 2011


Name:.....*Solutions*.....

Time Limit: 3 Hours



Open Book, Open Notes

Each problem has 20 points.


All transistors are in saturation.

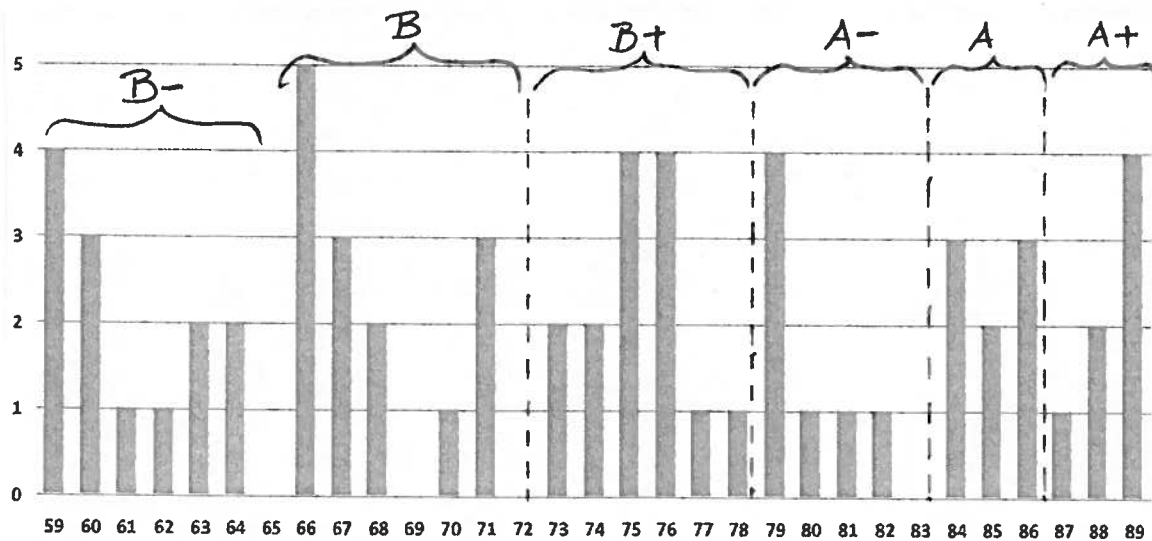

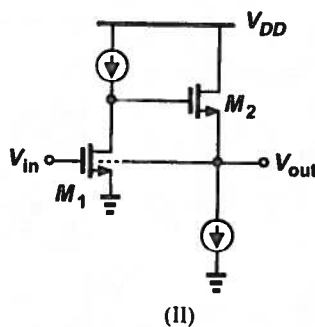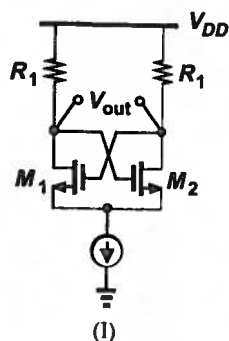1. Determine the output thermal noise voltage in each circuit. Neglect device capacitances and channel-length modulation. In the circuit in part (I), M_1 and M_2 are identical and carry equal bias currents. In the circuit in part (II), the output node is tied to the body of M_1 . Neglect the body effect of M_2 in this circuit. To avoid confusion between gammas, model the transistor noise as $4kT\Gamma g_m$.



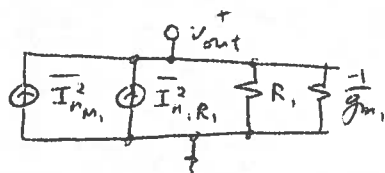Since the circuit is symmetrical, use half circuit:



$$\overline{V_{n,out}^2} = 2 \times (\overline{I_{n,M1}^2} + \overline{I_{n,R1}^2}) R_{out,half}^2$$


where:

$$\overline{I_{n,M1}^2} = 4kT\Gamma g_m$$

$$\overline{I_{n,R1}^2} = 4kT/R_1$$


$$R_{out,half}^2 = \left(R_1 \parallel \frac{1}{g_m} \right)^2$$

Small signal analysis:

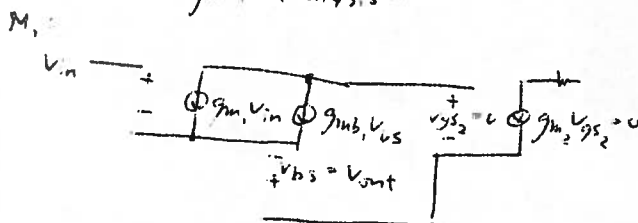

$$g_{m1} V_{ih} = -g_{m1b} V_{out}$$
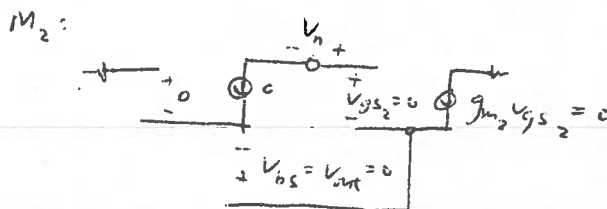
$$V_{out} = \frac{g_{m1}}{g_{m1b}} V_{ih}$$





noise of M_2 doesn't appear at the output (suppressed by the ∞ voltage gain from V_{out} to the drain voltage of M_1)

$$\overline{V_{n,out}^2} = \left(\frac{g_{m1}}{g_{m1b}} \right)^2 \frac{4kT\Gamma}{g_{m1}}$$

2. A differential pair can be degenerated to achieve greater linearity. Consider the two topologies shown below.


(a) How much headroom does the tail current source lose as a result of degeneration in circuit (I)?

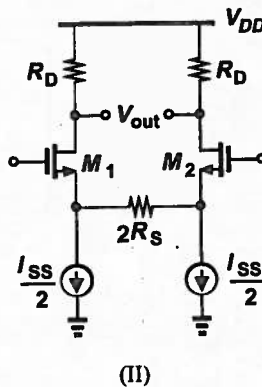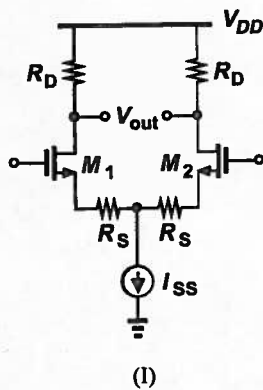(b) If we denote the noise current of each tail current source in circuit (II) by I_n , determine the output noise voltage of this circuit only due to I_n .



a) $R_S \frac{I_{SS}}{2}$

b)

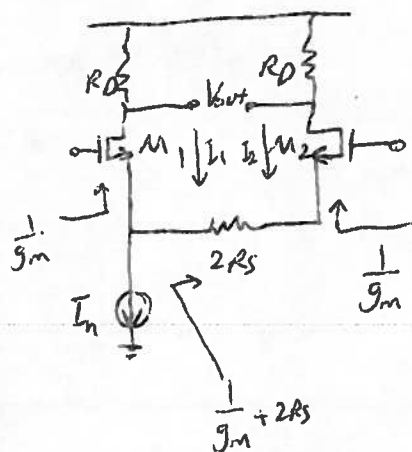

$$I_1 = I_n \times \frac{\frac{1}{g_m} + 2R_S}{\frac{2}{g_m} + 2R_S}$$

$$I_2 = I_n \times \frac{\frac{1}{g_m}}{\frac{2}{g_m} + 2R_S}$$

$$V_{out} = (I_1 - I_2) R_D = I_n \frac{2R_S}{\frac{2}{g_m} + 2R_S} R_D$$


$$= I_n \frac{R_S R_D}{\frac{1}{g_m} + R_S}$$

Two uncorrelated Noise Sources ; $\overline{V_{out,n}^2} = 2 \times \left(\frac{R_S R_D}{\frac{1}{g_m} + R_S} \right)^2 \overline{I_n^2}$

3. The differential pair shown below incorporates feedback capacitors to create a negative input capacitance. Neglect other capacitances and channel-length modulation.

(a) Determine the single-ended input impedance, defined as V_{in}/I_{in} .

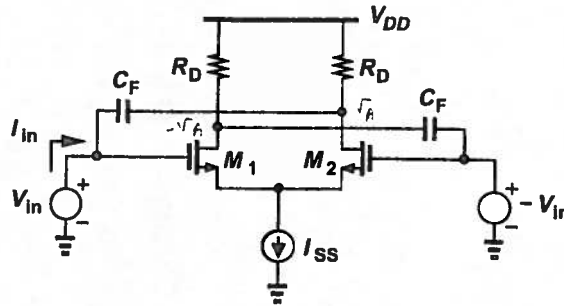
(b) Express the result as an RC network. What happens as $C_F \rightarrow \infty$? Explain why this result is to be expected.



(a) KCL @ drain of M_2 : $\frac{V_A}{R_D} - g_m V_{in} + (V_A - V_{in}) C_F \cdot s = 0 \Rightarrow V_A = V_{in} \cdot \frac{g_m C_F}{C_F s + 1}$

$$I_{in} = (V_{in} - V_A) C_F \cdot s \Rightarrow Z_{in} = \frac{V_{in}}{I_{in}} = \frac{R_D}{1 - g_m R_D} + \frac{1}{C_F s (1 - g_m R_D)}$$

$g_m R_D > 1 \Rightarrow$ negative cap

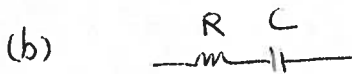


$$C = C_F (1 - g_m R_D)$$

$$R = R_D \cdot \frac{1}{1 - g_m R_D}$$

$$C_F \rightarrow \infty \Rightarrow Z_{in} = \frac{R_D}{1 - g_m R_D}$$

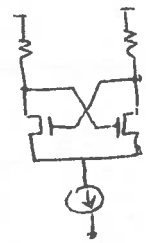when $C_F \rightarrow \infty$, it's like a cross coupled pair



$$Z = R_D \parallel \frac{1}{g_m} = \frac{R_D}{1 - g_m R_D}$$


4. The circuit shown below is a simplified model of a two-stage op amp, where C_C is the compensation capacitor. Neglect other capacitances and channel-length modulation.

(a) Assuming $g_m R_D \gg 1$, estimate ω_{p1} , ω_{p2} , and ω_z , where ω_z denotes the zero frequency.

(b) What condition is necessary for $|\omega_{p2}|$ to be equal to $|\omega_z|$?

(c) Suppose $|\omega_{p2}| = |\omega_z|$. Plot the magnitude and phase of $\beta H(s)$ (with $\beta = 1$) as a function of frequency.

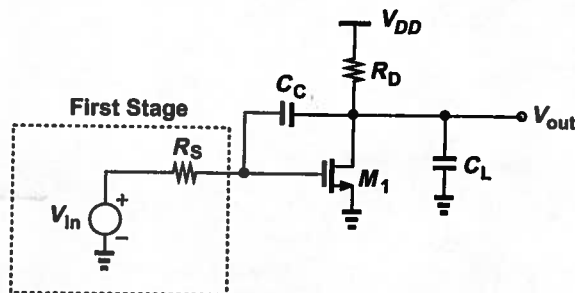(d) Construct the magnitude and phase plots if C_C increases or decreases from the value assumed in part (c). What happens to the phase margin in each case?




$$(a) \omega_{p1} \approx -\frac{1}{R_s g_m R_D C_L}$$

$$\omega_{p2} \approx -\frac{g_m}{C_L}$$


$$\omega_z \approx \frac{g_m}{C_C}$$

$$(b) |\omega_{p2}| = |\omega_z| \Rightarrow C_C = C_L$$

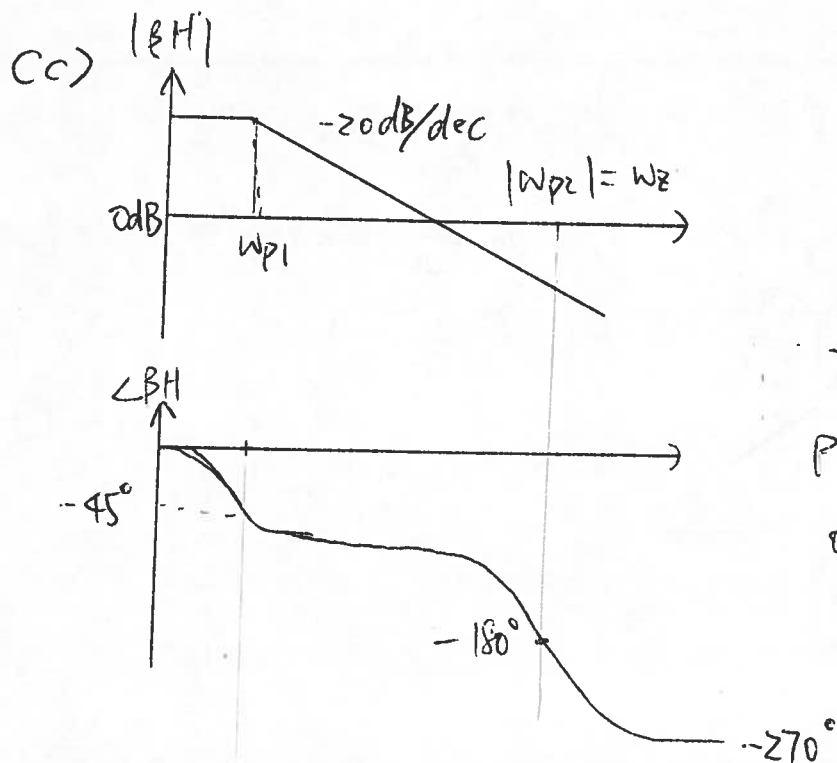


The 0dB point should be between ω_{p1} and ω_{p2} , so that we have a reasonable phase margin. (d) depends on this notion.

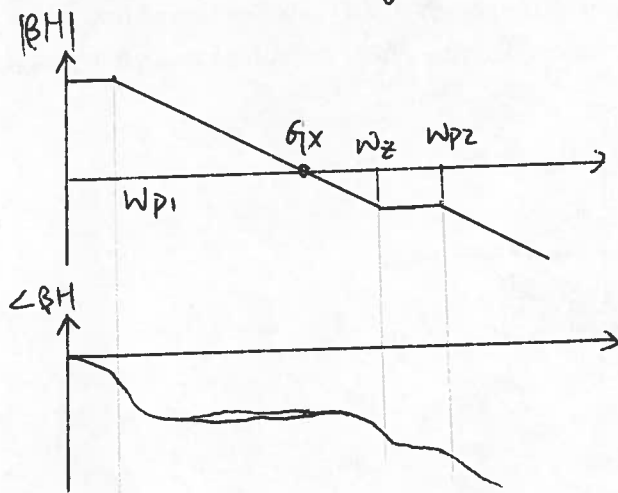(d) As C_c increases, ω_{p1} and ω_z moves toward the origin while ω_{p2} stays.




The gain crossing point G_x decrease while $\tan^{-1} \frac{G_x}{\omega_z}$ remains the same. Furthermore, $\tan^{-1} \frac{G_x}{\omega_{p2}}$ decreases. Therefore the phase margin increases.

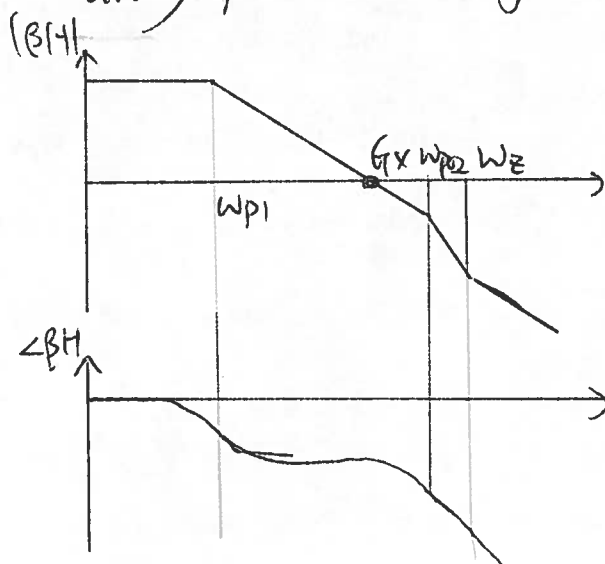As C_c decreases, ω_{p1} and ω_z moves away from the origin while ω_{p2} stays.



1. $G_x \uparrow$
 2. $\tan^{-1} \frac{G_x}{\omega_z}$ almost the same
 3. $\tan^{-1} \frac{G_x}{\omega_{p2}} \uparrow$
- $\Rightarrow$ phase margin $\downarrow$

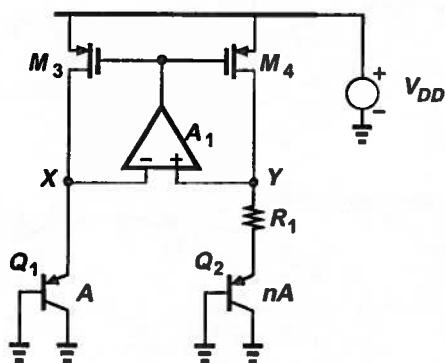
5. Consider the bandgap circuit shown below. We wish to study the noise in V_X and V_Y as a result of supply noise. Assume M_3 and M_4 are identical and model the bipolar devices by a resistance equal to $1/g_{mbi}$.
- (a) If $A_1 = \infty$ and channel-length modulation is neglected, compute the small signal gain from V_{DD} to V_X and V_Y .
- (b) If $A_1 = \infty$ and channel-length modulation is not neglected, compute the small signal gain from V_{DD} to V_X and V_Y .
- (c) If $A_1 < \infty$ and channel-length modulation is neglected, compute the small signal gain from V_{DD} to V_X and V_Y .



Points $\rightarrow 6 + 6 + 8$

For each case, we study the effect of a small disturbance v_{dd} on V_{DD} .

a)

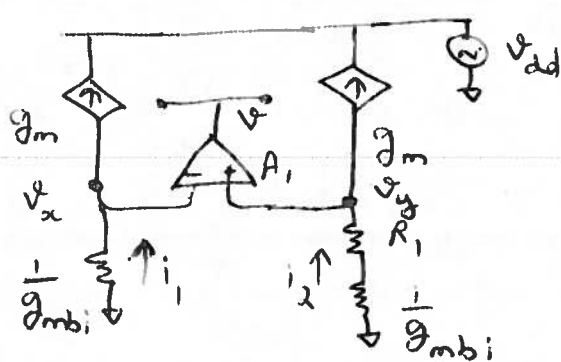

$A_1 = \infty$ no C.L.M


$$i_1 = i_2 = g_m(v - v_{dd})$$

But $v_x = v_y$ due to ∞ gain of op-amp.

$$\Rightarrow i_1 = i_2 = 0 \quad (v = v_{dd})$$

$$\Rightarrow \boxed{v_x = v_y = 0}$$

b)

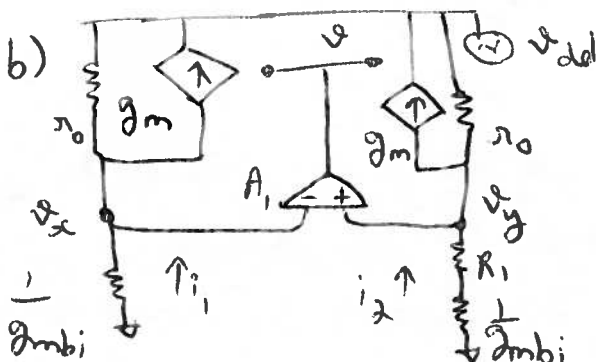

$A_1 = \infty$ $r_o \neq \infty$

Again $v_x = v_y$


$$\Rightarrow i_1 / g_{mbi} = i_2 (R_1 + \frac{1}{g_{mbi}})$$

$$\Rightarrow \frac{g_m(v - v_{dd}) + \frac{(v_x - v_{dd})}{r_o}}{g_{mbi}} = \left[\frac{g_m(v - v_{dd})}{g_{mbi}} + \frac{v_x - v_{dd}}{r_o} \right] \times \left[R_1 + \frac{1}{g_{mbi}} \right]$$

P.T.O.

$$\Rightarrow v_x = v_y = 0$$

c)

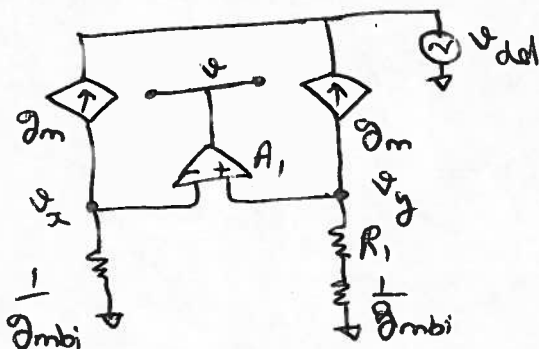

$A_1 < \infty$ no CLM

In this case, v_x & v_y are not equal & v does not track v_{dd} exactly.

$$v_x = -g_m(v - v_{dd}) \frac{1}{g_{mbi}}$$

$$v_y = -g_m(v - v_{dd}) \left[R_1 + \frac{1}{g_{mbi}} \right]$$

$$v = A(v_y - v_x) = -g_m(v - v_{dd}) R_1 A$$

$$\Rightarrow v = v_{dd} \frac{g_m R_1 A}{g_m R_1 A + 1}$$

$$\Rightarrow v_x = v_{dd} \cdot \frac{g_m / g_{mbi}}{g_m R_1 A + 1}$$

$$v_y = v_{dd} \cdot \frac{g_m \left[R_1 + \frac{1}{g_{mbi}} \right]}{g_m R_1 A + 1}$$