

EE215A

Midterm Exam

Fall 2011

Time Limit: 2 hours

Open Book, Open Notes

Calculators are allowed.

Your Name:

Solutions

Name of Person to Your Left:


Name of Person to Your Right:

1. 20


2. 20

3. 20

4. 20

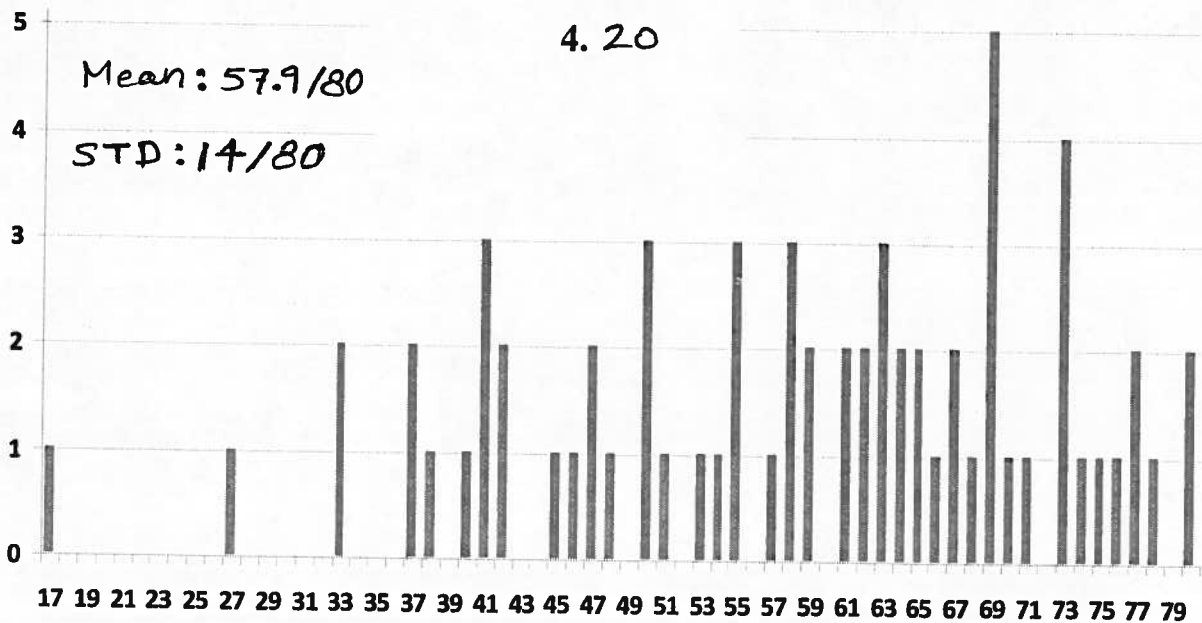

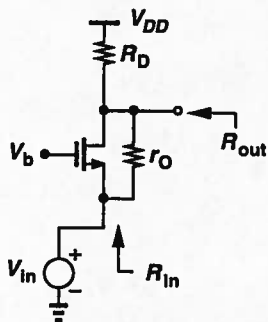1. (a) Neglecting body effect, use Miller's theorem to determine R_{in} and R_{out} for the circuit shown below.
 (b) Compare your results with our previous derivations and explain in detail.



(a) With $\gamma=0$, the voltage gain from the source to the drain is equal to $A = \frac{g_m r_o + 1}{r_o + R_D} R_D$. We divide r_o by $1-A$ and place the result in parallel with $\frac{1}{g_m}$:


$$R_{in} = \frac{1}{g_m} \parallel \frac{r_o}{1-A}$$

$$= \frac{r_o + R_D}{1 + g_m r_o}$$

For R_{out} , if we place $\frac{r_o}{1-A}$ in parallel with R_D , we obtain


$$R_{out} = \frac{r_o}{1 - \frac{r_o + R_D}{(1 + g_m r_o) R_D}} \parallel R_D$$
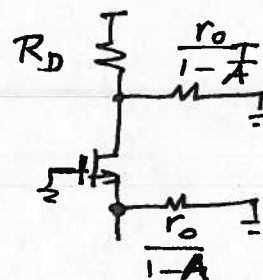
$$= \frac{(1 + g_m r_o) R_D}{g_m R_D - 1} \parallel R_D$$



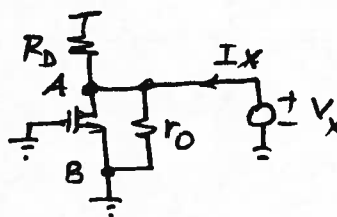
- (b) R_{in} is computed correctly. But, R_{out} is not. This is because for output resistance calculation, we apply the stimulus to the output node, altering the "gain" from the source to the drain:

We can still apply Miller's theorem here but with the "gain" from A to B (i.e., zero).



2. (a) Neglecting channel-length modulation and body effect, sketch I_X , V_A , and V_B as a function of V_X as V_X varies from zero to V_{DD} . Assume M_1 and M_2 are identical and so are M_3 and M_4 .

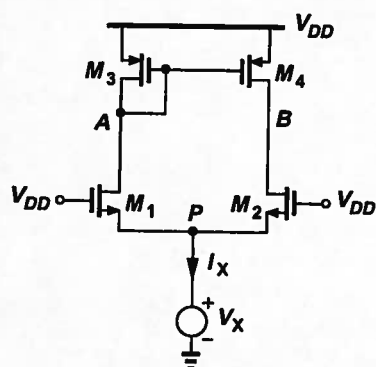(b) Write a quadratic equation that yields the value of V_B for $V_X = 0$. You need not solve the equation.




If M_1 and M_3 are in the saturation region,

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_X - V_{TN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (V_{DD} - V_A - |V_{TP}|)^2$$

For simplicity, let's assume $\mu_n \left(\frac{W}{L}\right)_1 = \mu_p \left(\frac{W}{L}\right)_3$, ~~$V_{TN} = |V_{TP}|$~~ .

$$V_A = V_{DD} - |V_{TP}| - (V_{DD} - V_{TN}) = \underline{V_{TN} - |V_{TP}|} \quad (\text{when } V_X = 0)$$

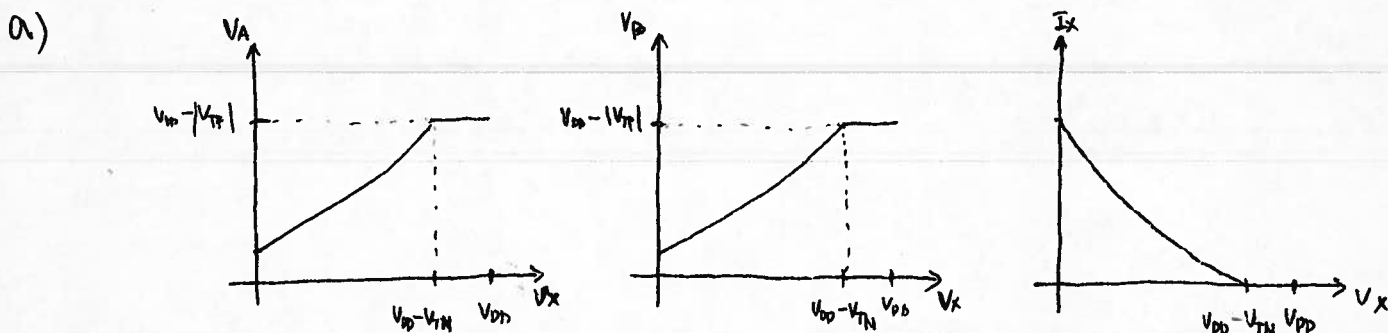So, M_1 is in the triode region. So as M_2 ^{very small}



When $V_X = V_{DD} - V_{TN}$, M_1 and M_2 are turned off, and V_A and V_B stay.


b) M_1 : triode region ($V_X = 0$)
 M_3 : saturation region

$$I_1 = I_3$$


$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left\{ (V_{DD} - V_{TN}) \cdot V_A - \frac{1}{2} V_A^2 \right\} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (V_{DD} - V_A - |V_{TP}|)^2 \quad \dots \textcircled{1}$$

$$V_A = V_B \quad \dots \textcircled{2}$$


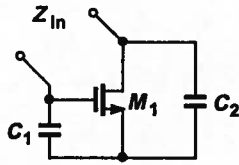
3. Neglecting channel-length modulation and body effect, determine Z_{in} for the circuits shown below. Assume M_1 is biased in saturation and neglect other capacitances. Can you express each Z_{in} as a series or parallel combination of resistors and capacitors?



(a)

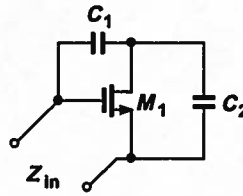



(b)

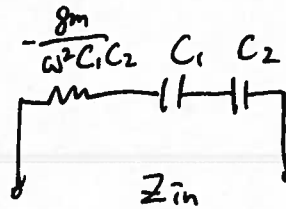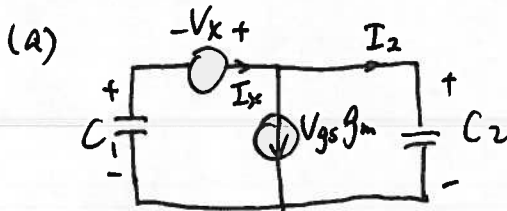

$$V_{gs} = V_{C1} = -I_x \frac{1}{sC_1}$$

$$I_x = V_{gs} g_m + I_2 = -I_x \frac{g_m}{sC_1} + (V_x - I_x \frac{1}{sC_1}) sC_2$$
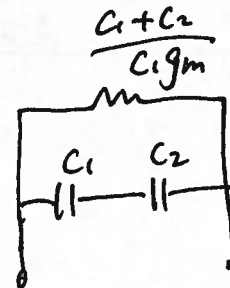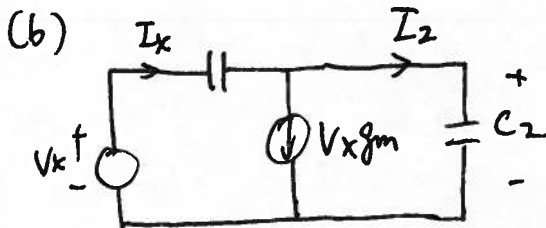
$$Z_{in} = \frac{V_x}{I_x} = \frac{g_m}{s^2 C_1 C_2} + \frac{1}{sC_1} + \frac{1}{sC_2} = -\frac{g_m}{\omega^2 C_1 C_2} + \frac{1}{sC_1} + \frac{1}{sC_2}$$




$$I_2 = (V_x - I_x \frac{1}{sC_1}) sC_2$$


$$\Rightarrow I_x = V_x g_m + I_2 = V_x g_m + (V_x - I_x \frac{1}{sC_1}) sC_2$$

$$\Rightarrow Z_{in} = \frac{V_x}{I_x} = \frac{1 + \frac{sC_2}{sC_1}}{g_m + sC_2} = \frac{C_1 + C_2}{C_1 g_m + sC_1 C_2}$$

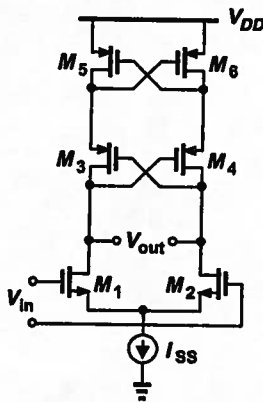
4. Determine the differential voltage gain of the circuit shown below if channel-length modulation and body effect are negligible.



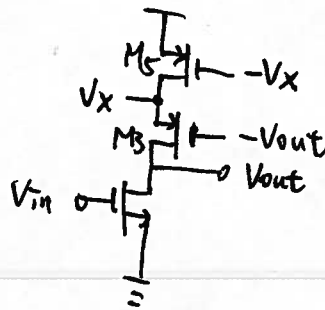When neglecting channel-length modulation and body effect, the half circuit:



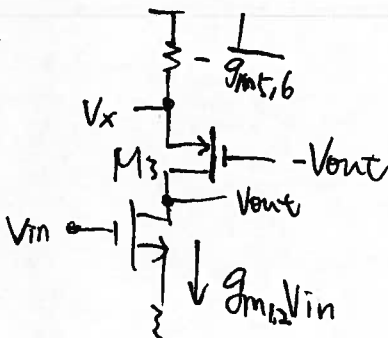Furthermore, M_5 can be equivalent to a resistor, whose resistance is $-\frac{1}{g_{m5,6}}$



$$g_{m1,2} V_{in} = V_x g_{m5,6} = (V_x + V_{out}) g_{m3,4}$$

$$\Rightarrow V_{out} = \left(\frac{g_{m5,6}}{g_{m3,4}} - 1 \right) V_x = \frac{g_{m5,6} - g_{m3,4}}{g_{m3,4}} V_x$$

$$g_{m1,2} V_{in} = \frac{g_{m3,4} \cdot g_{m5,6}}{g_{m5,6} - g_{m3,4}} V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = g_{m1,2} \cdot \frac{g_{m5,6} - g_{m3,4}}{g_{m3,4} \cdot g_{m5,6}}$$