
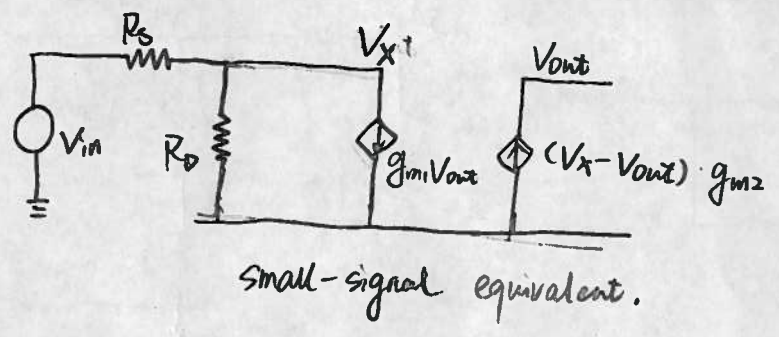


Problem 1

Jieqiong Du


40/40

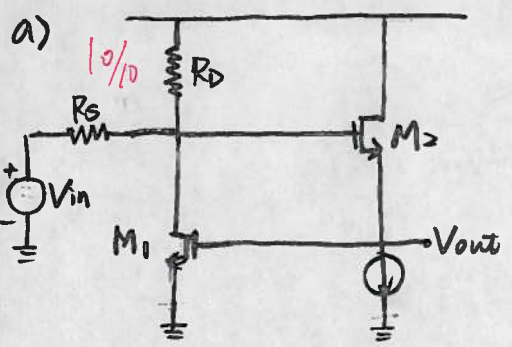

$$V_x = V_{out} \quad (1)$$

$$\frac{V_{in}}{R_s} = \frac{V_x}{R_s} + g_{m1} V_{out} \quad (2)$$
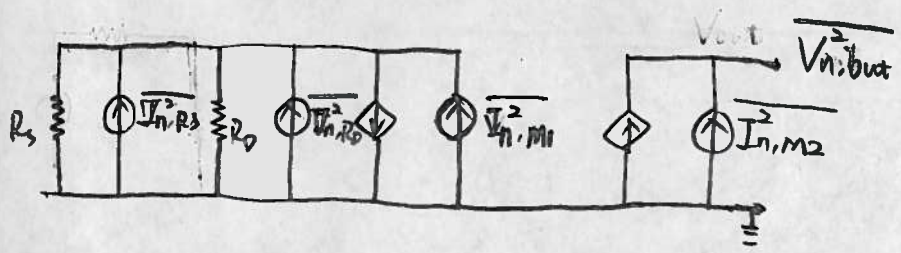
$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_D}{g_{m1} R_D \cdot R_s + R_s + R_D}$$




$$\overline{V_{n,out}^2} = \overline{V_{n,out,R_s}^2} + \overline{V_{n,out,R_D}^2} + \overline{V_{n,out,M_1}^2} + \overline{V_{n,out,M_2}^2}$$

$$\overline{V_{n,out,R_s}^2} = 4kTR_s A^2 \quad ; \quad \overline{V_{n,out,R_D}^2} = \frac{4kTR_s^2}{R_{D1}} A^2 \quad ; \quad \overline{V_{n,out,R_{M1}}^2} = 4kT \gamma g_{m1} R_s^2 A^2$$

$$\overline{V_{n,out,M_2}^2} = 4kT \gamma g_{m2} \left| \frac{V_{out}}{I} \right|^2$$

$$\left| \frac{V_{out}}{I} \right|^2 = \left(\frac{R_s + R_D}{g_{m2} (R_s + R_D) + g_{m1} g_{m2} R_s R_D} \right)^2$$


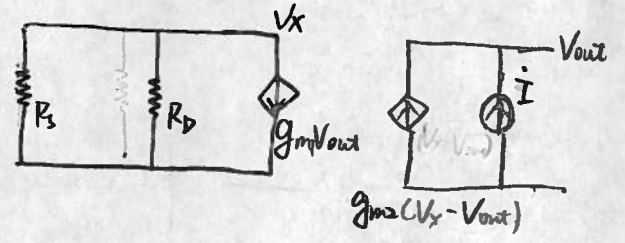


$$\overline{V_{n,out}^2} = (4kTR_s + \frac{4kTR_s^2}{R_{D1}} + 4kT \gamma g_{m1} R_s^2) A^2 + 4kT \gamma g_{m2} \left| \frac{V_{out}}{I} \right|^2$$

$$NF = \frac{\overline{V_{n,out}^2}}{4kTR_s A^2} = 1 + \frac{R_s}{R_D} + \gamma g_{m1} R_s + \gamma \frac{(R_s + R_D)^2}{g_{m2} R_D^2 R_s}$$

If $R_D \rightarrow \infty$, $NF = 1 + \gamma g_{m1} R_s + \frac{\gamma}{g_{m2} R_s}$ This is because even though $\overline{V_{n,RD}} \propto R_D$, $A \propto R_D^2$, thereby, NF is smaller. 3/3

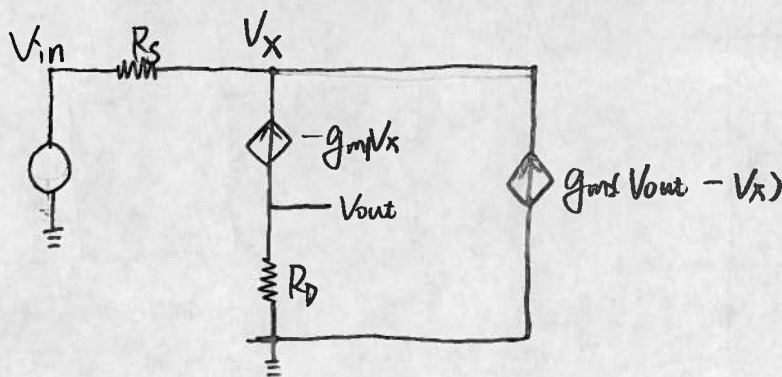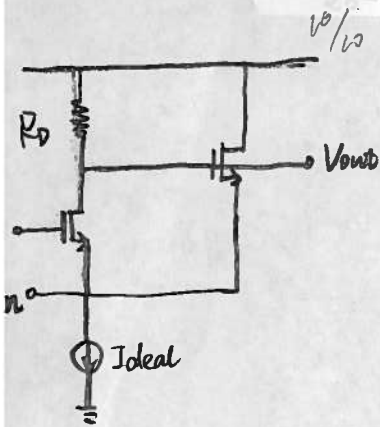
If $g_{m1} \rightarrow 0$, $NF = 1 + \frac{R_s}{R_D} + \gamma \frac{(R_s + R_D)^2}{g_{m2} R_D^2}$ The noise figure becomes smaller. 2/2




$$\frac{V_x - V_{in}}{R_S} = -g_m V_x + g_m(V_{out} - V_x)$$

$$+g_m V_x = V_{out}/R_D$$

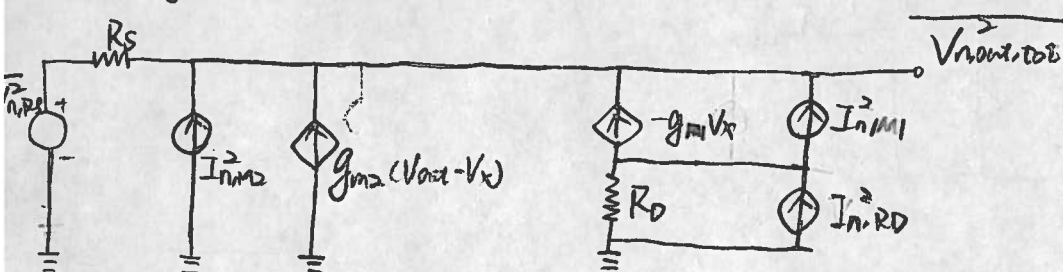
$$\begin{aligned} \textcircled{1} \quad A &= \frac{V_{out}}{V_{in}} = \frac{g_m R_D}{1 + g_m R_S - g_m g_{m2} R_S R_D} \\ \textcircled{2} \end{aligned}$$


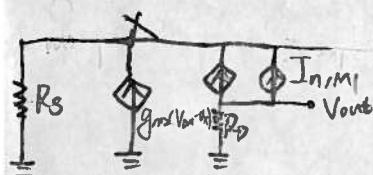
$$V_{n,out,RS}^2 = 4kTR_S A^2 \quad ; \quad V_{n,out \rightarrow n2}^2 = 4kT \gamma g_{m2} R_S^2 A^2$$



$$\left| \frac{V_{n,out}}{I_{n,M1}} \right| = \frac{(g_{m2} R_S + 1) R_D}{1 + g_{m1} R_S + g_{m2} R_S - g_{m1} g_{m2} R_S R_D}$$

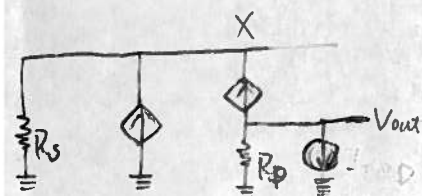

$$\left| \frac{V_{n,out}}{I_{n,RS}} \right| = \frac{(g_{m2} R_S + g_{m1} R_S + 1) R_D}{1 + g_{m1} R_S + g_{m2} R_S - g_{m1} g_{m2} R_S R_D}$$

$$V_{n,out,tot}^2 = 4kTR_S A^2 + 4kT \gamma g_{m2} R_S^2 A^2 + 4kT \gamma g_{m1} \left| \frac{V_{n,out}}{I_{n,M1}} \right|^2 + \frac{4kT}{R_D} \left| \frac{V_{n,out}}{I_{n,RS}} \right|^2$$

$$NF = \frac{V_{n,out,tot}^2}{4kTR_S A^2} = 1 + \gamma g_{m2} R_S + \frac{\gamma (g_{m2} R_S + 1)^2}{g_{m1} R_S} + \frac{(g_{m2} R_S + g_{m1} R_S + 1)^2}{g_{m1}^2 R_S R_D}$$


$$\text{If } R_D \rightarrow \infty, NF = 1 + \gamma g_{m2} R_S + \frac{\gamma (g_{m2} R_S + 1)^2}{g_{m1} R_S}$$

$$\text{If } g_{m2} \rightarrow 0, NF = 1 + \frac{\gamma}{g_{m1} R_S} + \frac{(g_{m1} R_S + 1)^2}{g_{m1}^2 R_S R_D}$$


As \$R_D\$ gets infinite, \$\overline{V_{n,RD}} \propto R_D\$,
But, the gain signal power increased by
\$R_D^2\$, so NF gets better.

Problem 2

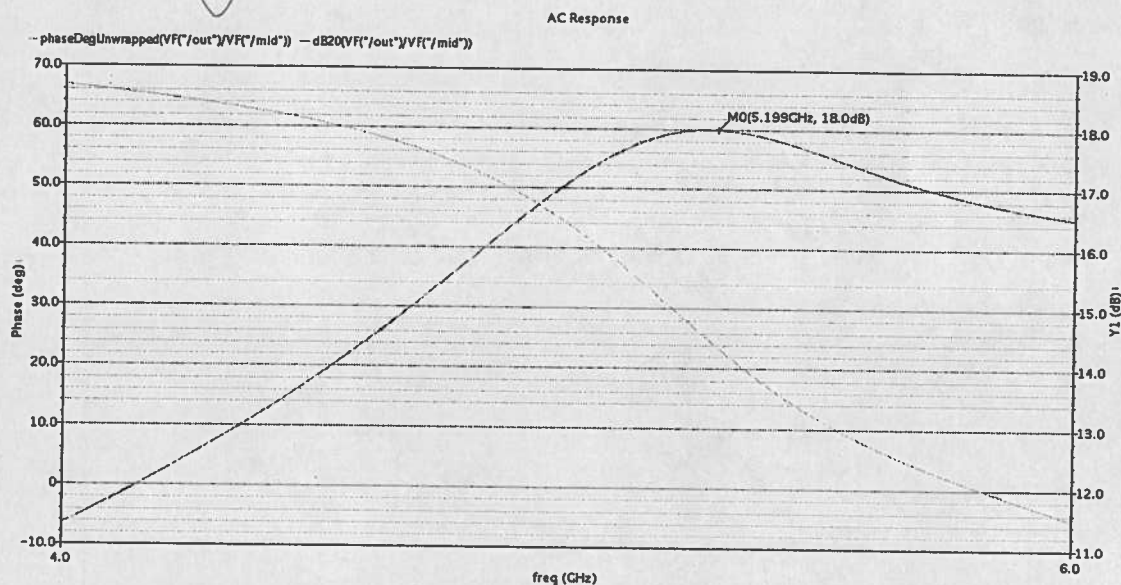a) $L_D = 8.5 \text{ nH}$
 $W_D = 4.1 \mu\text{M}$ ✓



b) Measured NF = 2.457 dB ✓

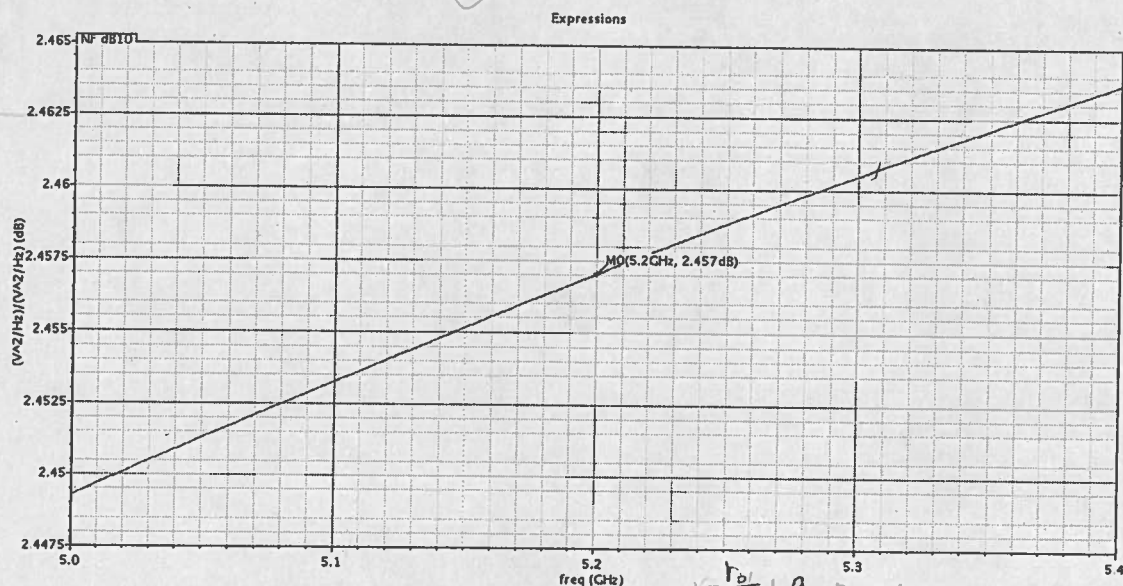

$$g_{m1} = 2.66 \text{ mS}$$

$$g_{mb} = 3.92 \text{ mS}$$


$$r_{o1} = \frac{1}{g_{ds}} = 1003.5 \Omega$$

$$A = \frac{V_{out}}{V_{in}} = \frac{1 + \frac{r_{o1}}{R_i} + g_{m1}r_{o1} + 1}{1 + \frac{R_s}{R_o} \cdot \frac{r_{o1}}{R_i} + g_{m1}r_{o1} + 1} = 5.4$$


$$NF = 1 + \frac{(R_o || r_{o1})^2 / R_o}{R_s A_o^2} + \frac{g_{mb}}{R_s A_o^2} \left(\frac{1}{1 + R_s g_{mb}} \right)^2 (R_o || r_{o1})^2$$

$$= 1 + 0.197 + 8 \cdot 0.76 \quad (r = 0.66)$$

$$= 1.6986$$

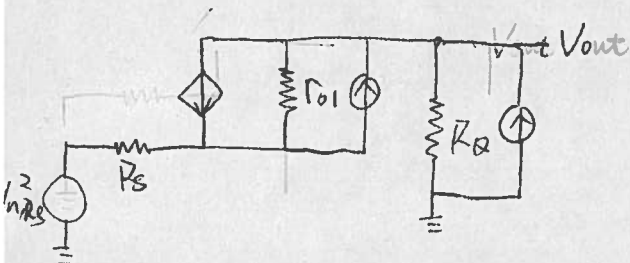

Expressions

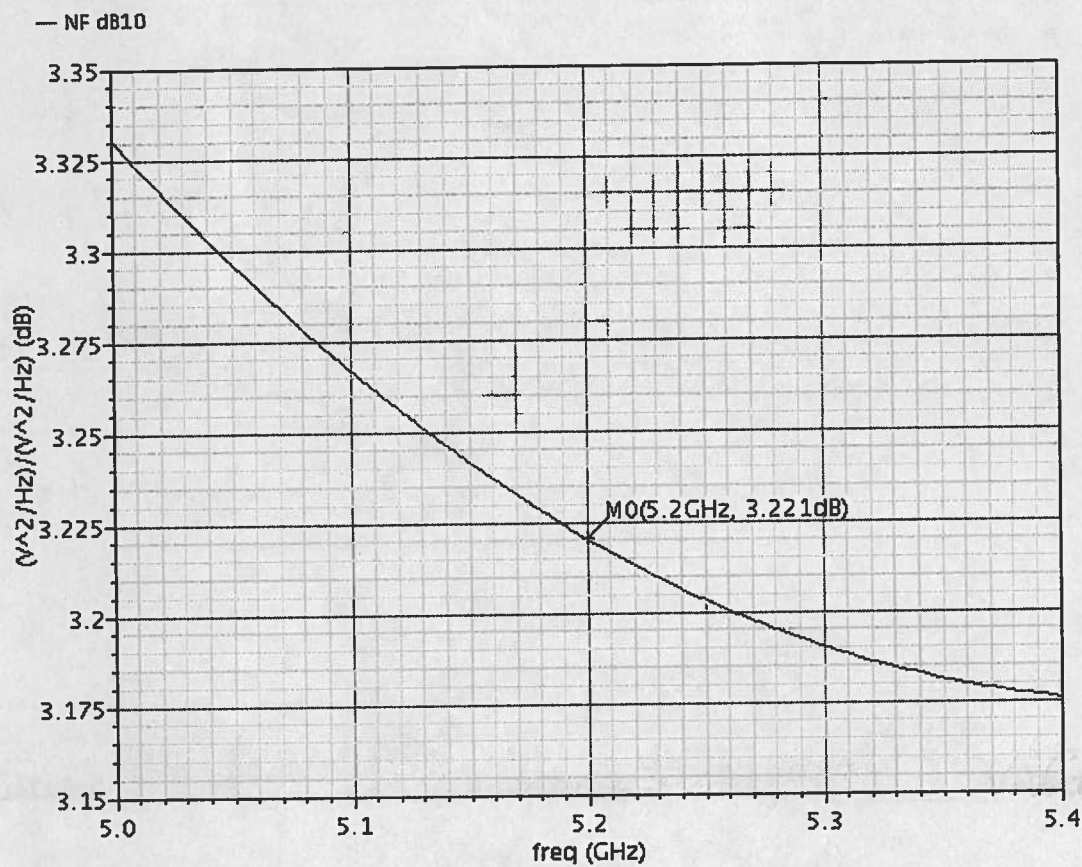

$$NF_1 = 1.76 \quad NF_{\text{tot}} = 2.10$$

$$\Delta NF = 0.34$$

The contribution of the second stage to NF is very small.