

**EE215C**


**Midterm Exam**

**Winter 2013**

Name: Solution S

**Time Limit: 2 Hours**

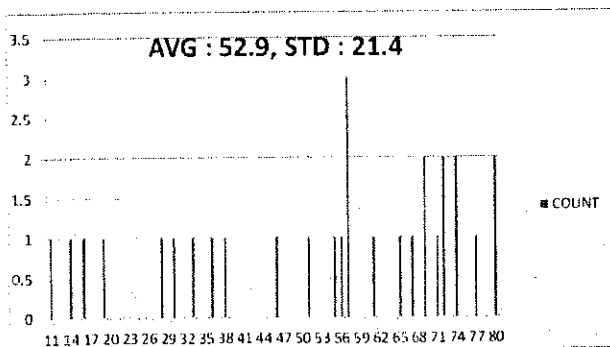**Open Book, Open Notes, Calculators are allowed.**



1. 20

2. 20

3. 20

4. 20

Total: 80


1. Consider the amplifier shown below. The transistors operate in saturation and channel-length modulation and body effect are neglected.

(a) Compute the input resistance,  $R_{in}$ .


(b) Compute the noise figure of the circuit with respect to a source impedance  $R_S$ .

(c) Simplify the NF expression if  $R_{in} = R_S$ . Can you compare this result with the NF of a simple CG stage?

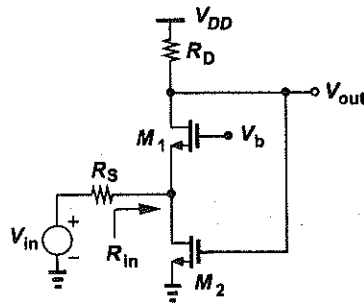(d) Suppose a mixer following this circuit produces an LO voltage waveform  $V_0 \cos \omega_0 t$  at the drain of  $M_1$ . Determine the LO leakage to the antenna.


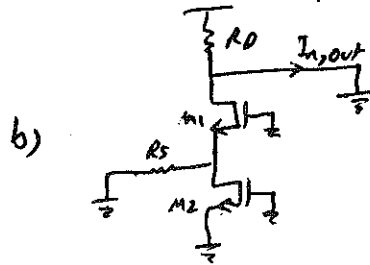
$$a) R_{in} = \frac{1}{g_{m1}} \parallel \frac{1}{g_{m1} R_D g_{m2}} = \frac{1}{g_{m1} (1 + g_{m2} R_D)}$$



$$\overline{I_{n,out,R_S}^2} = \frac{4kT}{R_S} \left( \frac{R_S}{R_S + \frac{1}{g_{m1}}} \right)^2$$

$$\overline{I_{n,out,R_D}^2} = \frac{4kT}{R_D}$$

$$\overline{I_{n,out,M_2}^2} = 4kT \gamma g_{m2} \left( \frac{R_S}{R_S + \frac{1}{g_{m1}}} \right)^2$$

$$\overline{I_{n,out,M_1}^2} = 4kT \gamma g_{m1} \left( \frac{\frac{1}{g_{m1}}}{R_S + \frac{1}{g_{m1}}} \right)^2$$


$$NF = \frac{\overline{I_{n,out,tot}^2}}{\overline{I_{n,out,R_S}^2}} = 1 + \gamma g_{m2} R_S + \frac{\gamma}{g_{m1} R_S} + \frac{(R_S + \frac{1}{g_{m1}})^2}{R_D R_S}$$

$$c) NF = 1 + \gamma [1 + g_{m2} (R_D + R_S)] + \frac{(R_S + \frac{1}{g_{m1}})^2}{R_D R_S} \quad \frac{1}{g_{m1}} = R_S (1 + g_{m2} R_D) > R_S$$

$$\Rightarrow \frac{(R_S + \frac{1}{g_{m1}})^2}{R_D R_S} > \frac{4R_S}{R_D} \quad , \quad \text{Also } \gamma [1 + g_{m2} (R_D + R_S)] > \gamma \Rightarrow NF > NF_{CG}$$

$$CG: NF_{CG} = 1 + \gamma + \frac{4R_S}{R_D}$$
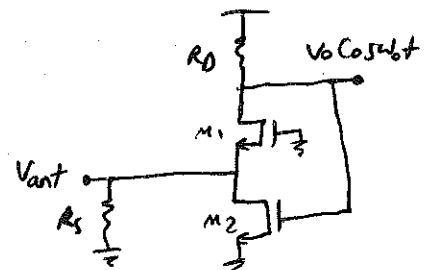
$$d) V_{ant} = g_{m2} V_0 \cos \omega_0 t \left( \frac{\frac{1}{g_{m1}}}{R_S + \frac{1}{g_{m1}}} \right) \times R_S$$




2. A single MOSFET can serve as a "poor man's" mixer. Suppose the device is in saturation and the output of interest is  $I_{out}$ . Neglect channel-length modulation and body effect. Assume the device is characterized by  $I_D = K(V_{RF} - V_{LO})^2$ , where  $V_{LO} = B \cos \omega_{LO} t$ . The LO amplitude is not large enough to cause complete switching.

(a) Suppose  $V_{RF} = A \cos \omega_1 t + V_{GS0}$ , where  $V_{GS0}$  is a bias value to ensure the device is on and has the required transconductance. Determine the voltage conversion gain of the mixer.

(b) Suppose  $V_{RF} = A \cos \omega_1 t + A \cos \omega_2 t + V_{GS0}$ . Determine the  $IIP_2$  of the mixer.

(a)

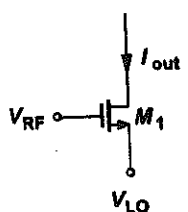

$$\begin{aligned}
 I_{out} &= K (V_{RF} - V_{LO})^2 \\
 &= K (A \cos \omega_1 t + V_{GS0} - B \cos \omega_{LO} t)^2 \\
 &= K (A^2 \cos^2 \omega_1 t + V_{GS0}^2 + B^2 \cos^2 \omega_{LO} t \\
 &\quad - 2AB \cos \omega_1 t \cos \omega_{LO} t + 2A V_{GS0} \cos \omega_1 t \\
 &\quad - 2B V_{GS0} \cos \omega_{LO} t) \\
 &= K \left( A^2 \frac{1 + \cos 2\omega_1 t}{2} + V_{GS0}^2 + B^2 \frac{1 + \cos 2\omega_{LO} t}{2} \right. \\
 &\quad \left. - 2AB \frac{\cos(\omega_1 + \omega_{LO})t + \cos(\omega_1 - \omega_{LO})t}{2} + 2A V_{GS0} \cos \omega_1 t \right. \\
 &\quad \left. - 2B V_{GS0} \cos \omega_{LO} t \right)
 \end{aligned}$$

$$\text{Conversion gain} = \frac{-ABK}{A} = -BK$$

(b)

$$\begin{aligned}
 I_{out} &= K (A \cos \omega_1 t + A \cos \omega_2 t + V_{GS0} - B \cos \omega_{LO} t)^2 \\
 &= K (A^2 \cos \omega_1 t \cos \omega_2 t - 2AB \cos \omega_1 t \cos \omega_{LO} t + \dots) \\
 &= K \{ A^2 [\cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t] - AB [\cos(\omega_1 - \omega_{LO})t + \cos(\omega_1 + \omega_{LO})t] \\
 &\quad + \dots \}
 \end{aligned}$$

$$A_{IIP2}^2 = A_{IP2} \cdot B$$


$$\Rightarrow A_{IIP2} = B$$

3. Consider the common-gate LNA shown below, where an auxiliary amplifier is added to cancel the noise of  $M_1$ . Neglect channel-length modulation and body effect.


(a) Determine  $A_0$  so that the noise of  $M_1$  is cancelled.

(b) Determine the overall voltage gain of the circuit,  $V_{out}/V_{in}$ .

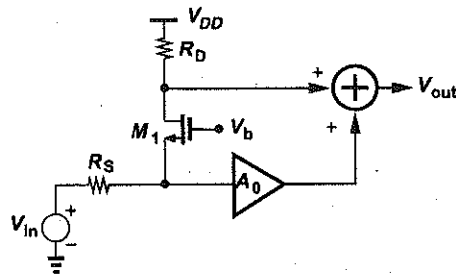(c) Determine the overall noise figure if the auxiliary amplifier exhibits an input-referred noise voltage of  $\overline{V_n^2}$ .



a)

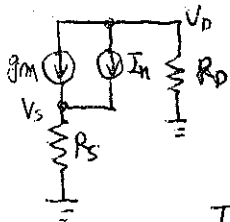

$$I_n = g_m V_S + \frac{V_S}{R_S}$$

$$\therefore \frac{R_S}{1 + g_m R_S} I_n = V_S$$

$$I_n - g_m V_S + \frac{V_D}{R_D} = 0$$


$$\therefore \frac{-R_D}{1 + g_m R_S} I_n = V_D$$

To cancel  $I_n$ ,

$$A_0 \cdot \frac{R_S}{1 + g_m R_S} I_n - \frac{R_D}{1 + g_m R_S} I_n = 0$$

$$\therefore A_0 = \frac{R_D}{R_S}$$

b)

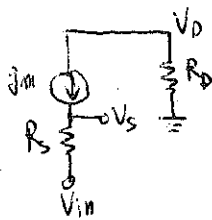

$$V_S = \frac{1}{\frac{1}{g_m} + R_S} V_{in}$$

$$V_D = g_m R_D V_S = \frac{g_m R_D}{1 + g_m R_S} V_{in}$$

$$V_{out} = A_0 V_S + V_D = \left( \frac{A_0}{1 + g_m R_S} + \frac{g_m R_D}{1 + g_m R_S} \right) V_{in}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{R_D}{R_S}$$

$$c) \overline{V_{n,out}^2} = 4kTR_S \left( \frac{R_D}{R_S} \right)^2 + \overline{V_n^2} \left( \frac{R_D}{R_S} \right)^2 + 4kTR_D$$


$$\overline{V_{n,in}^2} = 4kTR_S + \overline{V_n^2} + 4kT \cdot \frac{R_S^2}{R_D}$$

$$NF = \frac{\overline{V_{n,in}^2}}{4kTR_S} = 1 + \frac{R_S}{R_D} + \frac{\overline{V_n^2}}{4kTR_S}$$

4. We know that the input to a mixer can feed to the output without frequency translation if the circuit has asymmetries. We wish to study the feedthrough of the flicker noise of  $M_1$  to the output in the presence of an offset voltage,  $V_{OS}$ .

(a) Modeling  $M_1$  as shown on the right, where  $I_n$  represents its flicker noise, determine the total output flicker noise voltage.

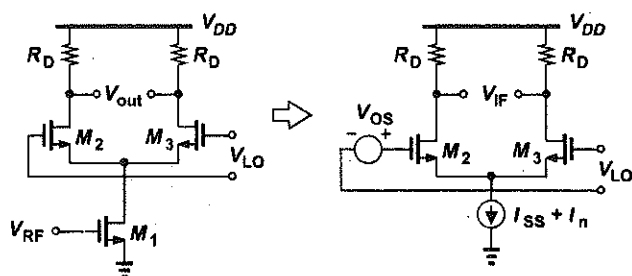(b) Can you roughly compare this result with the flicker noise contribution of  $M_2$  as derived in class?



(a) For zero crossing due to  $V_{OS}$ ,

$$V_{CM} + V_{p,LO} \sin \omega_{LO} t + V_{OS} = V_{CM} - V_{p,LO} \sin \omega_{LO} t$$

$$2V_{p,LO} \sin \omega_{LO} t = -V_{OS}$$

For  $t \rightarrow 0$

$$2V_{p,LO} \omega_{LO} t \approx -V_{OS}$$

$$|\Delta T| = \frac{|V_{OS}|}{2V_{p,LO} \omega_{LO}} = \frac{V_{OS}}{S_{LO}} \quad (\text{where } S_{LO} = 2V_{p,LO} \omega_{LO})$$

$$I_{out}(t) = \sum_{k=-\infty}^{\infty} \frac{2(I_{SS} + I_n) V_{OS}}{S_{LO}} \delta(t - k \frac{T_{LO}}{2})$$

$$\Rightarrow I_{out}(f) = \frac{4(I_{SS} + I_n)}{T_{LO} S_{LO}} V_{OS} \sum_{k=-\infty}^{\infty} \delta(f - 2kf_{LO})$$

For baseband component,  $k=0$ ,

$$I_{out}(f)|_{k=0} = \frac{I_{SS} + I_n}{\pi V_{p,LO}} \cdot V_{OS} \Rightarrow V_{out}(f)|_{k=0} = \frac{I_{SS} \cdot V_{OS} R_D}{\pi V_{p,LO}} + \frac{I_n V_{OS} R_D}{\pi V_{p,LO}}$$

Output offset

$$\boxed{\therefore V_{n1,out}(f) = \frac{I_n V_{OS} R_D}{\pi V_{p,LO}}}$$

(b) the flicker noise contribution of  $M_2$ :  $\frac{I_{SS} R_D}{\pi V_{p,LO}} V_{n2}(f) (=V_{n2,out})$

$$\frac{V_{n1,out}}{V_{n2,out}} = \frac{I_n V_{OS}}{I_{SS} V_{n2}} = \frac{g_{m1} V_{n1} V_{OS}}{I_{SS} V_{n2}} = \frac{2 V_{OS}}{(V_{GS} - V_{th})_1} \cdot \frac{V_{n1}}{V_{n2}} \quad (\text{where } g_{m1} = \frac{2 I_{SS}}{(V_{GS} - V_{th})_1})$$

Generally,  $(V_{GS} - V_{th})_1$  is larger than  $V_{OS}$  and hence  $V_{n1,out}$  is less than  $V_{n2,out}$ .

