

**EE215C**

**Midterm Exam**

**Winter 2010**

**Name:** ..... *Solutions* .....

**Time Limit: 2 Hours**

**Open Book, Open Notes, Calculators are allowed.**

1. *15*

2. *15*

3. *10*

4. *10*


**Total: *50***

1. Consider the amplifier shown below, where  $A_0$  is an ideal voltage amplifier, the transistor operates in saturation, and channel-length modulation and body effect are neglected. Neglect all device capacitances.

(a) Compute the input resistance,  $R_{in}$ .

(b) Compute the noise figure of the circuit with respect to a source impedance  $R_S$ . Assume  $A_0$  has an input-referred noise voltage of  $\overline{V_n^2}$ .

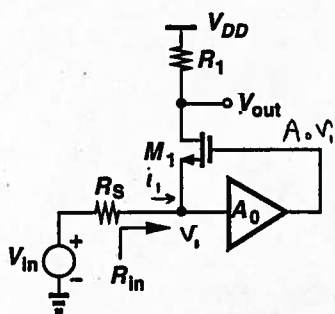(c) Simplify the NF expression if  $R_{in} = R_S$ .



$$(a) R_{in} = \frac{V_1}{i_1}$$

$$i_1 = -g_{m1} (A_0 - 1) V_1 \Rightarrow$$

$$R_{in} = \frac{-1}{g_{m1} (A_0 - 1)}$$


[3]

$$(b) \left. \overline{V_{n,out+1}^2} \right|_{R_1} = 4KT R_1$$

[2]

$$\left. \overline{V_{n,out+2}^2} \right|_{R_S} = \frac{4KT}{R_S} \cdot \left( \frac{R_S}{R_S + R_{in}} \cdot R_1 \right)^2$$

[2]

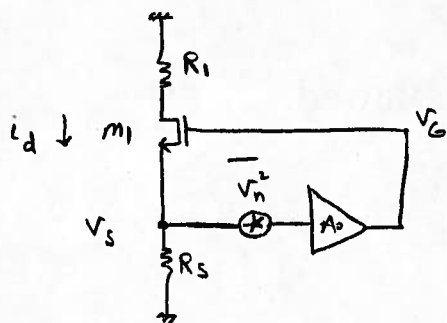

$$V_S = i_d \cdot R_S \quad V_G = (i_d R_S + V_n) A_0$$

$$\Rightarrow i_d = g_m V_{GS} = g_m [A_0 (V_n + i_d R_S) - i_d R_S]$$

$$\Rightarrow i_d = \frac{g_m A_0 V_n}{1 + g_m R_S - g_m A_0 R_S}$$

$$\Rightarrow \left. \overline{V_{n,out+3}^2} \right|_{A_0} = \overline{V_n^2} \frac{g_m^2 A_0^2 R_1^2}{[1 + g_m R_S (1 - A_0)]^2}$$

[2]

$$\left. \overline{V_{n,out+4}^2} \right|_{m_1} = \frac{4KT \gamma g_{m1}}{g_{m1}^2} \cdot \frac{1}{A_0^2} \cdot \frac{g_m^2 A_0^2 R_1^2}{[1 + g_m R_S (1 - A_0)]^2} = \frac{4KT \gamma g_m \cdot R_1^2}{[1 + g_m R_S (1 - A_0)]^2}$$

[2]

$$\overline{V_{n,tot}^2} = \sum \overline{V_{n,out+i}^2} \Rightarrow NF = \frac{\overline{V_{n,tot}^2}}{\overline{V_{n,RS}^2}}$$

$$\Rightarrow NF = 1 + \frac{(R_s + R_{in})^2}{R_s \cdot R_i} + \frac{\overline{V_n^2} \frac{g_m^2 A_o^2 R_i^2}{[1 + g_m R_s (1 - A_o)]^2}}{\frac{4KT}{R_s} \left( \frac{R_s R_i}{R_s + R_{in}} \right)^2} + \frac{\gamma g_m \cdot (R_s + R_{in})^2}{R_s [1 + g_m R_s (1 - A_o)]^2} \quad [1]$$

(C) if  $R_{in} = R_s = \frac{-1}{g_m (A_o - 1)} \Rightarrow$

$$NF = 1 + \frac{4R_s}{R_i} + \overline{V_n^2} \frac{g_m^2 A_o^2 R_s}{4KT} + \gamma g_m R_s \quad [3]$$

2. For the circuit shown below, we express the input-output characteristic as


$$I_{out} - I_0 = \alpha_1(V_{in} - V_0) + \alpha_2(V_{in} - V_0)^2 + \dots, \quad (1)$$

where  $I_0$  and  $V_0$  denote the bias values, i.e., the values in the absence of signals. We note that  $\partial I_{out} / \partial V_{in} = \alpha_1$  at  $V_{in} = V_0$  (or  $I_{out} = I_0$ ). Similarly,  $\partial^2 I_{out} / \partial^2 V_{in} = 2\alpha_2$  at  $V_{in} = V_0$  (or  $I_{out} = I_0$ ).

(a) Write a KVL around the input network in terms of  $V_{in}$  and  $I_{out}$  (with no  $V_{GS}$ ). Differentiate both sides implicitly with respect to  $V_{in}$ . You will need this equation in part (b). Noting that  $2\sqrt{KI_0} = g_m$ , where  $K = \mu_n C_{ox} W/L$ , find  $\partial I_{out} / \partial V_{in}$  and hence  $\alpha_1$ .

(b) Differentiate the equation obtained in part (a) with respect to  $V_{in}$  once more and compute  $\alpha_2$  in terms of  $I_0$  and  $g_m$ .

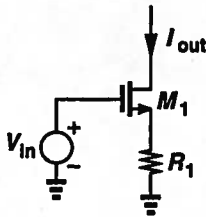(c) Determine the  $IP_2$  of the circuit.



$$(a) \quad \frac{1}{2} k (V_{in} - I_{out} R_1 - V_{th})^2 = I_{out}$$

$$V_{in} = R_1 I_{out} + V_{th} + \sqrt{\frac{2 I_{out}}{k}}$$

$$\frac{\partial V_{in}}{\partial I_{out}} = R_1 + \frac{1}{2} \left( \frac{2 I_{out}}{k} \right)^{-\frac{1}{2}} \cdot \frac{2}{k} \frac{\partial I_{out}}{\partial V_{in}}$$

$$1 = \left( R_1 + \sqrt{\frac{1}{2 I_{out} k}} \right) \frac{\partial I_{out}}{\partial V_{in}} \quad \#$$

$$\alpha_1 = \left. \frac{\partial I_{out}}{\partial V_{in}} \right|_{V_{in}=V_0} = \frac{g_m}{1 + g_m R_1} \quad \#$$

$$(b) \quad \frac{1}{\frac{\partial V_{in}}{\partial I_{out}}} = \frac{\partial I_{out}}{\partial V_{in}} \left[ -\frac{1}{2} \left( \frac{2 I_{out}}{k} \right)^{-\frac{1}{2}} \cdot 2k \frac{\partial I_{out}}{\partial V_{in}} \right] + \frac{1}{\alpha_1} \frac{\partial^2 I_{out}}{\partial^2 V_{in}}$$

$$0 = \alpha_1 \left[ -k \alpha_1 \frac{1}{g_m^3} \right] + \frac{1}{\alpha_1} \frac{\partial^2 I_{out}}{\partial^2 V_{in}}$$

$$\alpha_2 = \left. \frac{1}{2} \frac{\partial^2 I_{out}}{\partial^2 V_{in}} \right|_{V_{in}=V_0} = \frac{\alpha_1^3}{2 g_m^3} \frac{g_m^2}{2 I_0} = \frac{\alpha_1^3}{4 I_0 g_m} \quad \# \quad k = \frac{g_m^2}{2 I_0}$$

$$\left[ = \frac{k}{2(1 + g_m R_1)^3} \right]$$

$$(c) \quad (A_1 \cos \omega_1 t + A_2 \cos \omega_2 t)^2 = A_1^2 \cos^2 \omega_1 t + A_2^2 \cos^2 \omega_2 t + 2 A_1 A_2 \cos \omega_1 t \cos \omega_2 t$$


intermodulation term:  $A_1 A_2 [\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t]$

$$\alpha_1 \cdot IP_2 = \alpha_2 \cdot IP_2^2$$


$$IP_2 = \frac{\alpha_1}{\alpha_2} = \frac{4 I_0 g_m}{\alpha_1^2} = \frac{4 I_0 g_m}{\left( \frac{g_m}{1 + g_m R_1} \right)^2} \quad \#$$

$$\left( \text{or } \frac{2 g_m (1 + g_m R_1)^2}{k} \right)$$

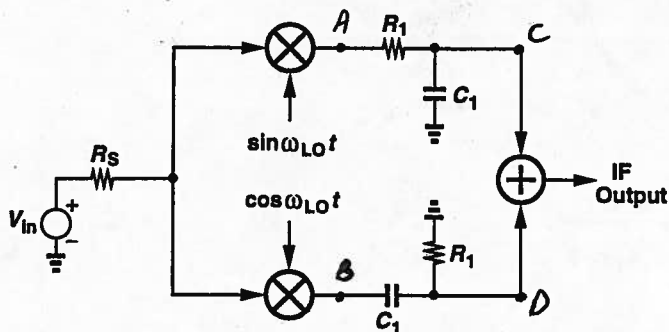3. The simplified Hartley architecture shown below incorporates mixers having a voltage conversion gain of  $A_{mix}$  and an infinite input impedance. Taking into account only the noise of the two resistors, compute the noise figure of the receiver with respect to a source resistance of  $R_S$  at an IF of  $1/(R_1 C_1)$ .




Assuming  $R_1 \gg R_{out}|_{mixer}$  :

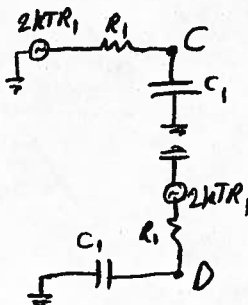

Note that we have used Two-sided

Noise spectrum.

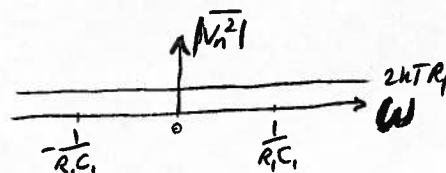


$$\overline{V_{n,c}}^2 = 2kTR_1 \left| \frac{1}{1 + R_1 C_1 j\omega} \right|^2$$

$$\overline{V_{n,D}}^2 = 2kTR_1 \left| \frac{1}{1 + R_1 C_1 j\omega} \right|^2$$


$$S = \pm j \left( \frac{1}{R_1 C_1} \right)$$

$$\overline{V_{n,c}}^2 = \overline{V_{n,D}}^2 = 2kTR_1 \left| \frac{1}{1 \pm j} \right|^2 = kTR_1 \Rightarrow \overline{V_{n,out}}^2 = \overline{V_{n,c}}^2 + \overline{V_{n,D}}^2$$

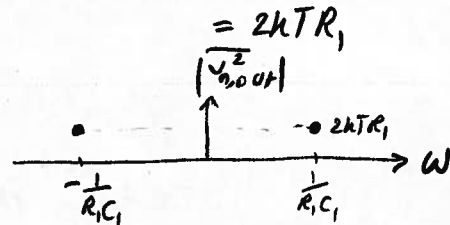


For noise of  $R_S$ , we should look into the noise at  $|\omega| = \omega_{LO} - \frac{1}{R_1 C_1}$ .



@ input :

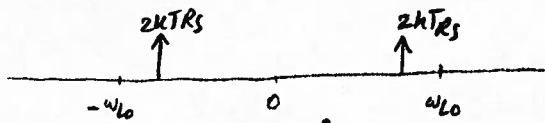


@ A :

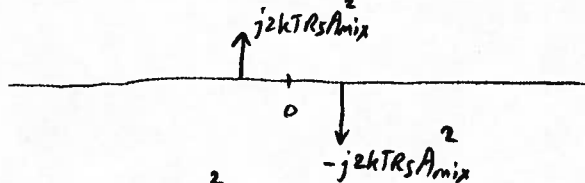

@ B :

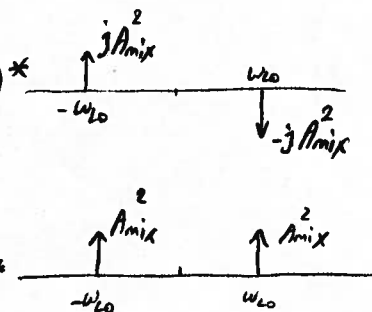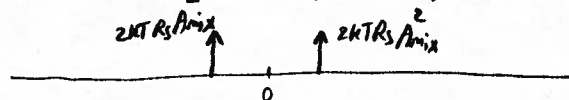

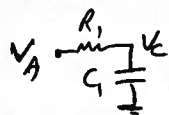


$$\frac{V_C}{V_A} = \frac{1}{R_1 C s + 1}$$

$$\left. \frac{V_C}{V_A} \right|_{j\frac{1}{R_1 C_1}} = \frac{1}{j+1}$$

$$\left. \frac{V_C}{V_A} \right|_{-j\frac{1}{R_1 C_1}} = \frac{1}{1-j}$$

@ C :

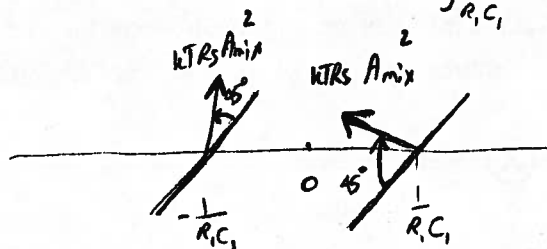


$$\frac{V_D}{V_B} = \frac{R_1 C s}{R_1 C s + 1}$$


$$\left. \frac{V_D}{V_B} \right|_{j\frac{1}{R_1 C_1}} = \frac{j}{j+1} = \frac{1}{1-j}$$

$$\left. \frac{V_D}{V_B} \right|_{-j\frac{1}{R_1 C_1}} = \frac{-j}{-j+1} = \frac{1}{1+j}$$

@ D :

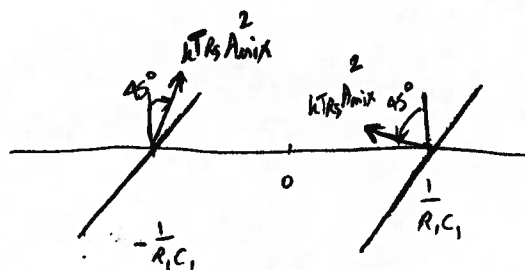

@ output

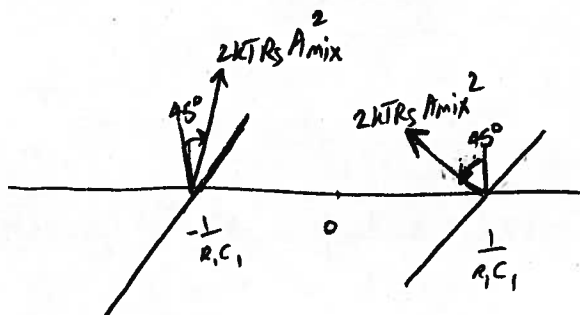


$$NF = \frac{2kTR_s A_{mix}^2 + 2kTR_1}{2kTR_s A_{mix}^2} = 1 + \frac{R_1}{R_s A_{mix}^2}$$

4. The sliding-IF architecture shown below is designed for the 11g band.

(a) Determine the image band.

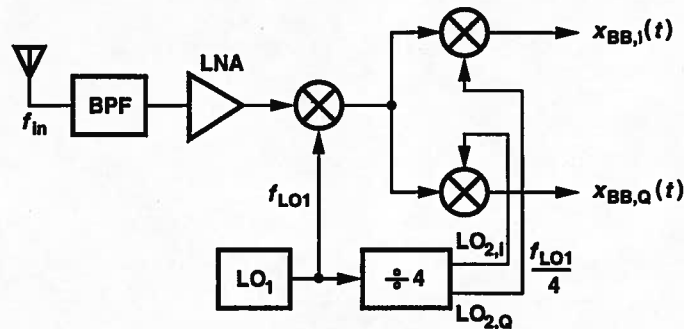(b) Determine interferer frequencies that can appear in the output baseband as a result of mixing with the third harmonic of the first LO or the third harmonic of the second LO.



a)  $f_{in} - f_{LO1} - \frac{f_{LO1}}{4} = 0 \quad \therefore f_{in} = \frac{5}{4} f_{LO1}$

Image Band =  $1.44 \text{ GHz} - 1.488 \text{ GHz}$

$f_{IM} = f_{LO1} - \frac{f_{LO1}}{4} = \frac{3}{4} f_{LO1}$

b) i) 3rd harmonic of the first LO

$$f_{INT} - 3f_{LO1} - \frac{f_{LO1}}{4} = 0 \quad \text{or} \quad 3f_{LO1} - f_{INT} - \frac{f_{LO1}}{4} = 0$$

$$\therefore f_{INT} = \frac{11}{4} f_{LO1} \quad \text{or} \quad \frac{13}{4} f_{LO1} \quad : \quad 5.28 \text{ GHz}, 6.24 \text{ GHz}$$

ii) 3rd harmonic of the second LO

$$f_{INT} - f_{LO1} - \frac{3}{4} f_{LO1} = 0 \quad \text{or} \quad f_{LO1} - f_{INT} - \frac{3}{4} f_{LO1} = 0$$

$$\therefore f_{INT} = \frac{1}{4} f_{LO1} \quad \text{or} \quad \frac{7}{4} f_{LO1} \quad : \quad 0.48 \text{ GHz}, 3.36 \text{ GHz}$$



EE215C

Midterm Exam

Winter 2009

Name: Solutions.....

Time Limit: 2 Hours

Open Book, Open Notes


1. 10

2. 15

3. 15

4. 10

Total: 50

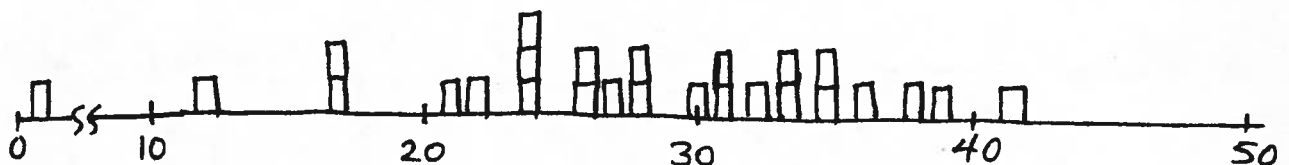

Avg. = 27/50

1. Consider the cascade of two nonlinear stages. The first stage is described by  $y = \alpha_1 x + \alpha_3 x^3$  and the second by  $y = \beta_1 x + \beta_3 x^3$ .

- 5 (a) Determine the overall input 1-dB compression point of the cascade in terms of the 1-dB compression points of each stage.
- 5 (b) Determine the output 1-dB compression point of the cascade in terms of  $\alpha_j$  and  $\beta_j$ .

$$(a) \quad A_{-1dB,1} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|} \quad (\text{Stage 1})$$

$$A_{-1dB,2} = \sqrt{0.145 \left| \frac{\beta_1}{\beta_3} \right|} \quad (\text{Stage 2})$$

$$\text{After cascading: } y = \beta_1 (\alpha_1 x + \alpha_3 x^3) + \beta_3 (\alpha_1 x + \alpha_3 x^3)^3$$

$$\Rightarrow y = (\beta_1 \alpha_1) x + (\beta_1 \alpha_3 + \beta_3 \alpha_1^3) x^3 + \dots$$

$$\Rightarrow A_{-1dB,tot} = \sqrt{0.145 \left| \frac{\alpha_1 \beta_1}{\beta_1 \alpha_3 + \beta_3 \alpha_1^3} \right|} \Rightarrow \frac{1}{A_{-1dB,tot}^2} = \frac{1}{0.145} \left[ \frac{\alpha_3}{\alpha_1} + \alpha_1^2 \frac{\beta_3}{\beta_1} \right] \quad [2]$$

$$\Rightarrow \frac{1}{A_{-1dB,tot}^2} = \frac{1}{A_{-1dB,1}^2} + \frac{\alpha_1^2}{A_{-1dB,2}^2} \quad [2]$$


$$(b) \quad A_{-1dB,tot,in} = \sqrt{0.145 \left| \frac{\alpha_1 \beta_1}{\beta_1 \alpha_3 + \beta_3 \alpha_1^3} \right|} \quad \text{at the input} \quad [3]$$

$$\text{ideal gain} = \alpha_1 \beta_1$$

$$20 \log (\alpha_1 \beta_1 A_{-1dB,tot,in}) - 1 \text{ dB} = 20 \log (A_{-1dB,tot,out})$$


$$\Rightarrow 20 \log \left( \frac{A_{-1dB,tot,out}}{\alpha_1 \beta_1 A_{-1dB,tot,in}} \right) = -1 \text{ dB} \quad [2]$$

$$\Rightarrow A_{-1dB,tot,out} = 10^{-1/20} \cdot \alpha_1 \beta_1 \sqrt{0.145 \left| \frac{\alpha_1 \beta_1}{\beta_1 \alpha_3 + \beta_3 \alpha_1^3} \right|} \quad \text{at the output}$$

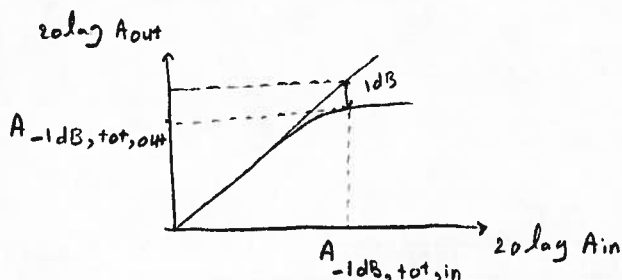

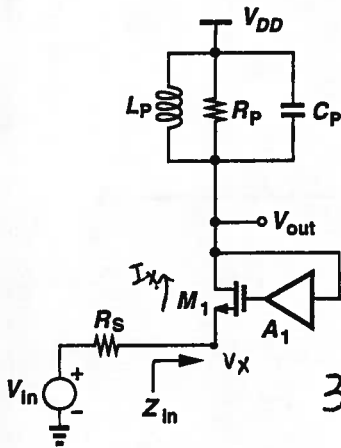2. Consider the circuits shown below, where an ideal voltage amplifier with a gain of  $A_1$  returns a fraction of the output to the gate of the input transistor. Neglect channel-length modulation, body effect, and other capacitances.

- 5 (a) Compute the input impedance. Can the real part become negative at any frequency? Explain in detail.  
 5 (b) Compute the noise figure with respect to a source resistance of  $R_S$  at the resonance frequency of the tank.  
 5 (c) Simplify the noise figure expression if the input is matched at the resonance frequency of the tank.



$$a) g_m (A_1 V_{out} - V_x) = -V_{out} \left( \frac{1}{sL_P} + \frac{1}{R_P} + sC_P \right)$$

$$V_{out} = \frac{g_m V_x}{g_m A_1 + \frac{1}{sL_P} + \frac{1}{R_P} + sC_P}$$

$$I_x = V_{out} \left( \frac{1}{sL_P} + \frac{1}{R_P} + sC_P \right)$$

$$= \frac{g_m V_x}{g_m A_1 + \frac{1}{sL_P} + \frac{1}{R_P} + sC_P} \left( \frac{1}{sL_P} + \frac{1}{R_P} + sC_P \right)$$

$$3 \quad Z_{in} = \frac{V_x}{I_x} = \frac{g_m A_1 + \frac{1}{sL_P} + \frac{1}{R_P} + sC_P}{g_m \left( \frac{1}{sL_P} + \frac{1}{R_P} + sC_P \right)} \quad \#$$

$$\text{real-} Z_{in} = \frac{1}{g_m} \frac{\left( g_m A_1 + \frac{1}{R_P} \right) \frac{1}{R_P} + \left( \omega C_P - \frac{1}{\omega L_P} \right)^2}{\left( \frac{1}{R_P} \right)^2 + \left( \omega C_P - \frac{1}{\omega L_P} \right)^2}$$

$$2 \quad \because \left( \omega C_P - \frac{1}{\omega L_P} \right)^2 > 0 \text{ at all frequencies, } \Rightarrow \text{real-} Z_{in} > 0$$

real- $Z_{in}$  never becomes negative. #

5b) Output noise from  $P_S$ :  $4kTR_S \Delta^2_{total}$

Output noise from  $R_P$ :  $\frac{4kT}{R_P} R_{out}$

Output noise from  $M_1$ :  $\frac{4kT}{g_m} \left( \frac{g_m}{1+g_m R_S} \right)^2 R_{out}$

$$\frac{P_{out}}{\Delta^2_{total}} = \frac{1}{G_m^2} = \left( \frac{1+g_m R_S}{g_m} \right)^2$$

$$F = \frac{\text{output noise} / \Delta^2_{total}}{4kTR_S} = 1 + \frac{1}{R_P R_S} \frac{R_{out}}{\Delta^2_{total}} + \frac{\delta}{g_m R_S} \left( \frac{g_m}{1+g_m R_S} \right)^2 \frac{P_{out}}{\Delta^2_{total}}$$

$$= 1 + \frac{1}{R_P R_S} \left( \frac{1+g_m R_S}{g_m} \right)^2 + \frac{\delta}{g_m R_S} = 1 + \frac{1}{R_P g_m^2 R_S} + \frac{R_S}{R_P} + \frac{\delta}{g_m R_S} \quad \#$$

$$NF = 10 \log(F) \quad \#$$





5 (c) If  $Z_{in} = R_S$  at resonate  $f \Rightarrow Z_{in} = \frac{1}{g_m} (1 + g_m A_1 R_P) = R_S \quad (2)$

$$\Rightarrow F = 1 + \frac{1}{R_P g_m (1 + g_m A_1 R_P)} + \frac{1 + g_m A_1 R_P}{g_m R_P} + \frac{\delta}{A_1 g_m A_1 R_P} \quad \#$$

(  $\because NF$  is dominated by the term with  $\delta$  in this case )  
 $\therefore A_1$  helps reduce the noise.

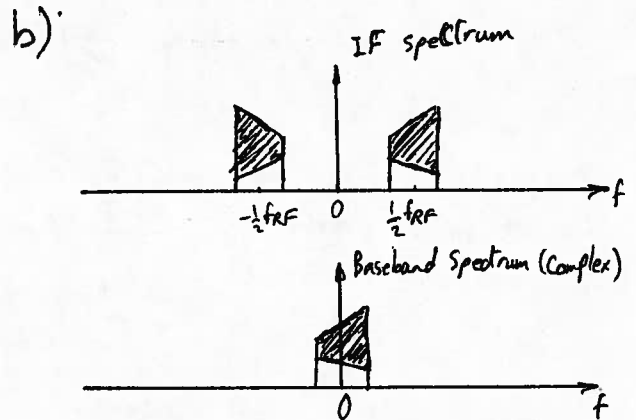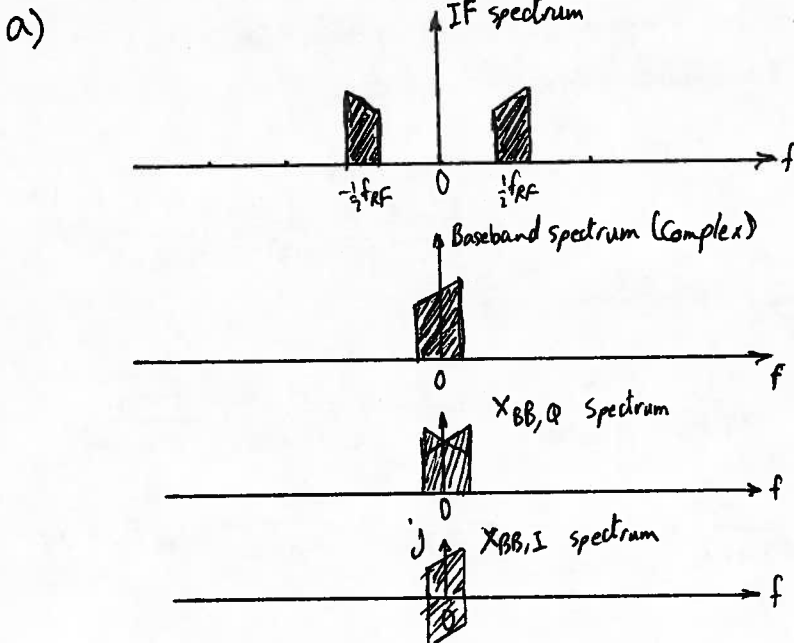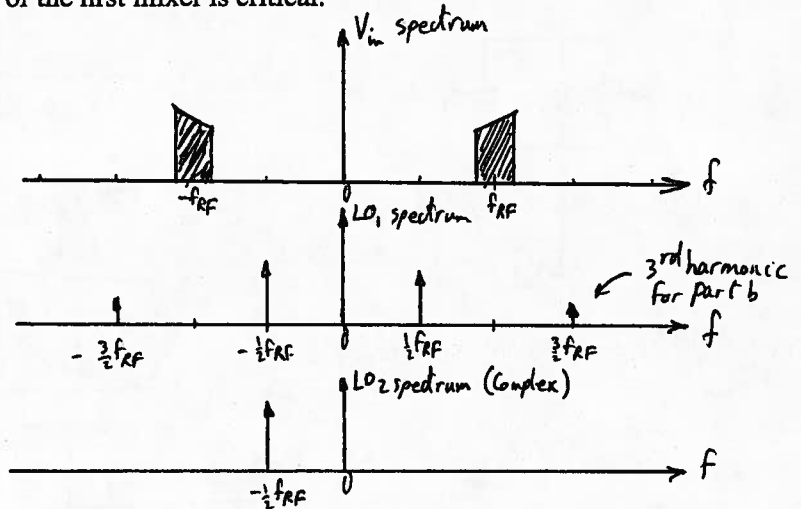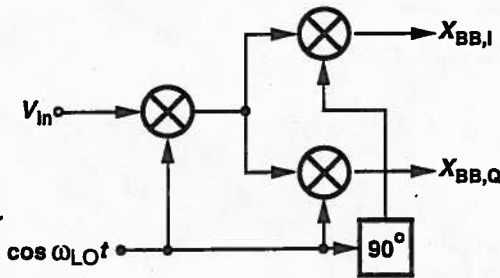3. The receiver architecture shown below operates with an LO frequency equal to half of the input carrier frequency. Assume the input has an asymmetrically-modulated spectrum.

- 5 (a) Plot the IF and baseband spectra assuming ideal mixers.
- 5 (b) Now suppose the first mixer experiences hard switching and introduces the third harmonic of the LO, i.e., it mixes the RF input with an LO of the form  $\cos \omega_{LO} t + \alpha \cos(3\omega_{LO} t)$ . Plot the IF spectrum and explain whether or not this architecture operates well with asymmetrically-modulated inputs.
- 5 (c) Explain why the flicker noise at the input of the first mixer is critical.




so this architectures will not work well with asymmetrically-modulated inputs in the presence of first LO third harmonic. This is because the third harmonic folds the signal on itself corrupting the information.


- c) The flicker noise is present at DC which is of equal distance from the first LO as the signal. The first LO will thus upconvert it to IF and this corrupts the signal. Also, this is in the very beginning of the RF receiver where noise is so critical and gets amplified.

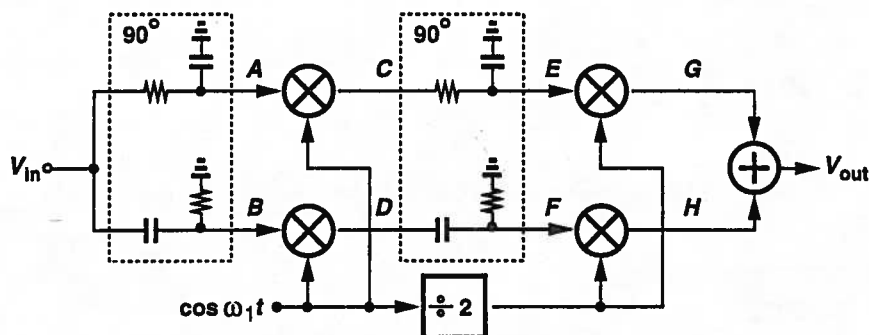4. An engineer constructs the receiver shown below and chooses  $\omega_1$  such that the second IF is zero. (Only the I branch is shown for the sake of simplicity.) The RC-CR networks are inserted to perform a  $90^\circ$  phase shift at the frequency of interest.

- 5 (a) Does the receiver reject the image? Explain with the aid of spectra at various points in the chain.
- 5 (b) Does the receiver reject the image with respect to the third harmonic of the LO, i.e., the mirror image of  $\omega_{in}$  with respect to  $3\omega_1$ ? Explain with the aid of spectra at various points in the chain.





#### 4. Simplified ckt Diagram

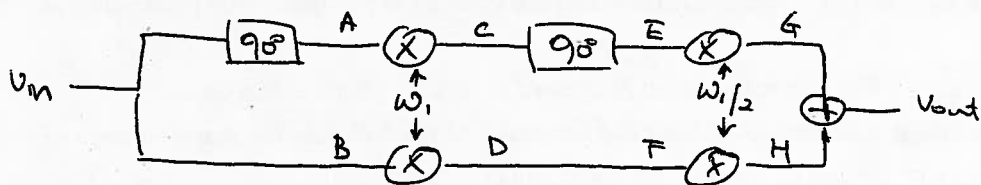

i) for zero IF,


$$\omega_{in} = \omega_1 + \frac{\omega_1}{2} = \frac{3}{2}\omega_1$$

ii) 90° phase shift,

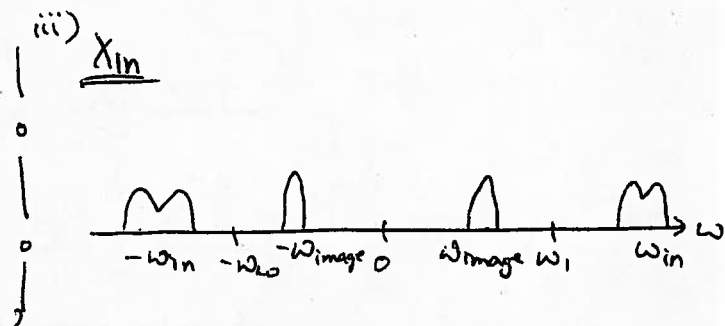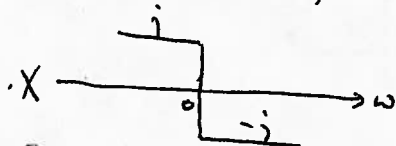


a)

$X_A$

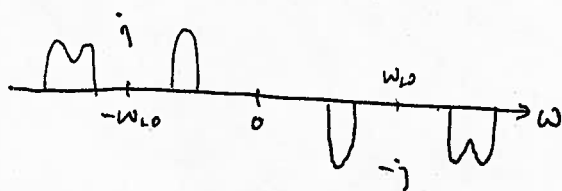


$X_B = X_{in}$


$X_C$

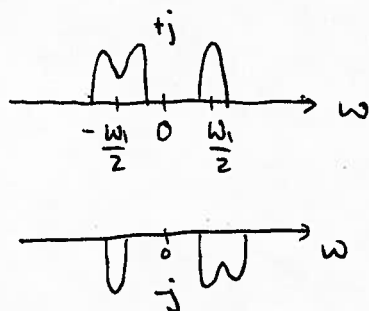

$X_D$

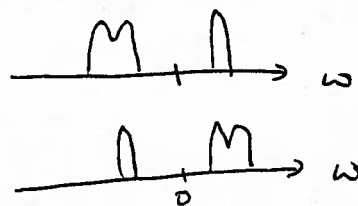


$X_E$

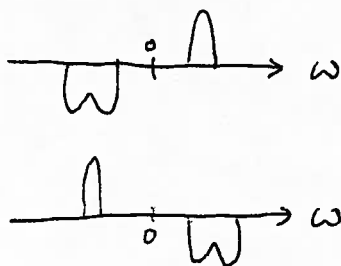


$X_F = X_D$


$X_G$

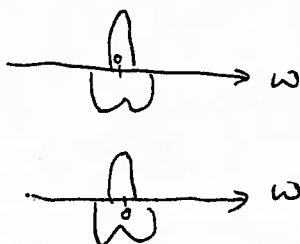

$X_H$

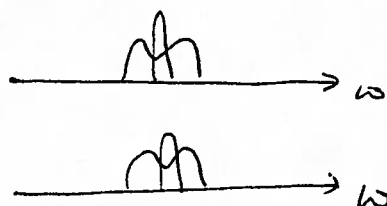

$\therefore \underline{X_{out}}$

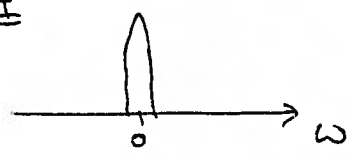



The signal will be rejected,

However if  $\omega_m = \frac{1}{2} \omega_1$ ,




the image will be rejected, but only <sup>magnitude</sup> to some extent, due to the mismatch between the upper / lower branch.

(RC-CR : 90° phase shift for all freq,  
same Amplitude response only at  $1/R_C$



(b)  $\underline{X_{in}}$

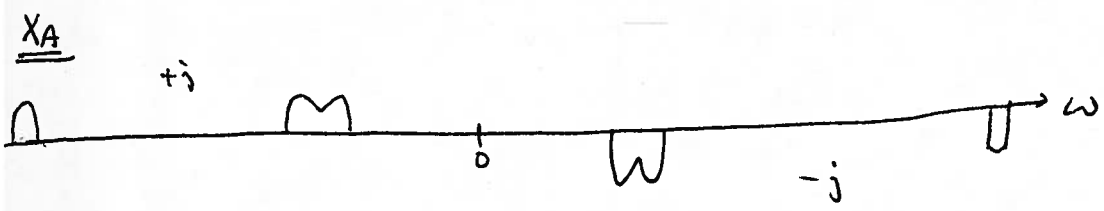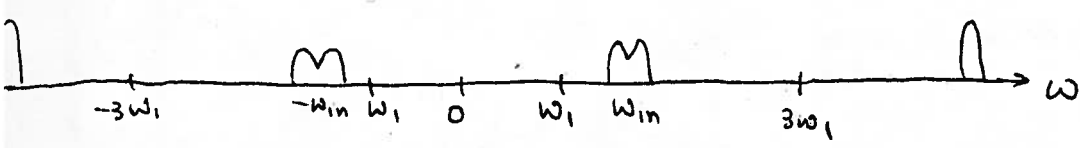


$\underline{X_B = X_{in}}$

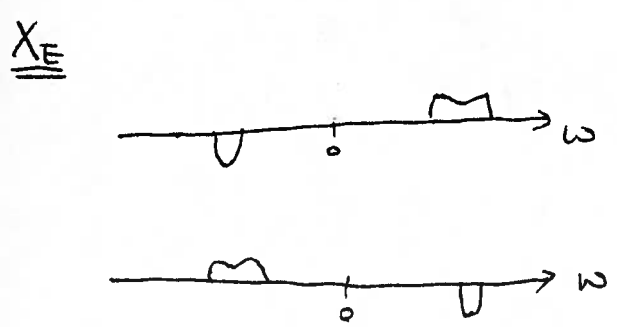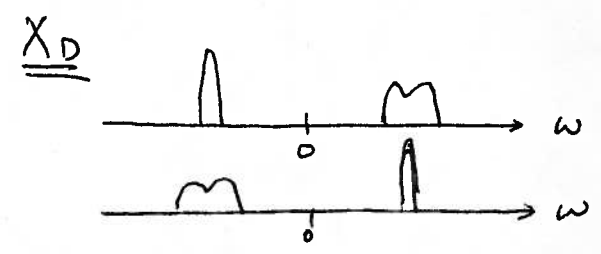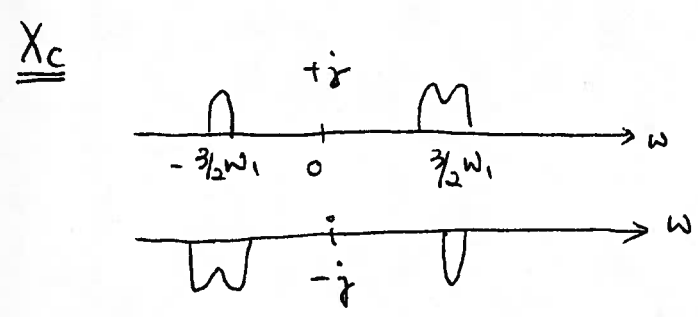

$\underline{X_F = X_D}$

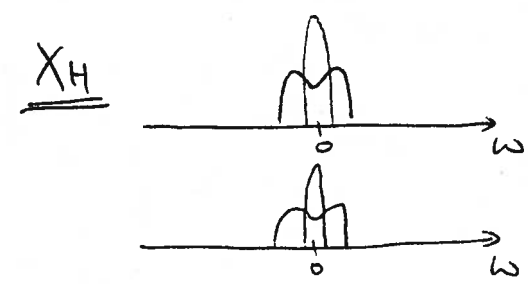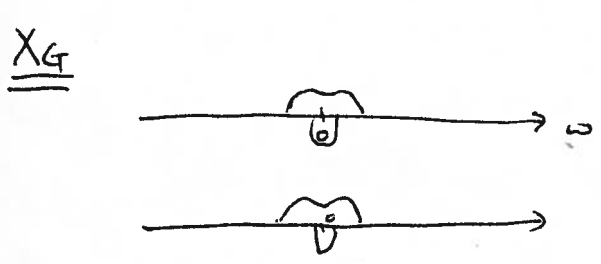

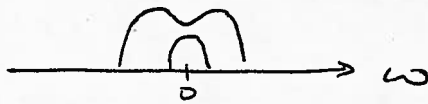$\therefore \underline{\underline{X_{out}}}$



The image would be attenuated (not fully rejected) because of the frequency dependent magnitude mismatch between upper/lower branch.