

EE215C

Final Exam

Winter 2009

Name: *Solutions*

Time Limit: 3 Hours

Open Book, Open Notes

1. 20


2. 10

3. 10

4. 10

5. 15


Total: 65

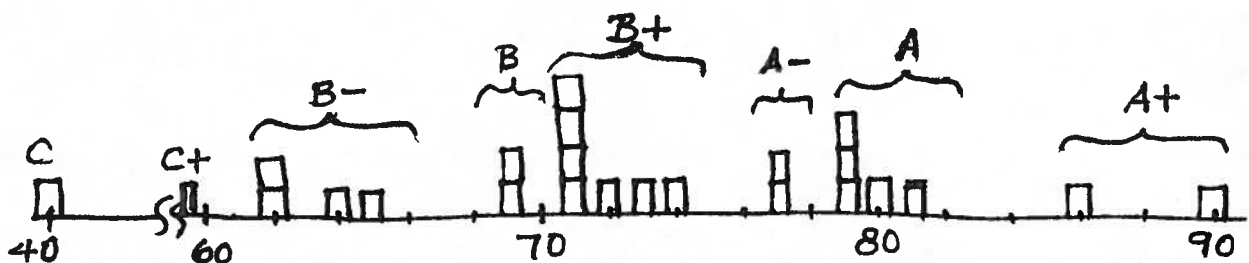

1. Consider the active mixer shown below, where all other capacitances are neglected and no transistor enters the triode region. Also, channel-length modulation and body effect are negligible.

(a) Suppose M_2 is on and M_3 is off. Derive an expression for the small-signal drain current of M_2 due to the thermal noise of M_2 . Plot the spectrum of the drain current. Neglect all other sources of noise.

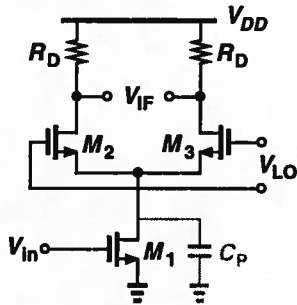
(b) Now suppose the impedance of C_P is much larger than $1/g_{m2}$ at the frequencies of interest, and the LO is applied with 50% duty cycle. If M_2 and M_3 switch abruptly, and only the first and third harmonics of the LO are considered, explain in detail how the thermal noise of M_2 appears at IF. Sketch the IF noise spectrum due to the first and third harmonics of the LO. Neglect all other sources of noise.




$$\overline{i_{dn}}^2 = 4kTg_{m2} \left| \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{j\omega C_P}} \right|^2$$

$$= 4kTg_{m2} \frac{\omega^2 C_P^2}{\omega^2 C_P^2 + g_{m2}^2} \quad (6)$$


spectrum:

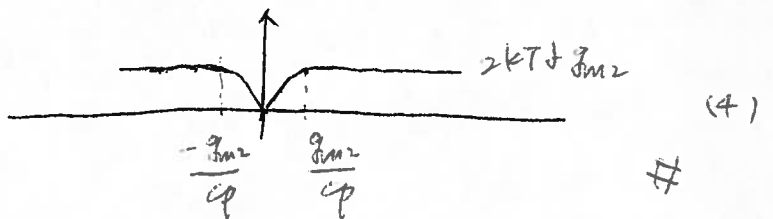


b) time domain: square wave x noise

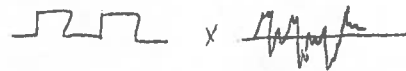

=> frequency domain:

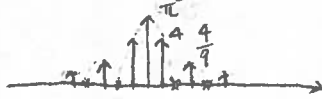

for $+f_{LO}$

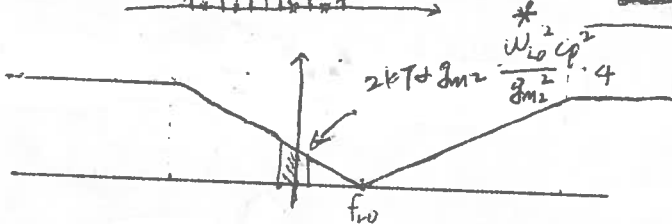


$$\because \frac{1}{\omega C_P} \gg \frac{1}{g_{m2}}$$


$$\Rightarrow \omega C_P \ll g_{m2}$$

$$\therefore \overline{i_{dn}}^2 = 4kTg_{m2} \frac{(\omega C_P)^2}{g_{m2}^2}$$


for $-f_{LO}$

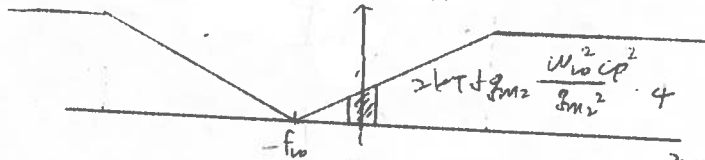


for $3f_{LO}$

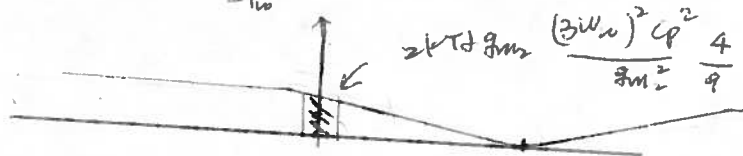

for $-3f_{LO}$

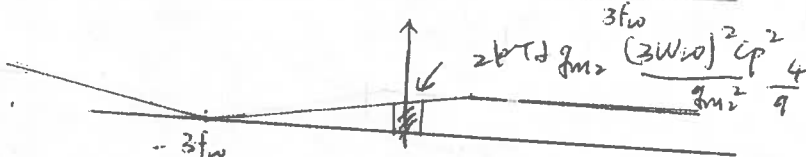
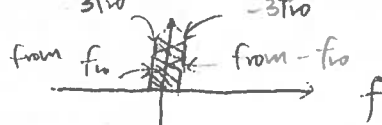
$$\therefore \text{the total noise at IF} \approx 2kTg_{m2} \frac{\omega_{LO}^2 C_P^2}{g_{m2}^2} \cdot 16 \quad \#$$




the 3rd harmonic contribute the same noise as the 1st

2. A student considers the arrangement shown on the left, where C_{GS} introduces LO leakage at the input and hence a dc component at the output. (Note that the capacitor does not carry a dc current.) The student then decides that the arrangement on the right is free from dc offsets, reasoning that a dc voltage, V_{ds} , at the output would require a dc current, V_{dc}/R_L , through R_L and hence an equal current through R_S . But this is impossible because a dc current through R_S gives rise to a negative voltage at node X.

(a) Explain in detail whether the student's conjecture is correct and why.

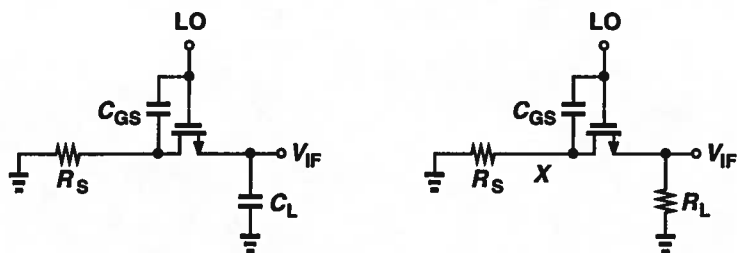
(b) Neglecting C_{GS} , calculate the voltage conversion gain of the circuit on the right. Assume a square-wave LO with 50% duty cycle. Also, assume the switch has an on-resistance of R_{on} .



(a) The flaw in the student's reasoning is that a dc current at the output requires a dc current at the input. In other words, KCL only holds for all of the frequency components summed together - not for each individual component. Thus, both circuits suffer from dc offsets.

(b) The mixer operates as an ideal return-to-zero topology, except that R_{on} and R_L attenuate the signal when the switch is on. That is, the input signal is multiplied by a square wave toggling between 0 and $\frac{R_L}{R_L + R_{on} + R_S}$. The conversion gain is therefore equal to $\frac{1}{\pi} \frac{R_L}{R_L + R_{on} + R_S}$.

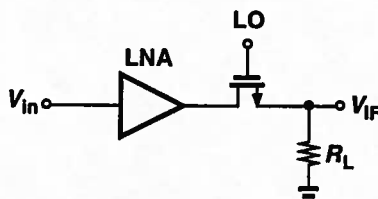3. Shown below is part of a direct-conversion receiver. Suppose the LNA input-output characteristic can be expressed as $y(t) = \alpha_1 x(t) + \alpha_2 x^2(t)$. If the mixer switches abruptly with a 50% duty cycle and if R_L is much greater than the on-resistance of the switch and the output resistance of the LNA, compute the IP_2 of the receiver.



The LO signal can be represented as $\frac{1}{2} + \sum_{n=1}^{\infty} \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\omega t)$

for a two tone test we have $V_{in} = A(\cos \omega_1 t + \cos \omega_2 t)$

\therefore we have $V_{IF} = \left[\alpha_1 A (\cos \omega_1 t + \cos \omega_2 t) + \alpha_2 A^2 (\cos \omega_1 t + \cos \omega_2 t)^2 \right] \left[\frac{1}{2} + \frac{2}{\pi} \cos(\omega_{LO} t) + \dots \right]$

for ω_2 slightly higher than ω_1 , $(\omega_2 - \omega_1)$ component at the output of the LNA appears at the output of the mixer multiplied by its DC gain and located close to DC.

$\omega_2 - \omega_1$: @ LO output $\alpha_2 A^2 \cos(\omega_2 - \omega_1)$

@ Mixer output $\frac{1}{2} \alpha_2 A^2 \cos(\omega_2 - \omega_1)$


This resides in the same band as the converted RF signal $\alpha_1 A$

At the IP_2 point $\frac{\alpha_1 A_{IP_2}}{\pi} = \frac{\alpha_2 A_{IP_2}^2}{2}$


$\therefore A_{IP_2} = \frac{\alpha_1}{\alpha_2} \frac{2}{\pi}$

4. Consider the simple type-I PLL shown below. Assume the loop is locked.

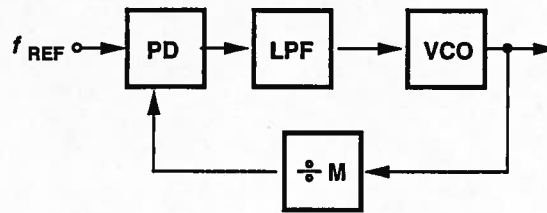- (a) If the input frequency is known, describe in detail how you compute the control voltage and the phase error (between the two inputs of the PD).
- (b) If the input frequency changes by $\Delta\omega$, compute the change in the phase error.



(a)

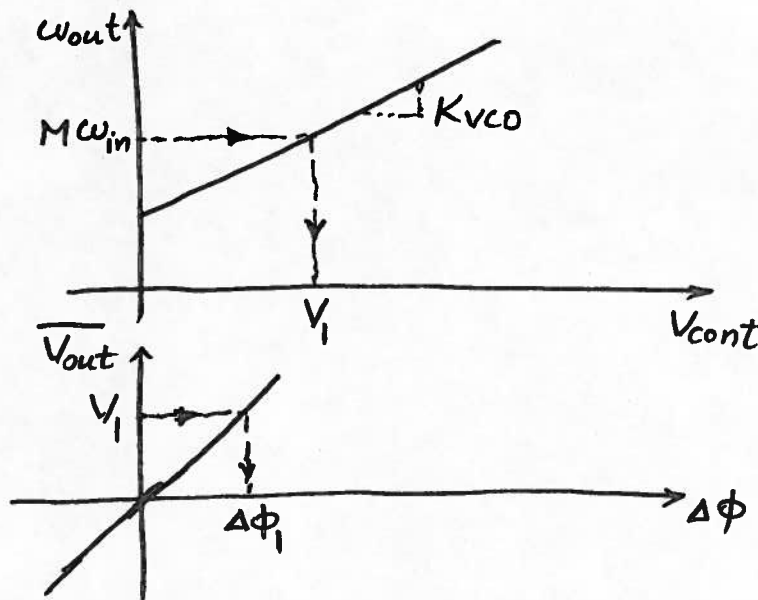


- (b) If the input frequency changes by $\Delta\omega$, ω_{out} changes by $M\Delta\omega$ and the control voltage by $\frac{M\Delta\omega}{K_{VCO}}$. Thus, the input phase error changes by $\frac{M\Delta\omega}{K_{VCO}K_{PD}}$.

5. A type-I PLL is shown below, where the control voltage experiences a sinusoidal ripple with a frequency of f_{REF} and a peak amplitude of V_r . Assume the loop is locked.

(a) Explain the difference between a harmonic and a sideband.

(b) Using the narrow-band FM approximation, determine the spectrum at point A.

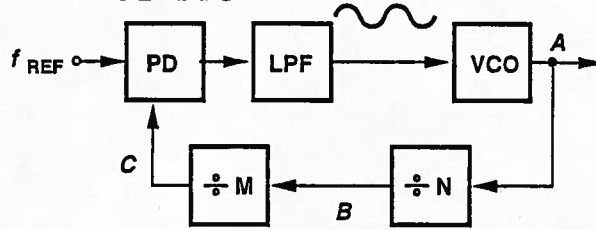(c) Now determine the spectrum at nodes B and C.



(a) HARMONICS - A frequency component in a spectrum that is an integer multiple of the fundamental frequency. Appears when a sinusoid is applied to a non-linear system.

SIDEBANDS - Deterministic frequency component that appears around the carrier frequency. A generic example are tones produced by a modulation process of the original signal.

(b) (NOTE) Narrowband FM Approx.


$$x_{FM}(t) = A_c \cos \left[\omega_c t + m \int_{-\infty}^t x_{BB}(t) dt \right] \approx A_c \cos \omega_c t - A_c \sin \omega_c t \int x_{BB}(t) dt.$$

given $x_{BB}(t) = V_r \cos(\omega_{REF} t)$, $\omega_{REF} = 2\pi f_{REF}$

$$x_{FM}(t) \approx A_c \cos(\omega_c t) - \frac{A_c V_r m}{\omega_{REF}} \sin(\omega_c t) \sin(\omega_{REF} t)$$

$$= A_c \cos(\omega_c t) - \frac{A_c V_r m}{2\omega_{REF}} \cos(\omega_c - \omega_{REF})t + \frac{A_c V_r m}{2\omega_{REF}} \cos(\omega_c + \omega_{REF})t$$

(SPECTRUM @ A)

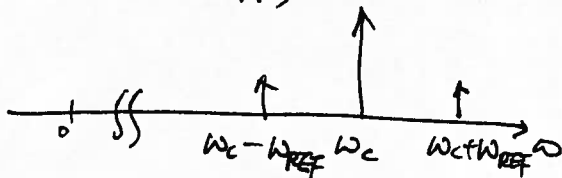


(c) When FM modulated signal is applied to a divider, ($\div N$)


fundamental: $\text{freq} \div N$

sideband: $\text{Amp} \div N$

\therefore @ B

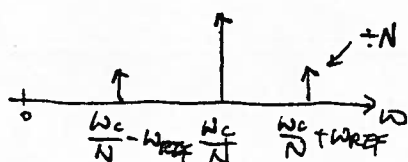

@ C

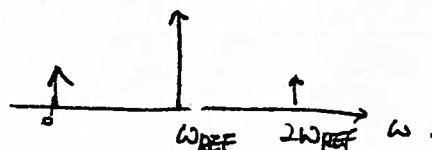

$$x_{FM} = A_c \cos \left(\underbrace{\omega_c t + m \int x_{BB}(t) dt}_{\div N} \right)$$

EE215C

Final Exam

Winter 2010

Name: *Solutions*

Time Limit: 3 Hours

Open Book, Open Notes

1. 10

2. 10

3. 10


4. 10

Total: 40

1. The circuit shown below is a mixer used in traditional microwave design. Assume when M_1 is on, it has an on-resistance of R_{on1} . Also, assume abrupt edges and a 50% duty cycle for the LO and neglect channel-length modulation and body effect.

(a) Compute the voltage conversion gain of the circuit. Assume M_2 does not enter the triode region and denote its transconductance by g_{m2} .

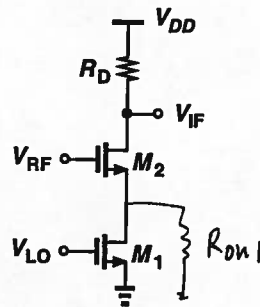(b) If R_{on1} is very small, determine the IP_2 of the circuit. Assume M_2 has an overdrive of $V_{GS0} - V_{TH}$ in the absence of signals (when it is on).



$$(a) \quad \frac{-R_D}{\frac{1}{g_{m2}} + R_{on1}} \times \frac{2}{\pi} \times \frac{1}{2} \text{ (for single-ended)}$$

$$= \frac{-R_D}{\frac{1}{g_{m2}} + R_{on1}} \times \frac{1}{\pi} \quad \#$$

(b)

for 2 tone test $V_m = V_0 \cos \omega_1 t + V_0 \cos \omega_2 t$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS0} - V_{th} + V_0 \cos \omega_1 t + V_0 \cos \omega_2 t)^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS0}^2 + V_{th}^2 + V_0^2 \cos^2 \omega_1 t + V_0^2 \cos^2 \omega_2 t$$

$$+ V_0^2 \cos(\omega_1 - \omega_2)t + V_0^2 \cos(\omega_1 + \omega_2)t - 2V_{GS0}V_{th}$$

$$+ 2V_0 V_{GS0} \cos \omega_1 t + 2V_0 V_{GS0} \cos \omega_2 t - 2V_0 V_{th} \cos \omega_1 t$$

$$- 2V_0 V_{th} \cos \omega_2 t)$$

the gain for $\omega_1 - \omega_{LO}$ & $\omega_2 - \omega_{LO}$ at $V_{IF} = \frac{1}{\pi} \times \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot 2(V_{GS0} - V_{th}) R_D$


the gain for $\omega_1 - \omega_2$ at $V_{IF} = \frac{1}{2} \times \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot R_D$

$$IIP2 = \frac{4(V_{GS0} - V_{th})}{\pi} \quad \#$$

2. Consider the active mixer shown below, where the LO has abrupt edges and a 50% duty cycle. Also, channel-length modulation and body effect are negligible. The load resistors exhibit mismatch but the circuit is otherwise symmetric. Assume M_1 carries a bias current of I_{SS} .

(a) Determine the output offset voltage.

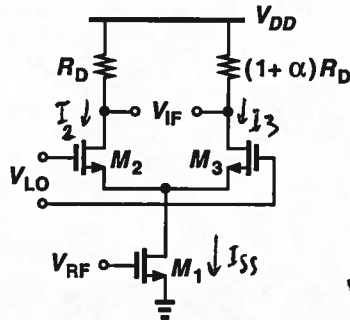(b) Determine the IP_2 of the circuit in terms of the overdrive and bias current of M_1 .



$$I_2 = I_{SS} \times S(t)$$

$$S(t): \text{ [50% duty cycle square wave] }$$

$$I_3 = I_{SS} \times (1 - S(t))$$

$$1 - S(t): \text{ [50% duty cycle square wave] }$$

$$V_{IF} = (1 + \alpha) R_D I_3 - R_D I_2 = R_D I_{SS} (1 - 2S(t)) + \alpha R_D I_{SS} (1 - S(t))$$

$$\left. \frac{V_{IF}}{DC} \right| = \alpha R_D I_{SS} \times \frac{1}{2}$$

b) Two-tone test: $V_{RF} = V_1 \cos \omega_1 t + V_1 \cos \omega_2 t + V_{GS0}$

$$I_{SS} = \overbrace{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1}^K \left(V_1 \cos \omega_1 t + V_1 \cos \omega_2 t + V_{GS0} - V_{TH} \right)^2$$

$$= K \left\{ V_1^2 \left[\frac{1 + \cos 2\omega_1 t}{2} + \frac{1 + \cos 2\omega_2 t}{2} + \underbrace{\cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t}_{\text{Beat Component}} \right] + (V_{GS0} - V_{TH})^2 + 2(V_{GS0} - V_{TH}) V_1 \left[\underbrace{\cos \omega_1 t + \cos \omega_2 t}_{\text{fundamentals}} \right] \right\}$$

$$\left. \frac{V_{IF}}{\text{fundamental}} \right| = K 2(V_{GS0} - V_{TH}) V_1 \times R_D \left(\frac{2}{\pi} + \alpha \frac{1}{\pi} \right) \left[\cos(\omega_1 - \omega_2)t + \cos(\omega_2 - \omega_1)t \right]$$

$$\left. \frac{V_{IF}}{\text{Beat}} \right| = K V_1^2 \times \alpha R_D \times \frac{1}{2} \times \cos(\omega_1 - \omega_2)t$$


$$\omega_{ASP2}: \left. \frac{V_{IF}}{\text{fundamental}} \right| = \left. \frac{V_{IF}}{\text{Beat}} \right|$$

$$\Rightarrow A_{SP2} = \frac{4}{\alpha} \left(\frac{2}{\pi} + \alpha \frac{1}{\pi} \right) \underbrace{\left(V_{GS0} - V_{TH} \right)}_{\text{overdrive}} = \left(\frac{8}{\alpha \pi} + \frac{4}{\pi} \right) (V_{GS0} - V_{TH})$$

3. In the VCO circuit shown below, the voltage dependence of each varactor can be expressed as $C_{var} = C_0(1 + \alpha_1 V_{var})$, where V_{var} denotes the average voltage across the varactor. Use the narrowband FM approximation in this problem. Also, neglect all other capacitances and assume the circuit oscillates at a frequency of ω_0 for the given value of V_{cont} . The dc drop across the inductors is negligible.

(a) Compute the "gain" from I_{SS} to the output frequency, ω_{out} . That is, assume I_{SS} changes by a small value and calculate the voltage change across the varactors and hence the change in the output frequency.

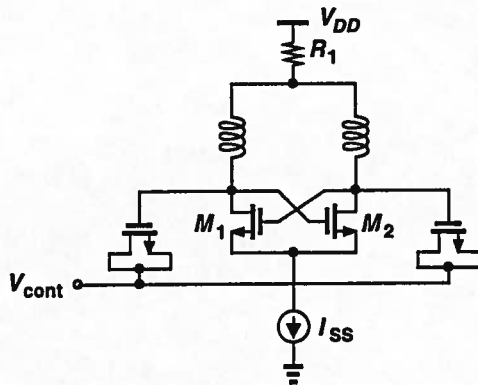(b) Assume I_{SS} has a noise component that can be expressed as $I_n \cos \omega_n t$. Using the result found in (a), determine the frequency and relative magnitude of the resulting output sidebands of the oscillator.



(a)

$$\omega_{out} = \frac{1}{\sqrt{LC_{eq}}} = \frac{1}{\sqrt{LC_0(1 + \alpha_1 V_{var})}}$$

$$\approx \frac{1}{\sqrt{LC_0}} \left(1 - \frac{\alpha_1 V_{var}}{2} \right) = \omega_0 \left(1 - \frac{\alpha_1 V_{var}}{2} \right)$$

$$\therefore \frac{\partial \omega_{out}}{\partial I_{SS}} = \frac{\partial \omega_{out}}{\partial V_{var}} \cdot \frac{\partial V_{var}}{\partial I_{SS}} = \left(-\frac{\alpha_1 \omega_0}{2} \right) \cdot (-R_1) = \frac{\alpha_1 R_1 \omega_0}{2}$$

(b) Using NB Approx.

$$V_{out}(t) = A \cos \left(\omega_0 t + \frac{\alpha_1 \omega_0 R_1}{2 \omega_n} \cdot I_n \sin(\omega_n t) \right)$$


$$\approx A \cos(\omega_0 t) - \frac{A \alpha_1 \omega_0 R_1 I_n}{4 \omega_n} \cos(\omega_0 - \omega_n)t + \frac{A \alpha_1 \omega_0 R_1 I_n}{4 \omega_n} \cos(\omega_0 + \omega_n)t$$

(\therefore) freq: $\omega_0 \pm \omega_n$

$$\text{rel. mag: } \frac{\alpha_1 \omega_0 R_1 I_n}{4 \omega_n}$$

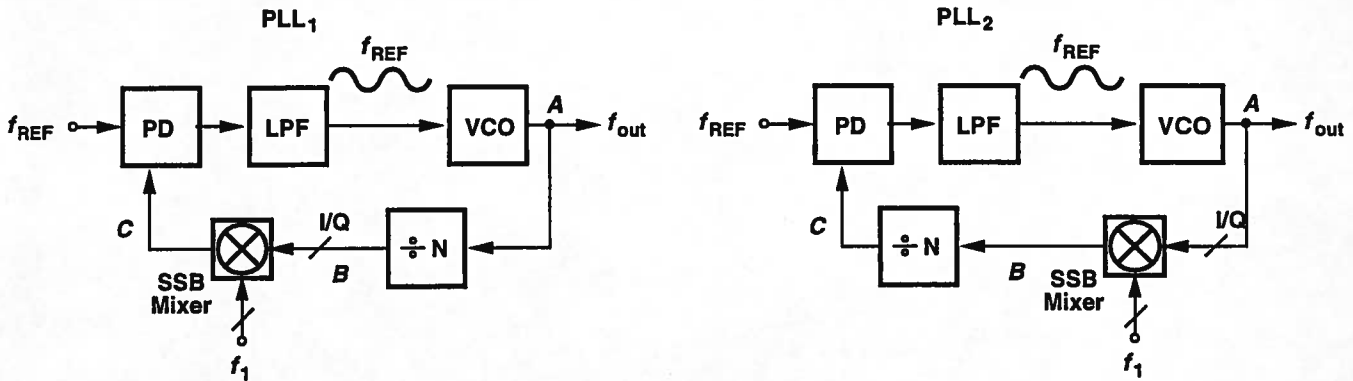4. Two PLL configurations are shown below. Assume the SSB mixer adds its input frequencies. Also, assume f_1 is a constant frequency provided externally and it is less than f_{REF} . The control voltage experiences a small sinusoidal ripple with a frequency of f_{REF} . Both PLLs are locked.


- Determine the output frequencies of the two PLLs.
- Determine the spectrum at point A due to the ripple.
- Now determine the spectrum at nodes B and C.




(a) PLL₁ : $\frac{f_{out}}{N} + f_1 = f_{REF} \Rightarrow f_{out} = N(f_{REF} - f_1)$

PLL₂ : $\frac{f_{out} + f_1}{N} = f_{REF} \Rightarrow f_{out} = N f_{REF} - f_1$


(b) PLL₁

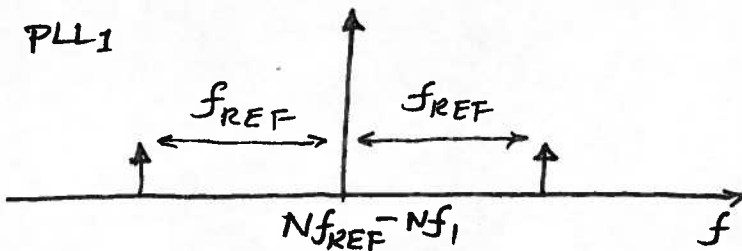


PLL₂

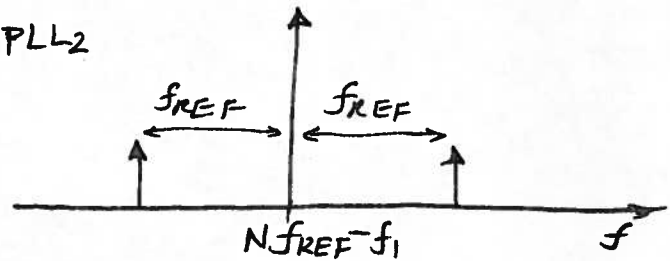


(c) PLL₁ Spectrum at B

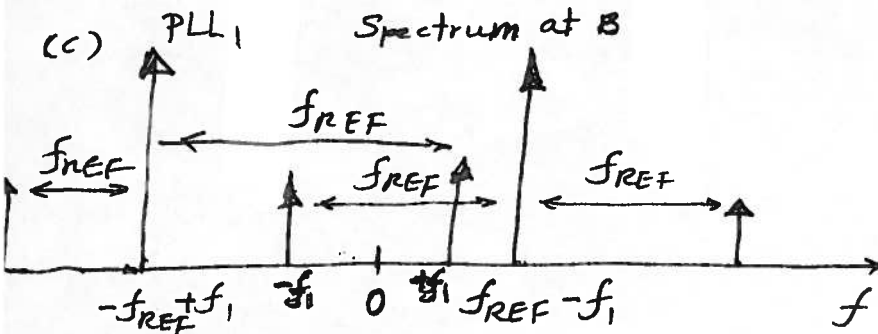

PLL₂ Spectrum at B

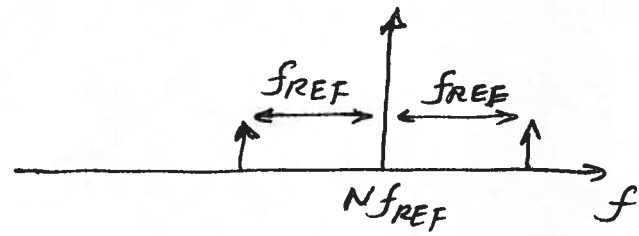

Spectrum at C

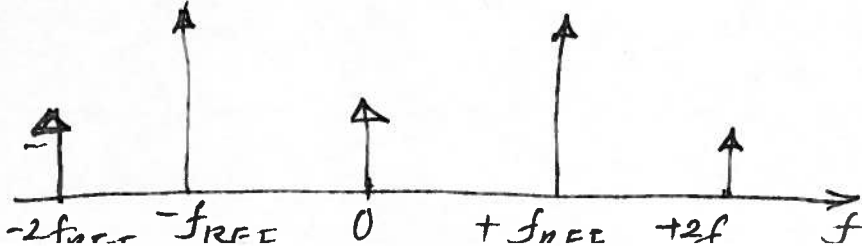

Spectrum at C

