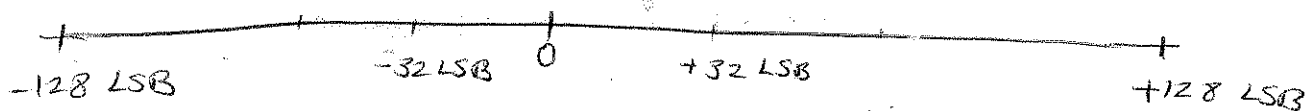


Digital Outputs of an 8-Bit 1.5-Bit/Stage ADC



$$\begin{aligned}
 V_{in} = +0.8 \text{ LSB} &\Rightarrow V_{res1} = 2V_{in} = 1.6 \text{ LSB} \Rightarrow 01 = D_1 \\
 &V_{res2} = 4V_{in} = 3.2 \text{ LSB} \Rightarrow 01 = D_2 \\
 &V_{res3} = 8V_{in} = 6.4 \text{ LSB} \Rightarrow 01 = D_3 \\
 &V_{res4} = 16V_{in} = 12.8 \text{ LSB} \Rightarrow 01 = D_4 \\
 &V_{res5} = 32V_{in} = 25.6 \text{ LSB} \Rightarrow 01 = D_5 \\
 &V_{res6} = 64V_{in} = 51.2 \text{ LSB} \Rightarrow 10 = D_6 \\
 &V_{res7} = 128V_{in} - V_R = -25.6 \text{ LSB} \Rightarrow 0 = D_7
 \end{aligned}$$

$$01 = D_0$$

$$\begin{aligned}
 D_{out} = &D_0 + D_1 2^{-1} + D_2 2^{-2} + D_3 2^{-3} \\
 &+ D_4 2^{-4} + D_5 2^{-5} + D_6 2^{-6} \\
 &+ D_7 2^{-7}
 \end{aligned}$$

$$\begin{array}{r}
 \Rightarrow D_{out} = \begin{array}{r} 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \end{array} \\
 \hline
 D_{out} = 10000000
 \end{array}$$

$$\Rightarrow D_{out} = 128$$

$$\begin{aligned}
 V_{in} = -0.8 \text{ LSB} &\Rightarrow V_{res1} = 2V_{in} = -1.6 \text{ LSB} \Rightarrow 01 = D_1 \\
 &V_{res2} = 4V_{in} = -3.2 \text{ LSB} \Rightarrow 01 = D_2 \\
 &V_{res3} = 8V_{in} = -6.4 \text{ LSB} \Rightarrow 01 = D_3 \\
 &V_{res4} = 16V_{in} = -12.8 \text{ LSB} \Rightarrow 01 = D_4 \\
 &V_{res5} = 32V_{in} = -25.6 \text{ LSB} \Rightarrow 01 = D_5 \\
 &V_{res6} = 64V_{in} = -51.2 \text{ LSB} \Rightarrow 00 = D_6 \\
 &V_{res7} = 128V_{in} + V_R = 25.6 \text{ LSB} \Rightarrow 1 = D_7
 \end{aligned}$$

$$\begin{array}{r}
 D_{out} = \begin{array}{r} 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \\ + \quad 01 \end{array} \\
 \hline
 D_{out} = 01111111
 \end{array}$$

$$\Rightarrow D_{out} = 127$$

$$\begin{aligned}
 V_{in} = +32.8 \text{ LSB} &\Rightarrow V_{res1} = (2V_{in} - V_R) = -62.4 \text{ LSB} \Rightarrow 00 = D_1 \\
 &V_{res2} = (2V_{res1} + V_R) = 3.2 \text{ LSB} \Rightarrow 01 = D_2 \\
 &V_{res3} = 2V_{res2} = 6.4 \text{ LSB} \Rightarrow 01 = D_3 \\
 &V_{res4} = 2V_{res3} = 12.8 \text{ LSB} \Rightarrow 01 = D_4 \\
 &V_{res5} = 2V_{res4} = 25.6 \text{ LSB} \Rightarrow 01 = D_5 \\
 &V_{res6} = 2V_{res5} = 51.2 \text{ LSB} \Rightarrow 10 = D_6 \\
 &V_{res7} = 2V_{res6} - V_R = -25.6 \text{ LSB} \Rightarrow 0 = D_7
 \end{aligned}$$

$$\begin{array}{r}
 D_{out} = \begin{array}{r} 10 \\ 00 \\ 00 \\ 01 \\ 01 \\ 01 \\ 01 \\ 01 \end{array} \\
 \hline
 D_{out} = 10100000
 \end{array}$$

$$\Rightarrow D_{out} = 160$$