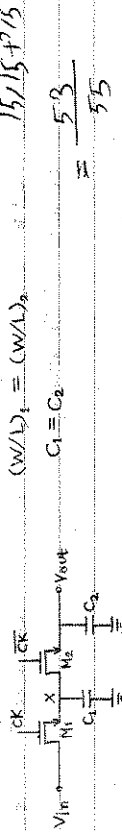


$$13/15 + \frac{10}{15} + \frac{10}{15} + \frac{10}{15} + \frac{10}{15}$$

Problem 12.10




$$(W/L)_1 = (W/L)_2$$

$$C_1 \approx C_2 = \frac{5.3}{5.5}$$

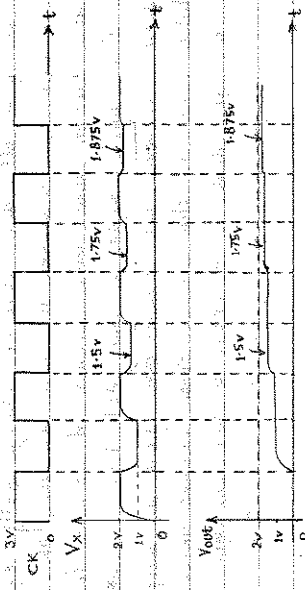(c) C_1, M_1 and M_2 can be together viewed as a resistor equal to $\frac{1}{f_{clk} C_1}$. Thus, the charging of C_2 on an average shall be given by a time constant $\tau = \frac{C_2}{f_{clk} C_1} = \frac{1}{f_{clk}}$


$$\text{Assuming that } V_{DD} = 3V, V_{TH} = 0.7V.$$



Initially when CK goes high, C_1 gets charged to $V_{in} \approx 2V$. When CK goes low, M_2 is ON and charge is shared between C_1 and C_2 . Since, $C_1 \approx C_2$, $V_x \approx V_{out} = 1V$. Again when CK goes high, M_2 is OFF, M_1 turns ON and C_1 again charges to $2V$. When CK goes low, $V_x \approx V_{out} = \frac{2C_1 + C_2}{C_1 + C_2} = 1.5V$ and so on.

31K

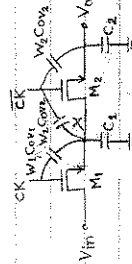(b) If M_1, M_2 are identical, when $CK \rightarrow 1$ to 0, $CK \rightarrow 0$ to 1, hence there will be no error in voltage at X since both the clock feedthrough errors will cancel off. When $CK \rightarrow 0$ to 1, there will be some feedthrough to V_{out} which we undo when $CK \rightarrow 1$ to 0 at the end of the cycle.



Hence the feedthrough does not affect the output voltage in steady state. Hence, no error is introduced in the op because of feedthrough.

Charge injection: When CK goes low, M_1 goes off. The worst case will be when all the charges in the inversion layer go towards the right. Error in V_x due to this will be $(W/L)_1 C_{ox} (V_{DD} - V_{TH}) \times \frac{1}{C_1}$.


Corresponding error at the output will be half of this value.

When M_2 goes off, the channel charge splits equally between C_1 and C_2 . However, in order to turn ON, M_2 would have taken that same amount of charge from C_1, C_2 which it gives back when it goes OFF. Hence, channel charge from M_2 does not cause any error in output. Hence total error in the output from charge injection is only due to M_1 . Thus, max. error $\approx \frac{(W/L)_1 C_{ox} (V_{DD} - V_{TH})}{2C_1}$.

$$\text{Max. total error in output} = \frac{(W/L)_1 C_{ox} (V_{DD} - V_{TH})}{2C_1}$$

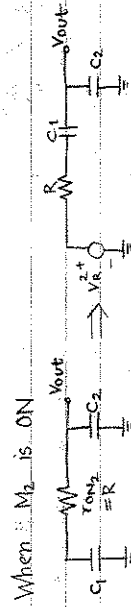(c) When M_1 is ON, rms noise voltage at X is given as $\sqrt{V_{in} \times \frac{W}{L} \times \frac{1}{f_{clk} C_1}} = \sqrt{\frac{kT}{C_1}}$

Half of this noise voltage will appear at the output when M_2 is ON.



$$\frac{V_{out}(s)}{V_R} = \frac{\frac{1}{sC_2}}{R + \frac{1}{sC_1} + \frac{1}{sC_2}} = \frac{1}{1 + \frac{C_2 + sCR}{C_1}}$$

$$S_{out}(f) = S_{in}(f) \left| \frac{V_{out}(j\omega)}{V_R} \right|^2$$

$$= 4kTR \frac{\left(\frac{1+C_2}{C_1} \right)^2 + 4\pi^2 R^2 C_2^2 f^2}{C_1^2}$$

$$\text{The total noise power at output}$$

$$P_{n,out} = \int_0^\infty \frac{4kTR df}{4\pi^2 R^2 C_2^2 f^2 + \left(1 + \frac{C_2}{C_1}\right)^2}$$

$$= \frac{4kTR}{2\pi RC} \times \frac{1}{1 + C_2/C_1} \tan^{-1} \left\{ \frac{2\pi R C f}{1 + C_2/C_1} \right\} \Big|_{f=0}^\infty$$

$$= \frac{2kT}{\pi C_2} \times \frac{1}{2} \times \frac{\pi}{2} \quad [C_1 = C_2]$$

$$= \frac{kT}{2C_2}$$

The total output noise voltage is given by

$$V_{n,out}^2 = \frac{1}{4} \frac{kT}{C_1} + \frac{kT}{2C_2} = \frac{3}{4} \frac{kT}{C_1}$$

575

Problem 12.11

$$V_{in} = V_0 \sin \omega_0 t + V_0 \quad f_{clk} = 50 \text{ MHz}$$

$$V_0 = 0.5 \text{ V}$$

$$\omega_0 = 2\pi \times 10 \text{ MHz}$$



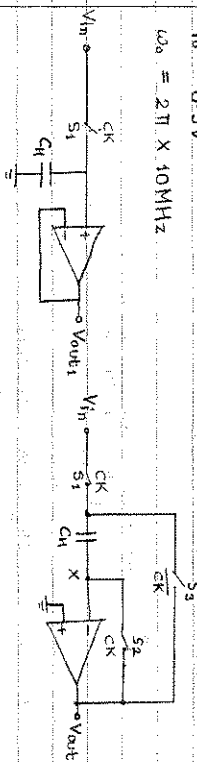
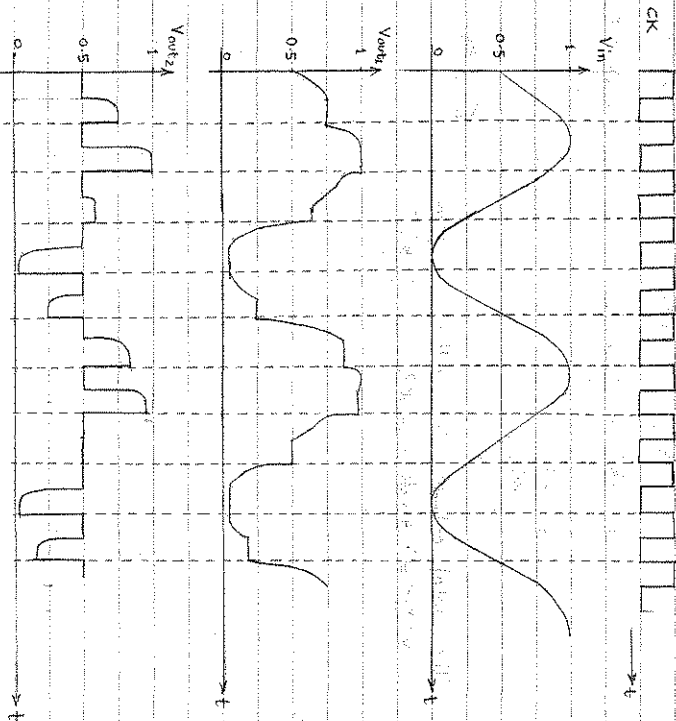


Fig 12.29(b)

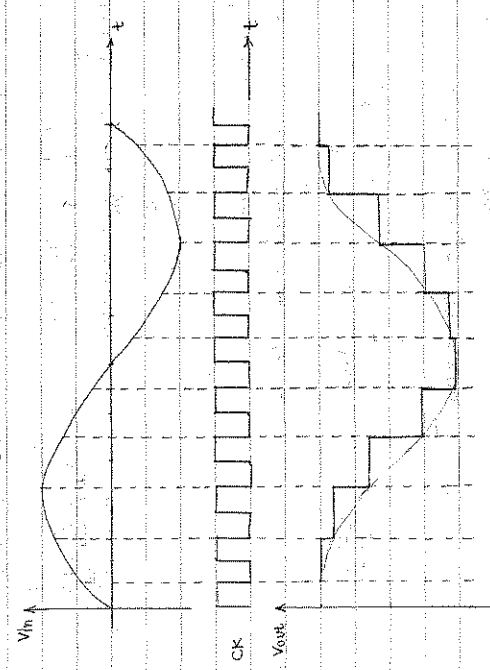

Problem 12.15

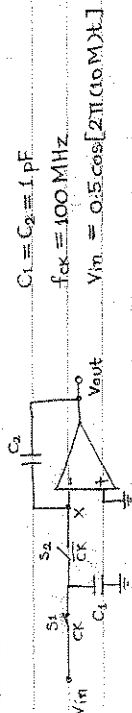

S_1, S_2 and C_1 form a resistor of value $R = \frac{1}{f_{CK} C_1} = 10k\Omega$


$$V_{out} = \frac{-1}{RC_1} \int V_{in} dt$$

$$V_{out} = \frac{-1}{RC_1} \int_0^t 0.5 \cos[2\pi(100M)t] dt$$

$$= \frac{-0.5}{RC_1} \times \frac{\sin[2\pi(100M)t]}{2\pi \times 10^6}$$

Hence, o/p amplitude = 0.796 V.

Problem 12.16

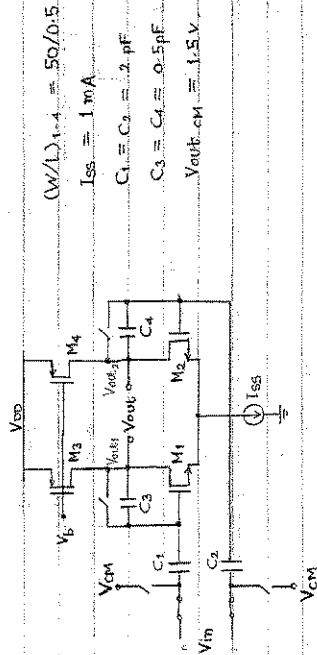

(a) Maximum o/p swing

$$V_{DD} - V_{ov3,4} \geq V_{out1,2} \geq V_{iss} + V_{ov1,2}$$

$$V_{DD} - \sqrt{\frac{2 \times 0.5m}{\mu_p C_{ox} (W/L)_3}} \geq V_{out1,2} \geq V_{iss} + \sqrt{\frac{2 \times 0.5m}{\mu_n C_{ox} (W/L)_1}}$$

$$3 - 0.508 \geq V_{out1,2} \geq V_{iss} + V_{ov1,2}$$

$$3 - 0.508 \geq V_{out1,2} \geq 1.5 - 0.7V$$

$$2.491V \geq V_{out1,2} \geq 0.8V$$

Maximum o/p swing is $2(2.491 - 0.8) = 3.382V$

(b) Gain error

$$Gain A_v = g_{m1,2} (r_{o1} || r_{o3})$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = 3.664mS$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = 20k\Omega$$

$$r_{o3} = \frac{1}{\lambda_3 I_{D3}} = 10k\Omega$$


$$A_v = 24.43$$

$$Gain error = \frac{1}{A_v} \left(\frac{C_4}{C_3} + 1 \right) = 20.46\%$$

c) In amplification mode

$$I_{amp} \approx C_1 \times \frac{1}{g_m} \approx C_1 \times \frac{1}{g_{m1}} \approx 545.85 \text{ pS}$$

Problem 12.21

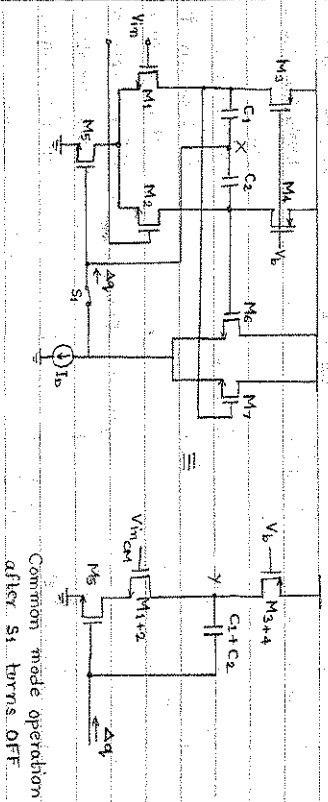

Common mode operation after S1 turns OFF.


If no charge was injected, C_1 and C_2 will hold a common mode voltage $= (V_{SS} + V_{GS7}) - V_{GS7} = V_{GS7}$. If Δq is injected towards the gate of M_5 , it will produce an error voltage in the capacitors equal to $\frac{\Delta q}{C_1 + C_2}$.

If the common-mode gain from gate of M_5 to node Y is very large, we may assume that the gate of M_5 remains fairly constant and all the error voltage appears at Y . Thus, change in the o/p CM level is approximately $\frac{\Delta q}{C_1 + C_2}$.


Gain from gate of M_5 to node Y is given by $A = g_{m5} \times [r_{o5} || r_{o4} || ((1 + g_{m1} g_{m2}) (r_{o1} || r_{o2}))]$.

Thus, change in voltage at gate of $M_5 = \frac{\Delta V}{A} = \frac{\Delta q}{A(C_1 + C_2)}$.

Problem 12.12

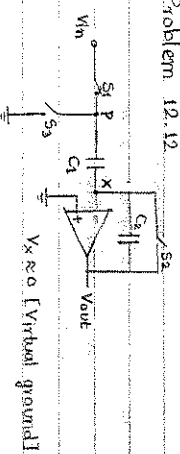

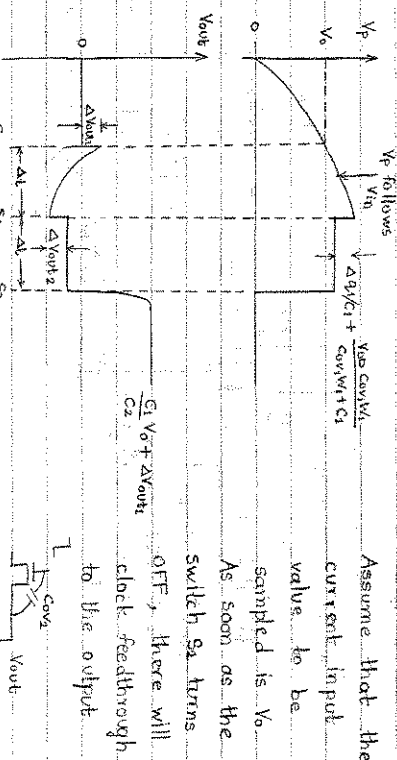Initially when S_2 is ON, $V_{out} = V_x \neq 0$, $V_{c2} = 0$.



Assume that the current input values to be sampled is V_0 . As soon as the switch S_2 turns OFF, there will be a clock feedthrough to the output.

$$\Delta V_{out, clk feedthrough} = -\frac{C_{ov2} W_2 V_{DD}}{C_{ov2} + C_2}$$

Also, in worst-case, there will be a charge injection on node X given by $\Delta q_2 = (W/L)_2 C_{ox} V_{DS} - V_{DS} - V_{th}$. This charge will end up on C_2 & hence, $\Delta V_{out, inj} = \pm C_2 \Delta q_2$. Thus $\Delta V_{out, 1} = \Delta q_2 C_2 = \frac{C_{ov2} W_2 V_{DD}}{C_{ov2} + C_2}$.

Even after S_2 turns OFF, V_x will follow V_{in} and hence this will get amplified by $(-C_1/C_2)$ and appear at output. When S_1 turns OFF, ΔV_P clk feedthrough $= \frac{-C_{ov1} W_1 V_{DD}}{C_{ov1} + C_1}$.

Worst-case charge injection will be towards the right $\Delta q_1 = (W/L)_1 C_{ox} (V_{DS} - V_{th})$. ΔV_P inj $= -\Delta q_1 C_1$. ΔV_P S_1 turns OFF $= -\Delta q_1 C_1 = \frac{-C_{ov1} W_1 V_{DD}}{C_{ov1} + C_1} \Rightarrow \Delta V_{out, 2} = \frac{C_2}{C_1} \Delta V_P$ S_1 turns OFF.

When S_s turns ON, $V_p \approx 0$ (i.e. V_p changes overall from V_0 to 0)
Hence, Y_{out} will change from $(0 + \Delta Y_{out})$ to $\{ \frac{C_2}{C_1} V_0 + \Delta Y_{out} \}$

where ΔY_{out} is only an offset.

