

NAME: KAISER NEHAL

UID: 004037325

HOMEWORK #3

EE 215D.

SPRING 2012.

$$\frac{20}{20} + \frac{14}{15} = \frac{34}{35}$$

Q. NO. 1

Part (a)


$$0.5 \text{ LSB} = 0.5 \times \frac{0.9}{2^{10}} = 0.4394 \text{ mV}$$

The worst case settling time occurs when $j=4$
i.e. $D_1, D_2, D_3, D_4 = 1.8\text{V}$ and rest are at 0V.

$$t_s = 418.8 \text{ ps}$$

(5/5)

Part (b)

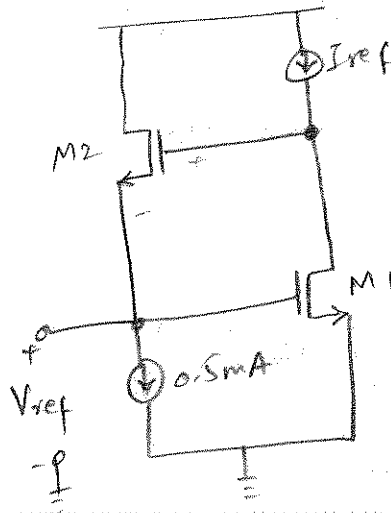

$V_{GS1} = V_{ref}$
Since M_2 is carrying $0.5\text{mA} \Rightarrow V_{GS2} \geq V_{TH}$
 $\therefore V_{GD1} < V_{TH}$ and M_1 is in saturation.

$$I_{D1} = I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TH})^2$$

$$\mu_n = 310.25 \times 10^{-4}$$



$$V_{GS1} = V_{ref} = 0.9$$

$$C_{ox} = 8.42 \times 10^{-3}$$

$$V_{TH} = 0.47$$

$$\Rightarrow I_{ref} = 5.32 \text{ mA}$$

(5/5)

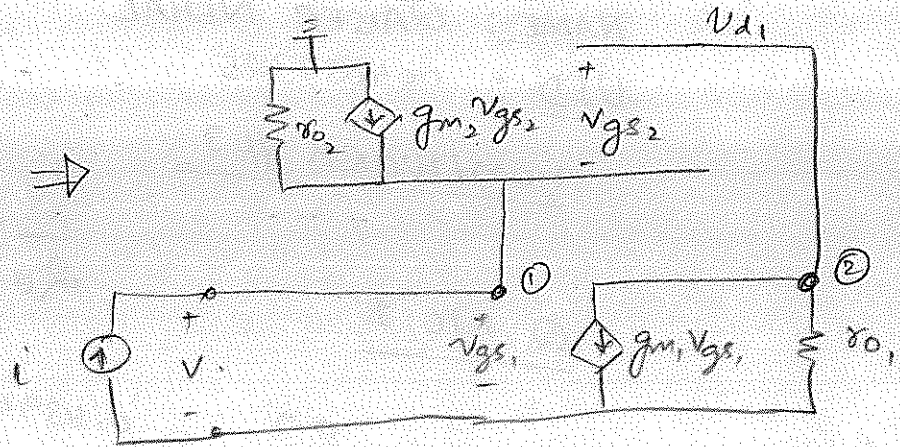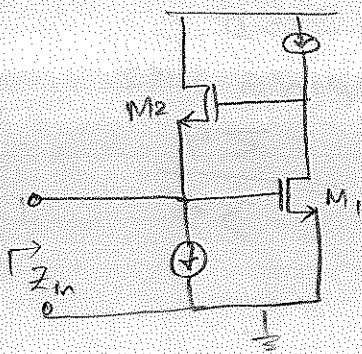

$$Z_{in} = \frac{V}{i}$$

$$v_{gs1} = V$$

KCL @ ①

$$i = \frac{V}{r_{o2}} - g_{m2} v_{gs2} \quad \text{--- ①}$$

KCL @ ②

$$0 = g_{m1} V + \frac{v_{d1}}{r_{o1}}$$

$$\Rightarrow v_{d1} = -g_{m1} r_{o1} V$$

$$v_{gs2} = v_{d1} - V$$

$$v_{gs2} = -V (1 + g_{m1} r_{o1})$$

Substitute in eq ①

$$i = V \left[\frac{1}{r_{o2}} + g_{m2} (g_{m1} r_{o1} + 1) \right]$$

$$\Rightarrow Z_{in} = \frac{V}{i} = \frac{r_{o2}}{1 + g_{m2} r_{o2} (1 + g_{m1} r_{o1})}$$

$$g_{m1} r_{o1} \gg 1$$

$$g_{m2} r_{o2} g_{m1} r_{o1} \gg 1$$

$$Z_{in} \approx \frac{1/g_{m2}}{g_{m1} r_{o1}}$$

Using

$$g_{m2} = 7.9 \text{ mS}$$

$$g_{m1} = 17.57 \text{ mS}$$


$$r_{o1} = 1.4 \text{ k}\Omega$$

$$\Rightarrow Z_{in} \approx 5.15 \Omega$$

↓ This is only the real part there is an imaginary part that affects the settling

the real part there is an imaginary part that affects the settling

The source can then be modelled as:

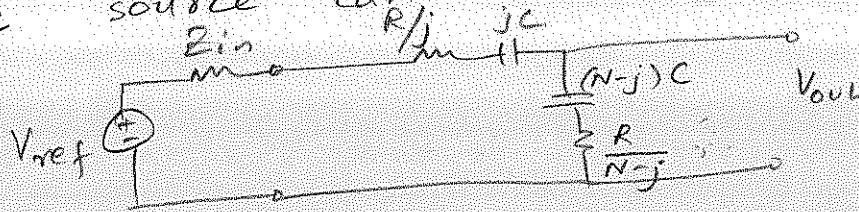

Due to the additional Z_{in} in the charging path, the settling should be increased.

Part (c)

The worst case settling time occurs when $j=3$
i.e. $D_1, D_2, D_3 = 1.8$, and rest are 0V.

$$t_s = 373.6 \text{ ps} \quad (5 \text{ M})$$

This is lower than that of part (a) because V_{ref} is now no longer maintained at 0.9V. In fact V_{ref} jumps to 1V initially and then settles to 0.9V resulting in smaller worst case settling time.

Part (d)

With $L_s = 2 \text{ nH}$ added, the settling time is $t_s = 4.27 \text{ ns}$ (when all caps are switched to V_{ref})

However using $R_s = 74 \Omega$ in series with L_s gives

$$t_s = 339.6 \text{ ps} \quad (5 \text{ M})$$

~~Q NO 2~~

Q1. 1. 1. 1.

19. 1. 1.

19. 1. 1.


19. 1. 1.

19. 1. 1.


19. 1. 1.

19. 1. 1.


Part(c) Settling time.

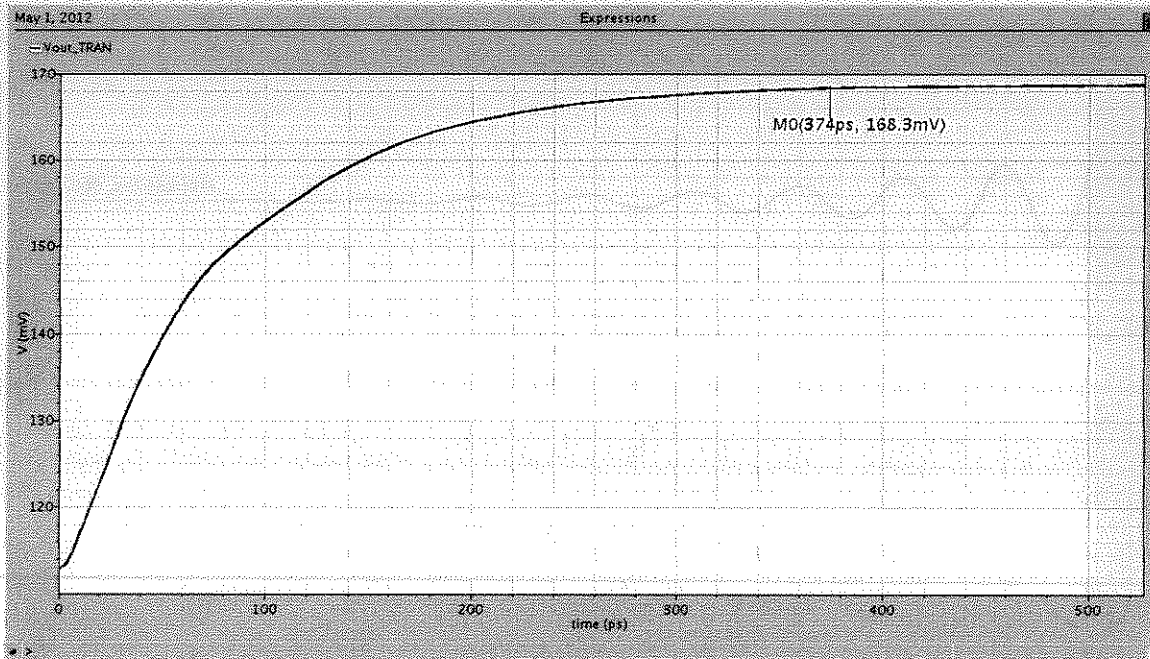


Part(c) Vref jumps to 1V initially.

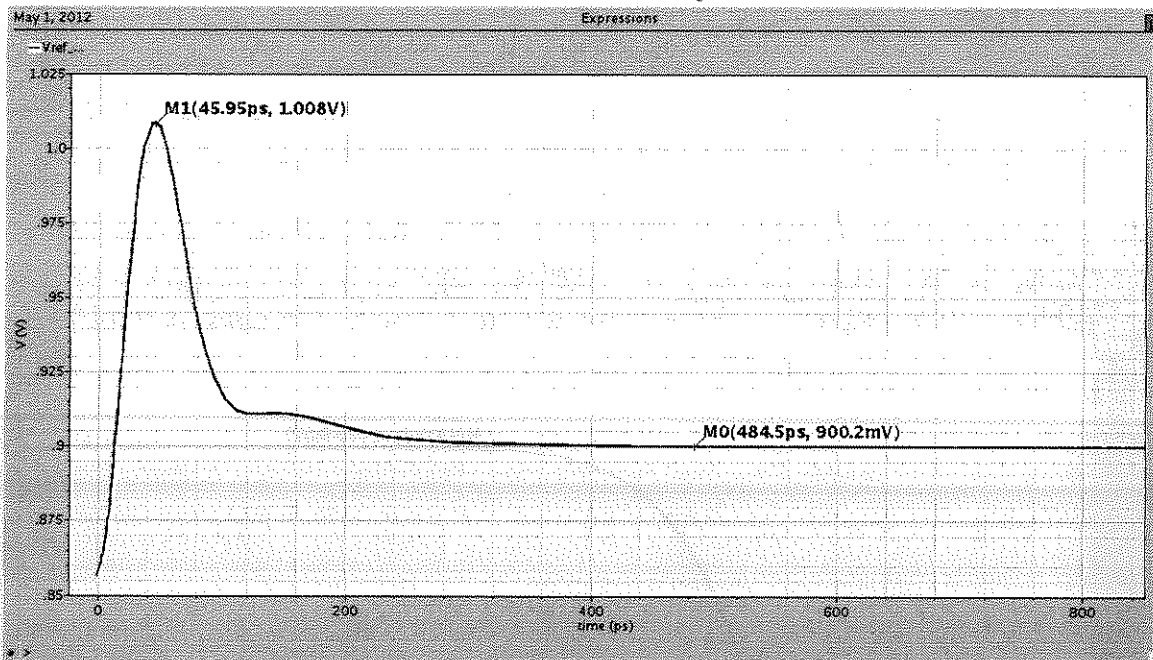

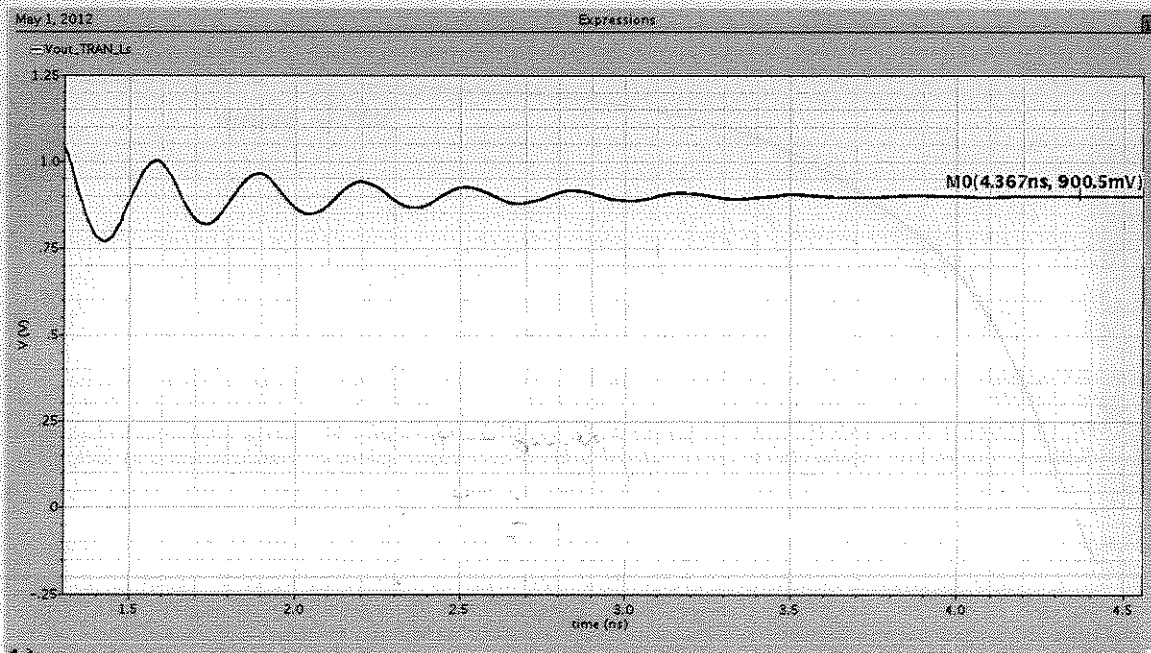Part d) Effect of $L_s = 2\text{nH}$ on settling time. (jump happens @ $t = 100\text{ps}$)





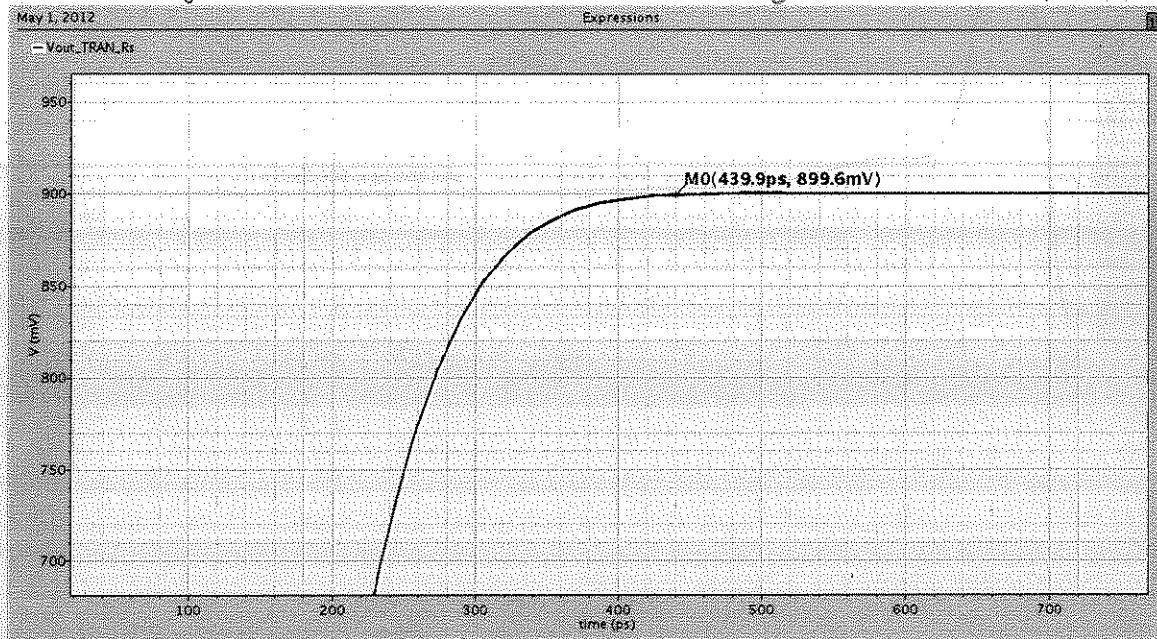Part d) Using $R_s = 74\Omega$ reduces settling time (jump occurs @ $t = 100\text{ps}$)



Q. NO. 2.

Part (a)

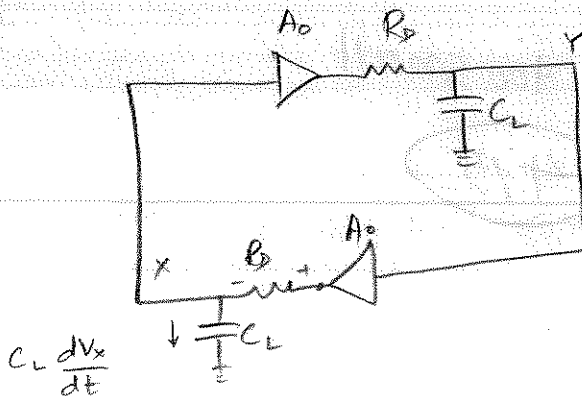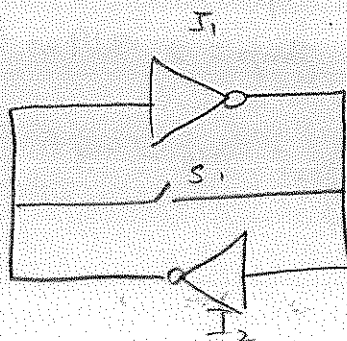

$$A_o V_y = R_D C_L \frac{dV_x}{dt} + V_x$$

$$A_o V_x = R_D C_L \frac{dV_y}{dt} + V_y$$

Similarly

$$V_{xy} \triangleq V_x - V_y$$

$$-A_o V_{xy} = R_D C_L \frac{dV_{xy}}{dt} + V_{xy}$$

$$\Rightarrow V_{xy} (1 + A_o) + R_D C_L \frac{dV_{xy}}{dt} = 0$$

$$\Rightarrow V_{xy}(t) = V_{xy0} e^{-t/\tau_P}$$

where V_{xy0} = Initial voltage difference between node X & Y.

$$\tau_P = \frac{R_D C_L}{-A_o - 1}$$

$$R_D = r_{on} \parallel r_{op}$$

where $A_o = -(g_{m_n} + g_{m_p})(r_{on} \parallel r_{op})$

$$r_{on} = 5.52 k\Omega, \quad r_{op} = 6.13 k\Omega$$

$$g_{mN} = 4.712 mS, \quad g_{mP} = 2.319 mS$$

$$C_L = C_{db1} + C_{db3} + C_{gs2} + C_{gs4} \approx 40 fF$$

$$R_D = r_{on} \parallel r_{op} = 2.9 k\Omega$$


$$C_L = 40 fF$$

$$A_o = -20.39$$

$$\tau_R \approx 6 ps$$

too small

4/5

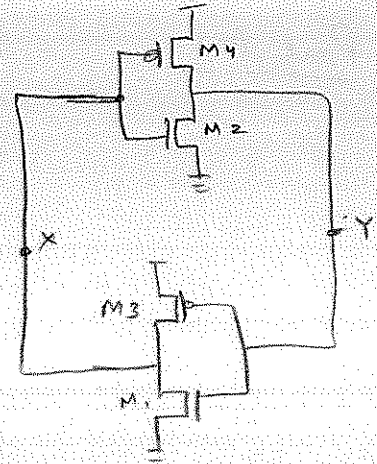

(b)

$$V_{xy}(t=0) = 2 mV$$

$$V_x = 1.6 V$$

$$V_y = 0.2 V$$

$$@ t = 164.03 ps$$

$$@ t = 136.28 ps$$

$$\tau_R = ?$$

$$t/\tau_R = \ln\left(\frac{V_{xy}}{V_{xy0}}\right)$$

Cadence.

Plot $\ln\left(\frac{V_{xy}}{V_{xy0}}\right)$ using

find $t/\tau_R = \ln\left(\frac{V_{xy}}{V_{xy0}}\right)$

@ $t = 5 ps, 10 ps, 15 ps$

From this data we can find out τ_R .

@ $t = 5 ps$

$$\ln\left(\frac{V_{xy}}{V_{xy0}}\right) = \frac{t}{\tau_R} = 2.57 mV$$

$$\Rightarrow \tau_R = \frac{5 ps}{2.57 mV} = 20.1 ps$$

$$(average) \tau_R = 20.39 ps.$$

$$V_{xy}(t=0) = 4 \text{ mV}$$

$$V_x = 1.6 \text{ V} @$$

$$V_y = 0.2 \text{ V} @$$

$$t = 149.713 \text{ ps}$$

$$t = 121.94 \text{ ps}$$

515

$$\text{Power dissipation} = 2.8746 \text{ mW.}$$

$$\gamma_R = 20.44$$

(C) when $\left(\frac{W}{L}\right) = \frac{24 \mu\text{m}}{0.18 \mu\text{m}}$

$$V_{xy}(t=0) = 2 \text{ mV}$$

$$V_x = 1.6 \text{ V} @ t = 163.848 \text{ ps}$$

$$V_y = 0.2 \text{ V} @ t = 136.22 \text{ ps}$$

$$\gamma_R = 20.1$$

$$V_{xy}(t=0) = 4 \text{ mV}$$

$$V_x = 1.6 \text{ V} @ t = 149.53 \text{ ps}$$

$$V_y = 0.2 \text{ V} @ t = 121.88 \text{ ps}$$

$$\gamma_R = 20.1$$

$$\text{Power dissipation} = 5.74 \text{ mW.}$$

515

Percentage change in $\gamma_R = 1.66 \%$

Percentage change in Power = 100%
dissipation when S_1 is ON

413


Handwritten notes and scribbles in the upper right quadrant.

Handwritten circled text, possibly "7/17".


Q.NO.2

$$(W/L) = \frac{12 \mu m}{0.18 \mu m}$$

Part (b) $V_{xy}(t=0) = 2mV$

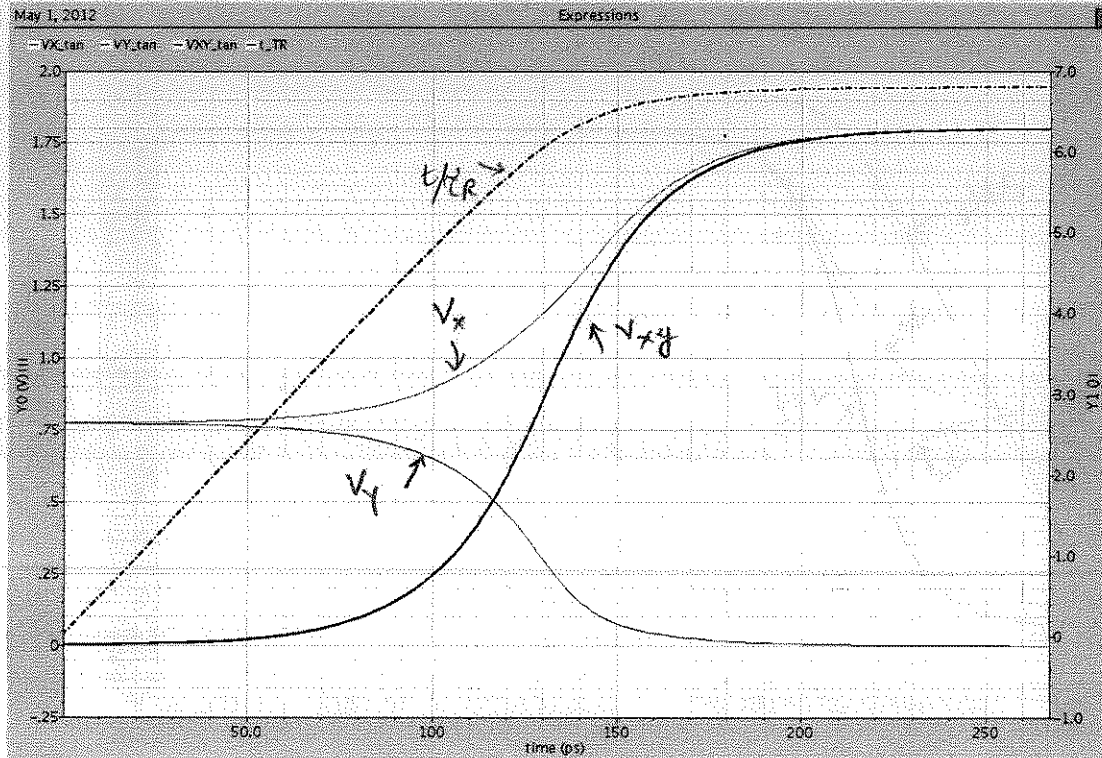


$V_{xy}(t=0) = 4mV$

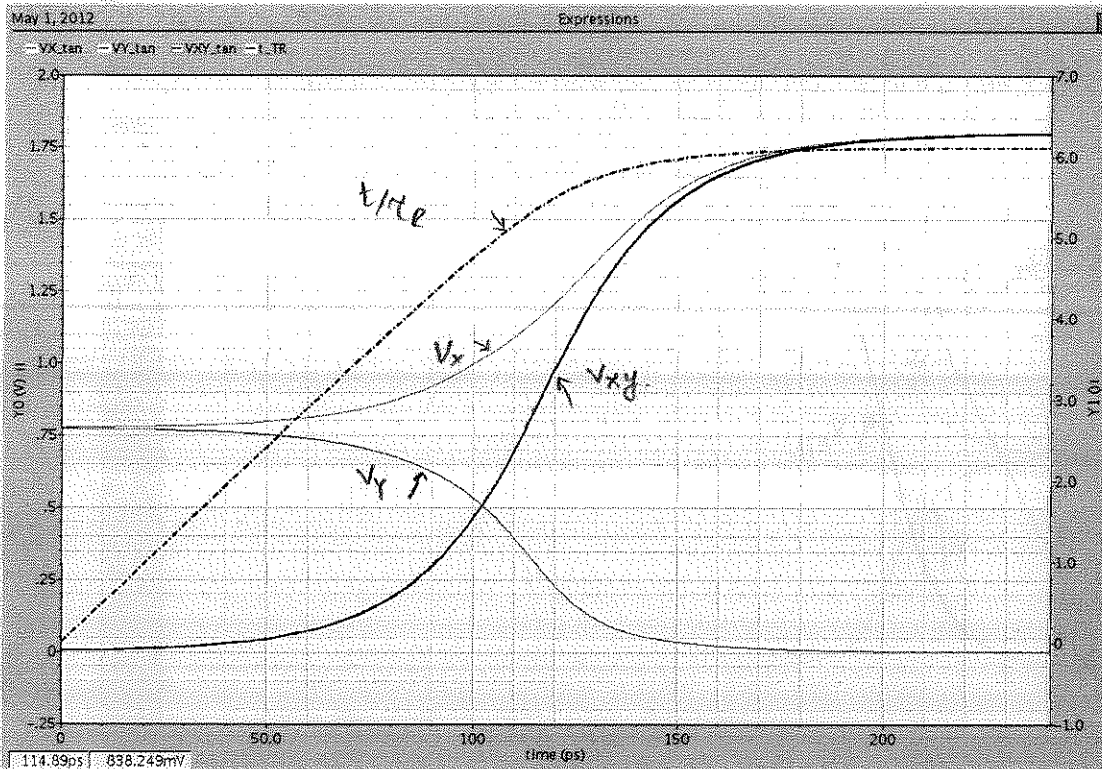

$$(W/L) = \frac{24 \mu m}{0.18 \mu m}$$

Part (c)

$$V_{xy}(t=0) = 2 \text{ mV}$$

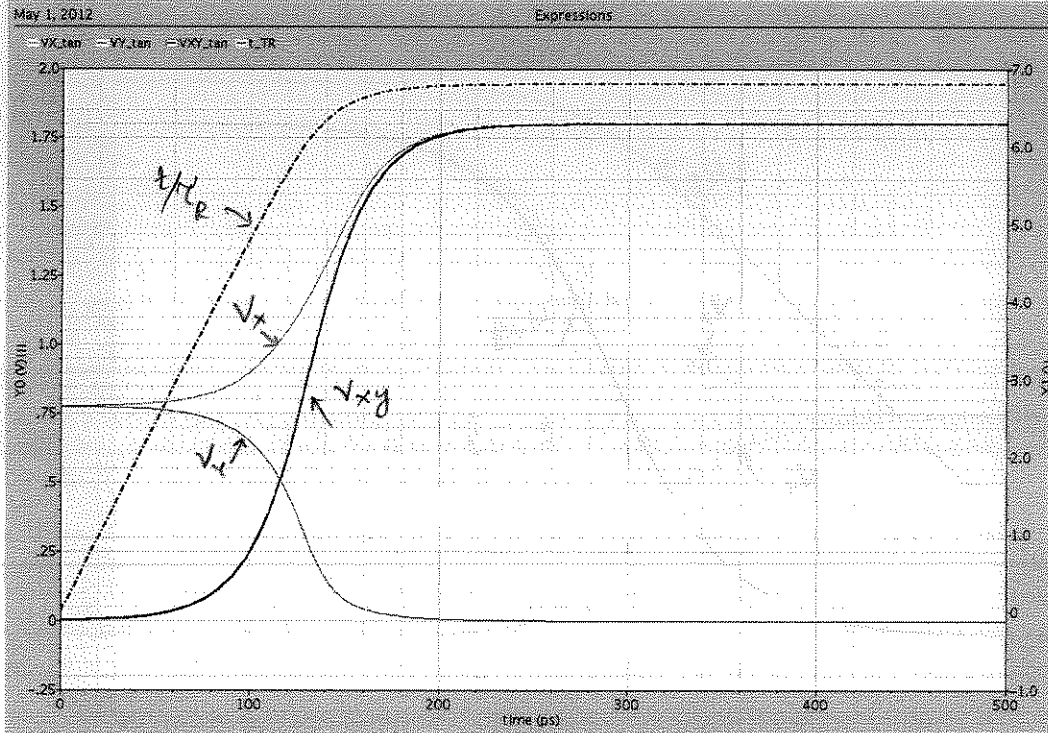

$$V_{xy}(t=0) = 4 \text{ mV}$$

