

Homework #4

Due Mon. May 14, 2007

1. In this problem, we study the effect of nonidealities on the performance of a two-step 10-bit ADC (with 5 bits resolved in each stage). For each of the following errors, explain how the input/output characteristic of the ADC is affected and demonstrate using proper plots (e.g. residue plots, input/output plots, etc.).



- (a) Comparator A_j in the first stage has an offset voltage of $+1.3$ LSB.
- (b) The reference ladder of the first stage has an INL of $+0.7$ LSB at its midpoint.
- (c) The DAC has an offset voltage of $+0.8$ LSB.
- (d) The DAC has a gain error of $+0.04\%$.
- (e) The DAC has a DNL of $+1.3$ LSB.
- (f) The DAC has an INL of $+1.4$ LSB.
- (g) The subtractor has an offset of $+1.7$ LSB.
- (h) The subtractor has a gain error $+0.9\%$.
- (i) The subtractor has an INL of $+1.5$ LSB.

(j) Suppose the subtractor has a nominal voltage gain of 8. What should the full-scale voltage of the second stage be (in LSB)? How much error can we tolerate in the gain of the subtractor or the full-scale voltage of the second stage if DNL is to remain below 0.2 LSB? How much comparator offset is allowed in the second stage?






2. Design an 8-bit folding and interpolating ADC. Consider two cases:

- (a) The analog input can be loaded by at most 16 differential pairs.
- (b) The analog input can be loaded by at most 32 differential pairs.

(Assume the input stage of each comparator requires a differential pair.) Provide a diagram similar to that of the 6-bit example in the lecture notes for each case, but also show the interpolation network in detail. Summarize the hardware requirements in two tables, showing the total number of differential pairs, comparators, and resistors for each case. (You need not count the load resistors used in the differential pairs.)
  
$$\begin{array}{r} 100 \\ \hline 100 \end{array}$$
 $(N = 2^5)$

     
$\therefore \text{DNL} = +1.3 \text{ LSB}$
 $\rightarrow 1 \text{ missing code.}$




∴ DNL of $+0.7 \text{ LSB}$

(c)



DAC output (Analog)

 

Residue

 

Digital

  


$\therefore$ DNL of 0.9 LSB

(d) DAC has 0.03% error


$$\frac{1}{2^{10}} \times 100 = 0.0976\% \text{ (1 LSB)}$$

$\therefore$ 0.03% error $\Rightarrow \approx 0.3 \text{ LSB}$



DAC output

 

Residue

 


Digital

  


$\therefore$ DNL of 0.3 LSB (0.9998 LSB)

(e) DAC has a DNL of $+1.5$ LSB.


DAC output

 

Residue

 


Digital output

 


$\therefore$ DNL of 1.5 LSB
 $\rightarrow$ 1 missing code

 (f) DAC has a INL of -1.2 LSB to $+3.2 \text{ LSB}$

(I did this for the case of -1.2 LSB INL , and the result will be very similar)




Digital output

 


$\therefore$ 1 missing code
 and more possible
 missing codes.
 DNL of 1.2 LSB

$\uparrow (+1.2 \text{ LSB})$
 case

 (g) Subtractor has an offset of $+1.8 \text{ LSB}$.




 ∴ DNL of 1.8 LSB
1 missing code @ each 2^5 set.




 (h) Subtractor has a gain error $+0.9\%$.

$$32 \text{ LSB} \times \frac{0.9}{100} = 0.288 \text{ LSB}$$




∴ DNL of 0.288 LSB

 

(1) Subtractor has an INL of $\pm 1.4 \text{ LSB}$.


Residue

 


(I did the case of -1.4 LSB)

The result is actually almost same with opposite trend. (narrower $\rightarrow$ wider)


$\therefore$ Narrower, wider Repeated.

 

(j) Subtractor : Nominal gain 4

 

When $\text{DNL} < 0.2 \text{ LSB}$

 


$$\frac{12.8 - E}{32} \times 0.8 \text{ LSB} = 4 - E$$

$$102.4 - 0.8 E = 128 - 32 E \quad \rightarrow \quad E \approx 0.82 \text{ LSB}$$

$$31.2 E = 25.6$$

$$\therefore \text{Gain Error} = \frac{0.82 \text{ LSB}}{12.8 \text{ LSB}} \times 100 = 0.64\%$$

 
$$\text{Full Scale} = 127.18 \text{ LSB}$$





$\therefore 0.8 \text{ LSB}$ offset is allowed.

2. 8-bit folding and interpolating ADC.

(a) At most 8 differential pairs.

 

8bit $\rightarrow$ 56 LSB.

  

1 DP


1 comparator

8bits

5 DP

4 resistors


128 comparators

 

64 resistors

64 resistors

256 Resistors



 


128 comparators

6 Differential Pairs
129 comparators
260 Resistors

" Assumed
the comparator for 1 MSB
also has a differential pair.

(b) At most 16 differential pairs.

   

3 DP


3 comparators

9 DP

8 Resistors

64 comparators

6 LSBs

 

12 Differential Pairs
67 comparators
136 Resistors.

* Summary

	DP	Comparators	Resistors
(a)	6	129	260
(b)	12	67	136

