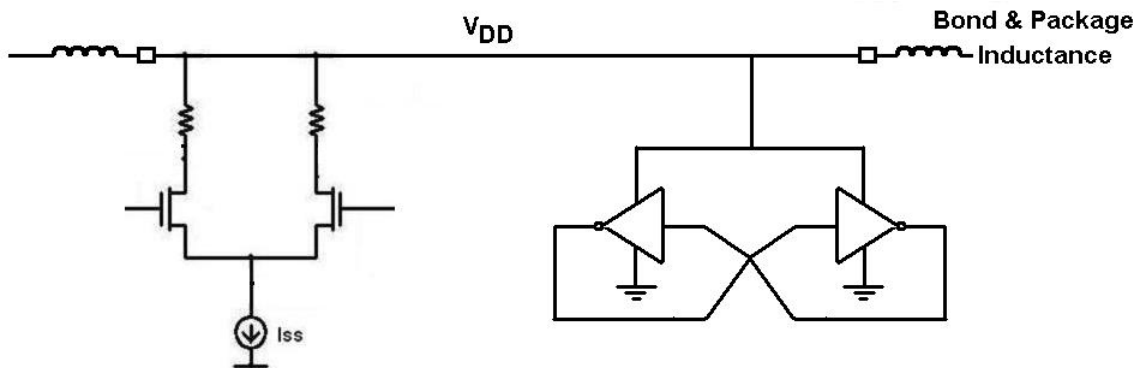


Layout Considerations


Basic Issues

- Analog vs. Digital Supplies




-

- DC Voltage Drops

 


**e.g. for 1mm long wire (i.e. 100 sq) and 50mΩ/sq,
this corresponds to: Resistance = 5Ω**

- - Bond Wires & Device Capacitances

 


-Substrate Coupling

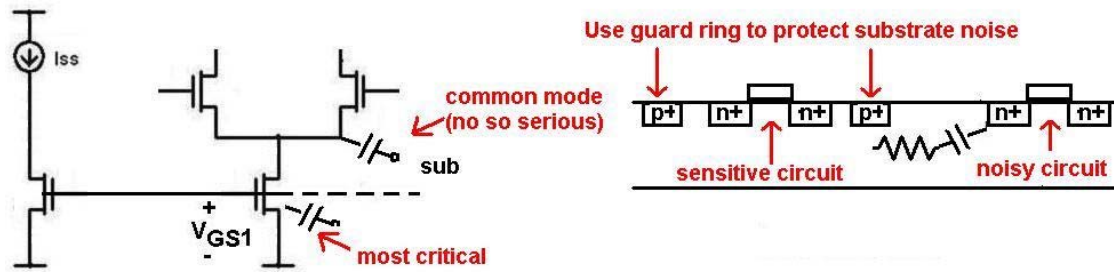

Different arguments for connecting substrate to analog ground and digital ground. Not clear. But the best way is to have a low-inductance connection to substrate.

- **Clock Noise Coupling**

 

Need a clean buffer.


Layout of MOS Devices

- **Multi-Finger Structures**

Slicided poly

RD = 8~10Ω

e.g. with 0.13-
umtech,
 
$$\text{gate} = 360 \times 10 = 3.6\text{k}$$


 
- MOS Devices Used as Capacitors

Do not use if linearity of capacitor is important. Good for bypassing:

This cap should really behave like a cap at the frequency of interest.

Thus, $R_{on} \ll 1 / C\omega$

Since $C = WL \times C_{ox}$,
Choose minimum L




But must make sure on-resistance is sufficiently small (Q is high.)



- Measure on-resistance for given gate voltage.
- Divide the value by 12.

Sometimes deliberately choose a low Q to dampen ringing due to bond wire inductance.

 - Matched MOS structures
 - o Use same orientation
 - o Account for asymmetries due to nonvertical implants:



Bad for S1, S2, D1 and D2 to match

  


Better solution
(require dummy at the sides)



Even better solution
(No dummy required)

 - Make the surroundings of transistors the same.
- Cross connect to cancel gradients.




Which connection (red or black) is less sensitive to mismatch?

Capacitors

Poly-Diffusion

Metal-Poly


“Native Caps”

 


Issues:

Nonlinearity, matching, temp. coefficient, bottom- and top-plate parasitics, series resistance, contact placement

Matched Caps

 


Output Drivers & Clock Buffers

 


Need to simulate with bond wire inductance to Vdd

- Don't make the driver too large!
- If possible, make the driver differential.
- If possible, reduce the output swing.

 In a fully custom-designed system, we can try to route currents rather than voltages.



Guard Rings

 


Guard ring can be N+, P+ or N-well

Can do the same in n-well. It is also believed that guard rings improve matching as well.

In most modern CMOS technologies, the substrate has a low resistivity. As a result, the distance between analog and digital blocks has little effect on the amount of coupled noise.

Miscellaneous

- Resistor Ladder Layout

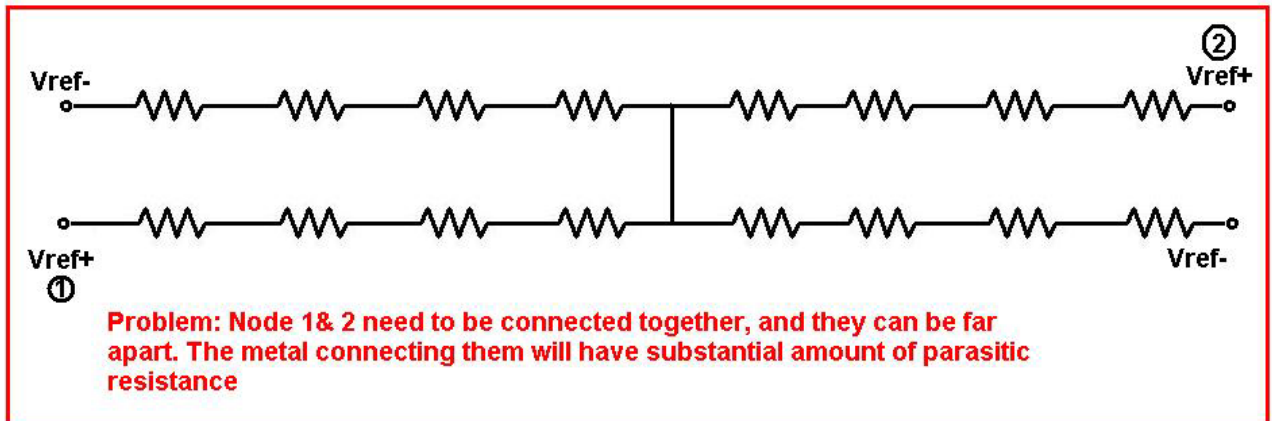

- Coupling through Bias Line

