

63/65

HW 2

13/15 + 29/20 + 30/30

Long Kong

503 990 487

1. (a). Output voltage is $V_{out} = V_i - V_i e^{-\frac{t}{R_{on}C_H}}$ when $V_{in} = V_i$ is a constant.

Now, let $V_{out} = V_i - 0.5 \text{ LSB}$

$$\Rightarrow V_i e^{-\frac{t}{R_{on}C_H}} = 0.5 \text{ LSB} = 0.5 \times \frac{V_i}{2^8}$$

where $R_{on} = 400 \Omega$, $C_H = 0.35 \text{ pF}$

$$\Rightarrow \underline{t = 0.873 \text{ ns}}$$

(b). First we should find the initial voltage on C_H . Since the previous hold value is at the negative peak, it's obvious that $V_{out}(t=0) = -0.35 \text{ V}$.

According to the time domain equation: $\frac{V_{in} - V_{out}}{R_{on}} = C_H \frac{dV_{out}}{dt}$

$$\Rightarrow \frac{V_i \sin \omega t - V_{out}}{R_{on} C_H} = \frac{dV_{out}}{dt}$$

Take s domain transform, $V_{out}(s) = \frac{V_i \omega_{in}}{(s^2 + \omega_{in}^2)(1 + s R_{on} C_H)} = V_i \omega_{in} \left[\frac{(As + B)}{s^2 + \omega_{in}^2} - \frac{C}{1 + R_{on} C_H s} \right]$

$$\Rightarrow \begin{cases} A R_{on} C_H = C \\ A + B R_{on} C_H = 0 \\ B - C \omega_{in}^2 = 1 \end{cases} \Rightarrow \begin{cases} A = \frac{-1}{\frac{1}{R_{on} C_H} + R_{on} C_H \omega_{in}^2} \\ B = \frac{1}{1 + R_{on}^2 C_H^2 \omega_{in}^2} \\ C = -\frac{R_{on} C_H}{\frac{1}{R_{on} C_H} + R_{on} C_H \omega_{in}^2} \end{cases}$$

Take inverse s transform, $V_{out}(t) = V_i \omega_{in} \left(A \cos \omega_{in} t + \frac{B}{\omega_{in}} \sin \omega_{in} t - \frac{C}{R_{on} C_H} e^{-\frac{t}{R_{on} C_H}} \right)$
 $= V_i \sin(\omega_{in} t - \phi) + \left(V_i \frac{R_{on} C_H \omega_{in}}{1 + R_{on}^2 C_H^2 \omega_{in}^2} - V_i \right) e^{-\frac{t}{R_{on} C_H}} \quad (V_{out}(0) = -V_i)$


where $\arctan \phi = R_{on} C_H \omega_{in} = 0.0219905$

Since $1 \text{ LSB} = \frac{2V_i}{2^8}$, we shall make the exponential term equal to -0.5 LSB

$$\Rightarrow V_i \left(\frac{R_{on} C_H \omega_{in}}{1 + R_{on}^2 C_H^2 \omega_{in}^2} - 1 \right) e^{-\frac{t}{R_{on} C_H}} = -0.5 \times \frac{2V_i}{2^8}$$

$$\Rightarrow \underline{t \approx 0.773 \text{ ns}}$$

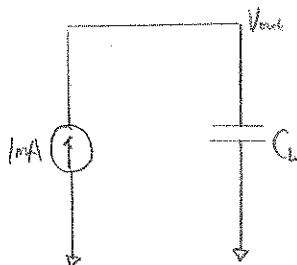2. (a) when S_1, S_2 turn off and S_3 turns on, $V_x < -0.2 \text{ V}$. So model should be:




This continues until $V_x = -0.2 \text{ V}$ which corresponds to $V_{out} = 0.9 \text{ V}$

Since $I = \frac{Q}{t} = \frac{C \Delta V}{t}$

$$\Rightarrow t = \frac{C \Delta V}{I} = \frac{0.7 \times 10^{-12} \times 0.9}{10^{-9}} = 0.63 \text{ ns}$$

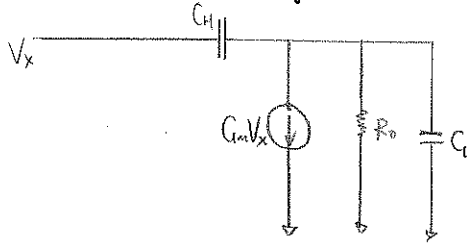After $V_x \geq -0.2V$, The equivalent circuit can be shown:



According to KCL at V_{out} ,

$$\frac{V_{out}}{R_o} + C_L \frac{dV_{out}}{dt} + G_m(V_{out} - 1.1) = 0$$

$$\Rightarrow \left(\frac{1}{R_o} + G_m\right) V_{out} + C_L \frac{dV_{out}}{dt} - 1.1 G_m = 0$$

Since $G_m = 0.025 \mu A/V$, $R_o = 20 k\Omega$, $C_L = 0.7 pF$.



Let $V_{out}(t) = A + B e^{-\frac{1}{R_o + \frac{1}{G_m} + C_L} t}$, $V_{out}(0) = 0.9V$

$$\Rightarrow \begin{cases} A = 1.0978 \\ B = -0.1978 \end{cases} \Rightarrow V_{out}(t) = 1.0978 - 0.1978 e^{-3.58 \times 10^{10} t}$$

To settle to 0.5LSB for 10-bit resolution, $V_{out}(t) = 1.0978 \left(1 - 0.5 \times \frac{1}{2^{10}}\right)$

$$\Rightarrow t \approx 0.165 ns$$

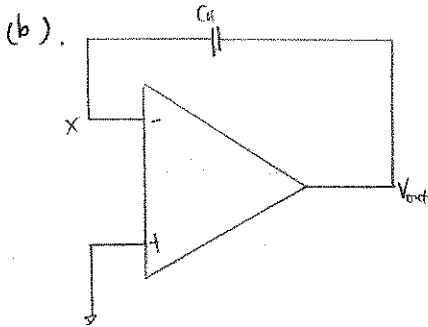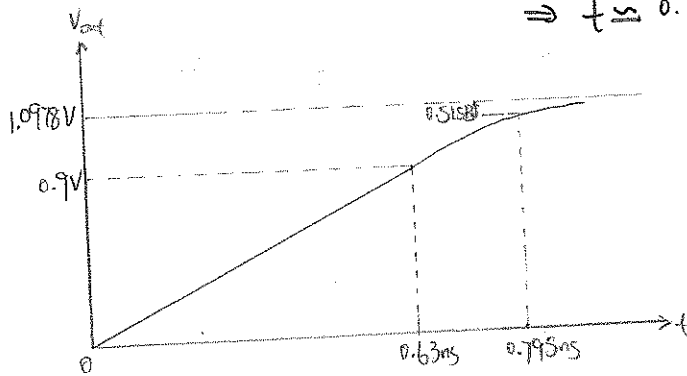$\Rightarrow$ Total hold settling time is $\frac{0.795 ns}{1010}$




According to charge conservation at node X, we have

$$(V_{out} - V_x) C_H = C_H \cdot V_{in} \quad \& \quad V_x = -\frac{V_{out}}{A_v}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{A_v}} \approx 1 - \frac{1}{A_v} = 1 - \frac{1}{G_m R_o}$$
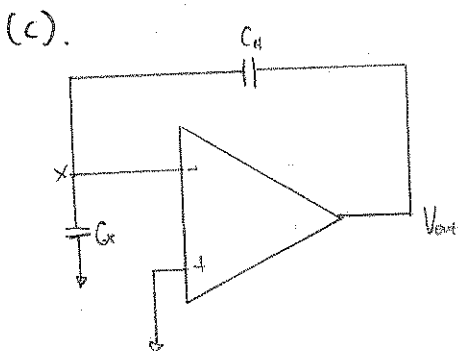
$$\Rightarrow \text{gain error} = \frac{1}{G_m R_o} = 0.2\% \quad \text{h/h}$$



According to charge conservation at node X, we have

$$V_x C_X - (V_{out} - V_x) C_H = -V_{in} \cdot C_H$$

$$\& \quad V_x = -\frac{V_{out}}{A_v}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{C_H}{C_H + \frac{1}{A_v} (C_H + C_X)} = \frac{1}{1 + \frac{1}{A_v} \cdot \frac{C_H + C_X}{C_H}} \approx 1 - \frac{1}{A_v} \cdot \frac{C_H + C_X}{C_H}$$

$$= 1 - \frac{3}{2 G_m R_o}$$

$$\Rightarrow \text{gain error} = \frac{3}{2 G_m R_o} = 0.3\% \quad \text{h/h}$$

3. (a).

$$V_{GS} = \sqrt{\frac{2I_0}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} \Rightarrow \Delta V_{in} = \Delta V_{GS} = \sqrt{\frac{2I_0}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{02}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$\Rightarrow \begin{cases} \Delta V_{in}^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{01} - 2\sqrt{I_{01}I_{02}}) \\ I_{01} + I_{02} = I_{SS} \end{cases}$$

$$\Rightarrow I_{01} - I_{02} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \Delta V_{in} \cdot \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (\Delta V_{in})^2}$$

$$\text{Since } \mu_n C_{ox} = 265 \times 10^{-6} \text{ A/V}^2,$$

$$\therefore (0.99 - 0.01) \times 203 \times 10^{-6} = \frac{1}{2} \times 265 \times 10^{-6} \times \frac{W}{L} \times 0.2 \times \sqrt{\frac{4 \times 203 \times 10^{-6}}{265 \times 10^{-6} \times \frac{W}{L}} - 0.2^2}$$

$$\Rightarrow \frac{W}{L} = 45.9 \text{ or } 30.7$$

$$\Rightarrow W = 8.3 \mu\text{m or } 5.5 \mu\text{m}$$

According to simulation, $W = 8.3 \mu\text{m}$ is the desired width to switch 99% of the tail current.

(b).

$$V_{out} = jI(R_L // \frac{r_o}{j}) = \frac{jR_L r_o}{R_L + \frac{r_o}{j}}; \text{ Ending point is } \frac{jR_L r_o}{R_L + \frac{r_o}{j}} \text{ when } j=N$$

$$\text{So } 1NL = \frac{jR_L r_o}{R_L + \frac{r_o}{j}} - \frac{jR_L r_o}{R_L + \frac{r_o}{j}} \cdot \frac{j}{N} = \frac{R_L(1 - \frac{j}{N})}{(R_L + \frac{r_o}{j})(R_L + \frac{r_o}{N})} \cdot jR_L r_o$$

$$\text{if } r_o \gg NR_L$$

$$\text{we have } 1NL = \frac{jR_L^2}{r_o} j(N-j)$$

$$\Rightarrow 1NL_{max} = \frac{jR_L^2}{4r_o} N^2 \text{ when } j = \frac{N}{2}$$

r_o is the cascode output impedance which equals to

$$(1 + g_m r_{o1}) r_{o2} + r_{o1}$$

$$g_m = \sqrt{2I_0 \mu_n C_{ox} \frac{W}{L}} = \sqrt{2 \times 0.99 \times 203 \times 10^{-6} \times 265 \times 10^{-6} \times 45.9} = 2.21 \text{ mA/V}^{-1}$$

$$r_{o1} = \frac{1}{\lambda_1 I_0} = \frac{1}{0.37 \times 0.99 \times 203 \times 10^{-6}} = 13.45 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_0} = \frac{1}{0.37 \times 203 \times 10^{-6}} = 13.31 \text{ k}\Omega$$

$$\Rightarrow r_o = 422.4 \text{ k}\Omega$$

$$\Rightarrow 1NL_{max} = \frac{203 \times 10^{-6} \times 50^2}{4 \times 422.4 \times 10^3} \times 64^2 = 1.23 \text{ mV}$$

(c).

$$1NL_{max} = \frac{jR_L^2}{4r_o} N^2 = 0.5LSB = 0.5 \times \frac{0.65}{2} = 0.317 \text{ mV}$$

$$\Rightarrow \frac{r_o'}{r_o} = \frac{1.23}{0.317} \Rightarrow 30.72 r_{o2} + r_{o1} = 1638.96 \text{ k}\Omega \Rightarrow \lambda_2' = 0.093$$

$$\Rightarrow L' = \frac{\lambda}{\lambda_2'} L = \frac{0.37}{0.093} \times 0.18 = 0.72 \mu\text{m}$$

$$\text{The minimum width is } W = \frac{2I_0}{\mu_n C_{ox} \frac{1}{L} V_{DD}^2} = \frac{2 \times 203 \times 10^{-6}}{265 \times 10^{-6} \times \frac{1}{0.72 \mu\text{m}} \times 0.25^2} = 17.65 \mu\text{m}$$

(d) The schematic is shown below:

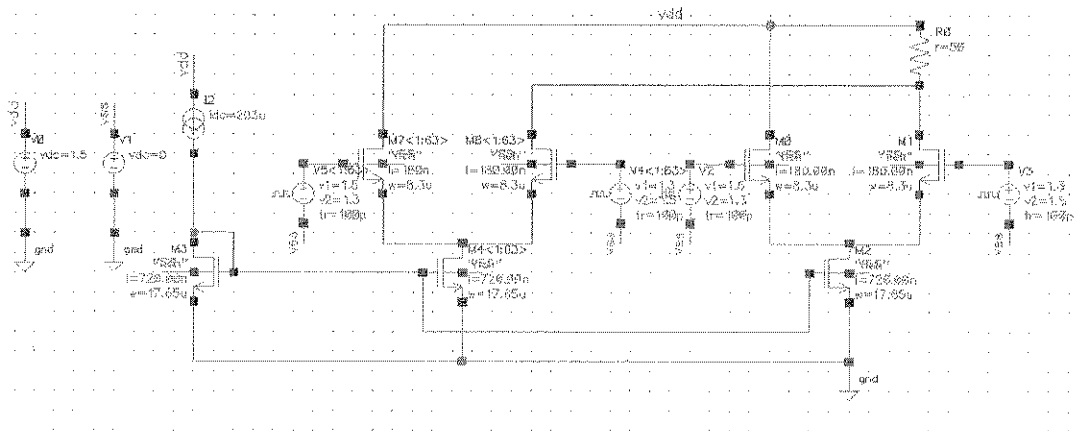


Figure 1 64 segmented DAC schematic

Transient simulation for output voltage is shown:

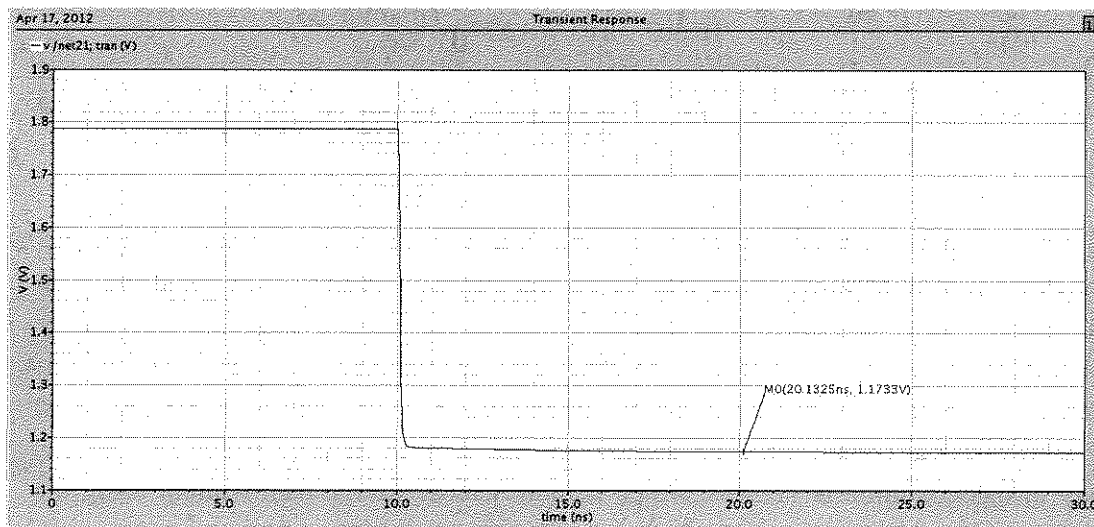


Figure 2 Output transient simulation

The final value is 1.173V, adding 0.5LSB which is 0.317mV corresponds to the voltage of 1.1733V. And settling time is:

$$20.13 - 10.09 = 10.04 \text{ ns}$$

(e) After adding a 1uF capacitor, the transient response is shown:

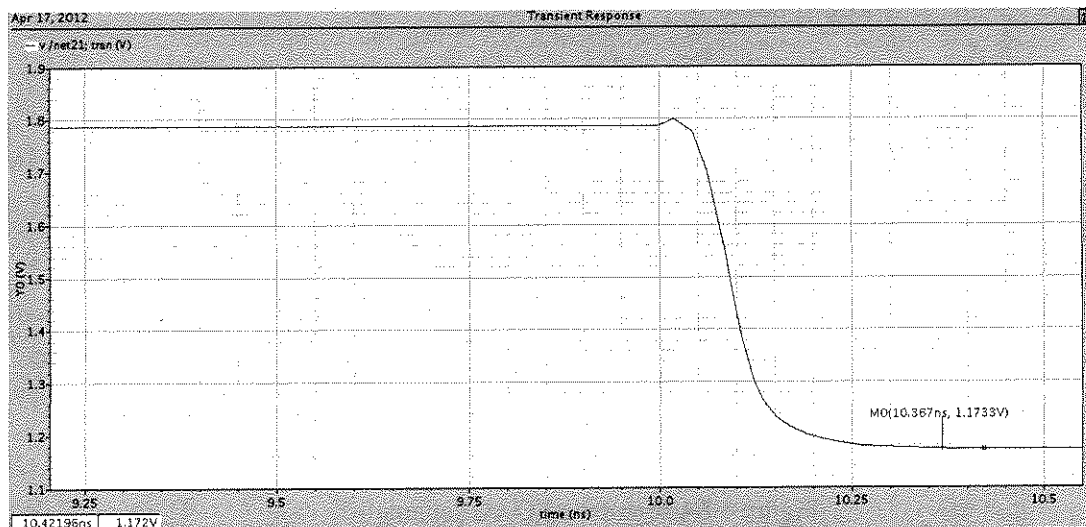


Figure 3 Output transient simulation with 1uF filtering capacitor

The settling time now drops to

$$10.367 - 10.09 = 277\text{ps}$$

This capacitor improves speed dramatically because it makes the bias voltage for the tail current source relatively stable. Thus, coupling effect from the tail node to the gate bias point is reduced. Therefore, the settling speed is quite fast.

(f) If the maximum capacitor is 4pF, I will **not use it** to increase the speed because this increases the time constant at the gate of the tail current source. Even though this cap reduces the voltage jump at the bias node, it results longer time to recover because of the increased time constant. As a result, speed may be even worse than without the capacitor. Simulation results in figure 4 have proven this analysis. It is clear that with 4pF capacitor, the instantaneous voltage drop is reduced, but the recovering time is longer. Finally, delay in this condition is 12.28ns, which is more than 2ns large than without using the capacitor.

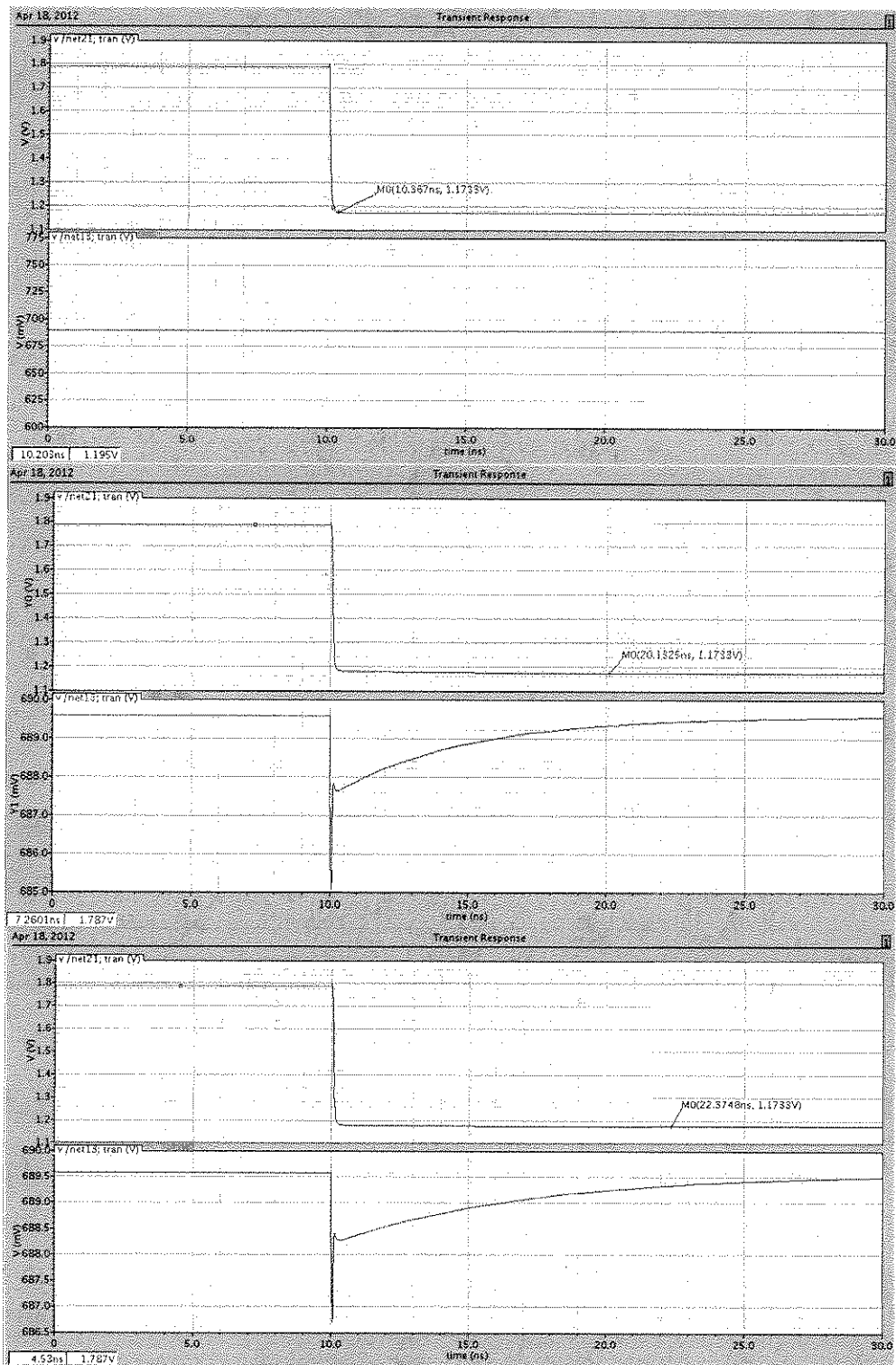


Figure 4 Transient simulation of output and gate of tail current source
(with 1uF cap, without cap, with 4pF cap)

